

Introduction To Small Signal And Averaged Switch Modeling

Robert V. White

bob.white@embeddedpowerlabs.com

Seminar Prepared For APEC 2015

Seminar Introduction

- This Is An Introductory Seminar
 - Why Do We Need Small Signal Modeling?
 - Small Signal Model Derivation
 - Deriving Transfer Functions From The Small Signal Model
 - Averaged Switch Modeling
- Detailed Examples (All The Algebra)




Seminar Introduction: Not Discussed

- Models For Discontinuous Conduction Mode
- Control Loop Design
 - Error Amp/Compensator Design
 - Pole-Zero Placement
 - Loop Stability

Seminar Introduction

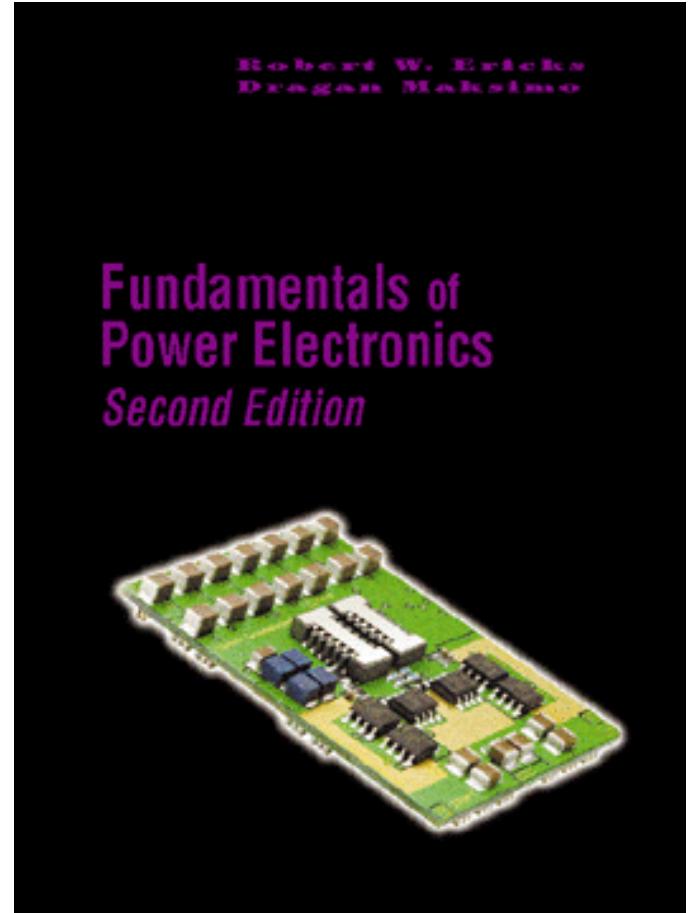
- Much Of This Seminar Is Based On Material From “Fundamentals Of Power Electronics”, 2nd Edition, Erickson & Maksimovic, Kluwer Academic Publishers, ISBN 0-7923-7270-0
 - Chapter 7, AC Equivalent Circuit Modeling
 - Chapter 8, Converter Transfer Functions



Seminar Introduction


- Timing
 - 90 Minutes Presentation
 - 30 Minute Break
 - 90 Minutes Presentation
- Ask Questions At Any Time
- Fill Out The Survey Form!

Controls 101 Review

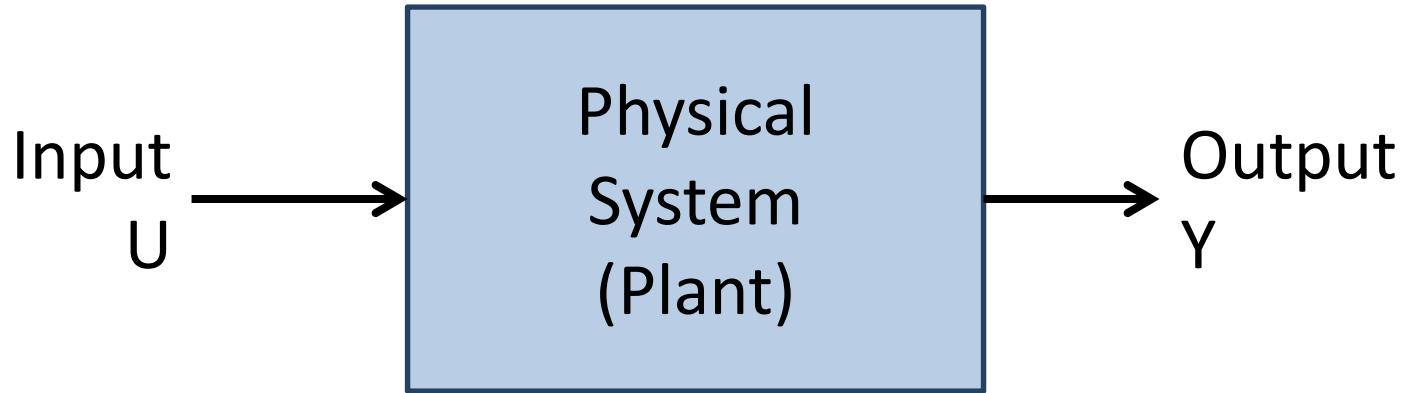

Issue: The Actual Output
Is Not The Desired Output

Feedback

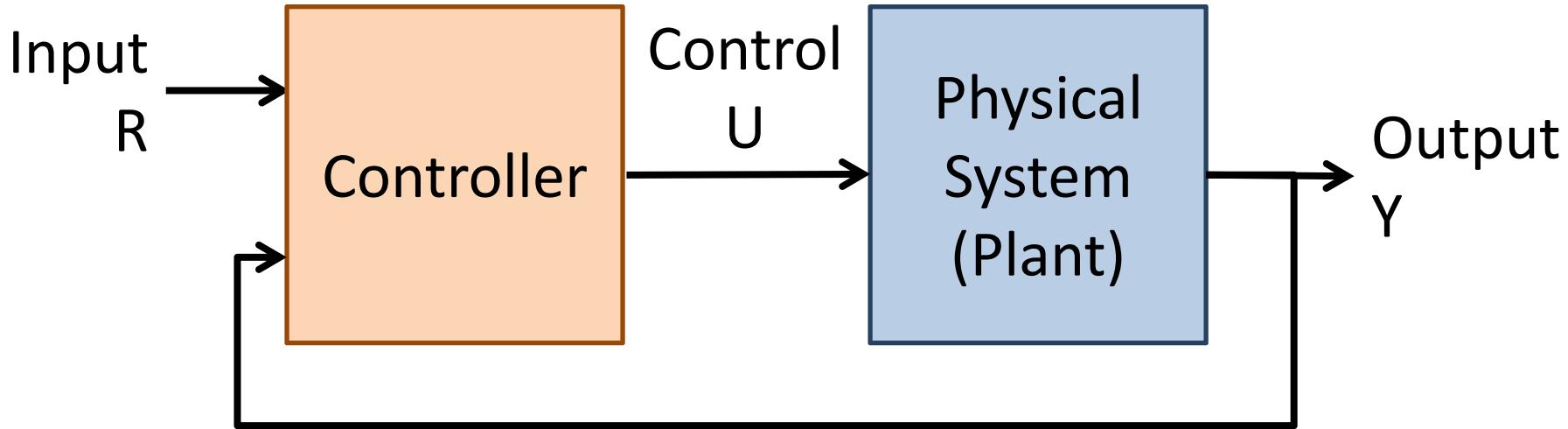

Goals:


- Make the output track the reference input
- Reject disturbances

Requirement: Remain stable at all times

Stability

- Bounded Input-Bounded Output (BIBO)
 - Finite input results in finite output
- Lyapunov
 - System has an equilibrium point or points
 - Small disturbance from equilibrium results in small change in output
 - Exponential: Output change decays in time

Design And Analysis

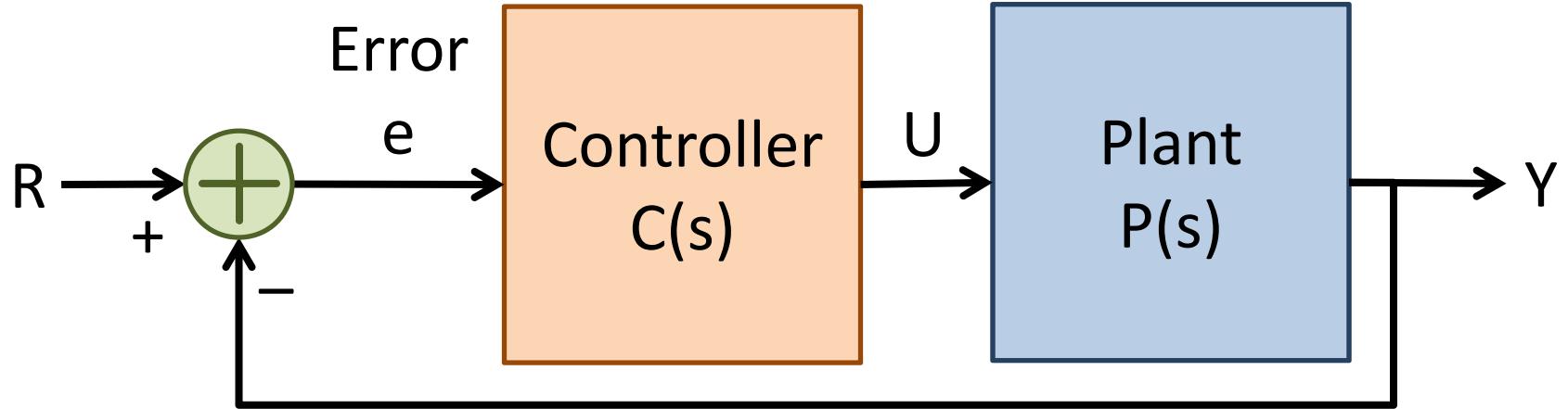

- Time domain solutions too tedious
- Transform to frequency or s domain

$$Y(s) = \frac{P(s) \cdot C(s)}{1 + P(s) \cdot C(s)} \cdot R(s)$$

$$H(s) = \frac{Y(s)}{R(s)} = \frac{P(s) \cdot C(s)}{1 + P(s) \cdot C(s)}$$



Design And Analysis

R —

→ Y

Stable Means

This Term Can Never Be Equal To Zero

$H(s)$ Has No Poles In RHP

No RHP Poles In $P(s)$ Or $C(s)$


Cancelled By Matching RHP Zeroes

$$Y(s) = \frac{P(s) \cdot C(s)}{1 + P(s) \cdot C(s)} \cdot R(s)$$


$$H(s) = \frac{Y(s)}{R(s)} = \frac{P(s) \cdot C(s)}{1 + P(s) \cdot C(s)}$$



Design And Analysis

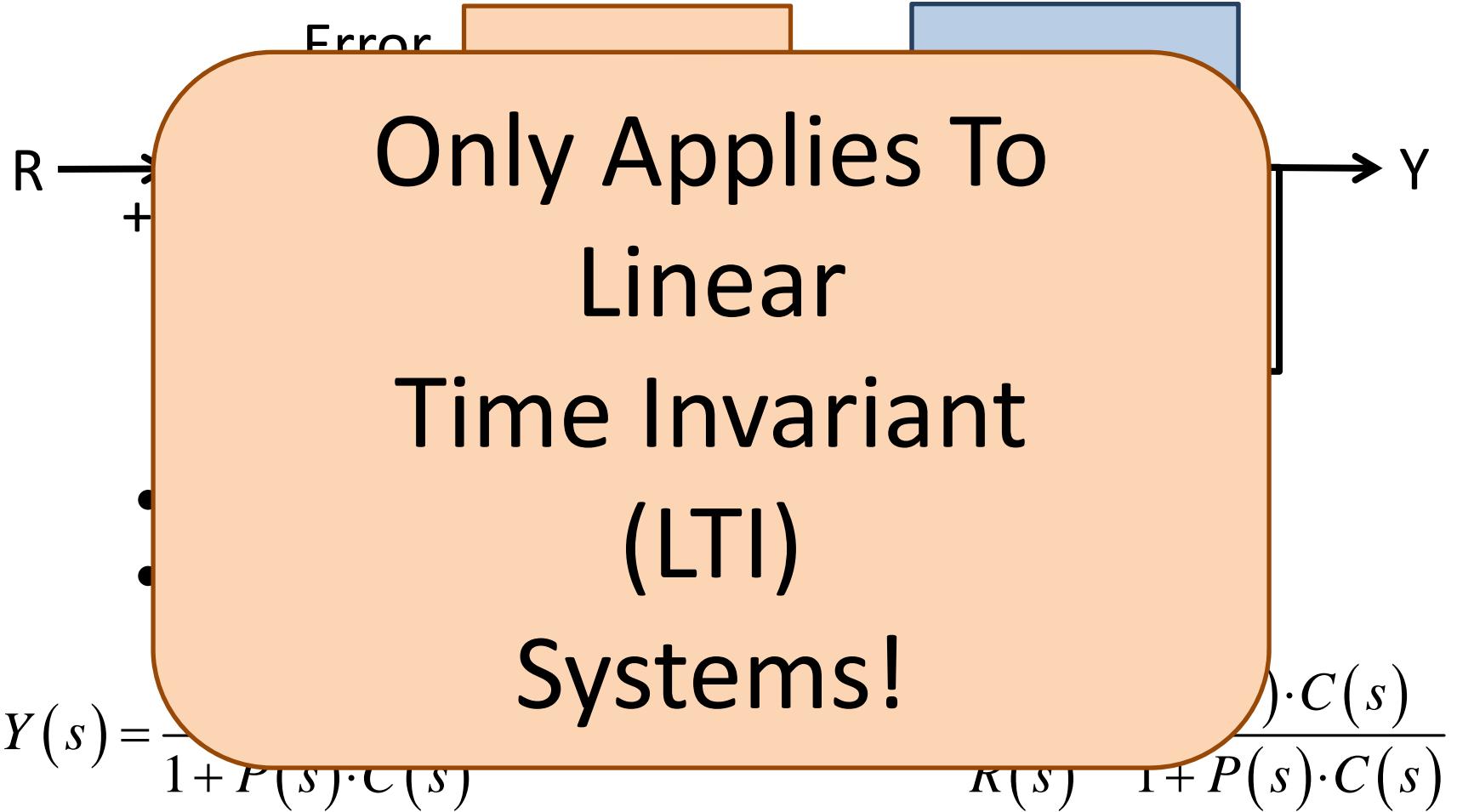

Power Supply Model

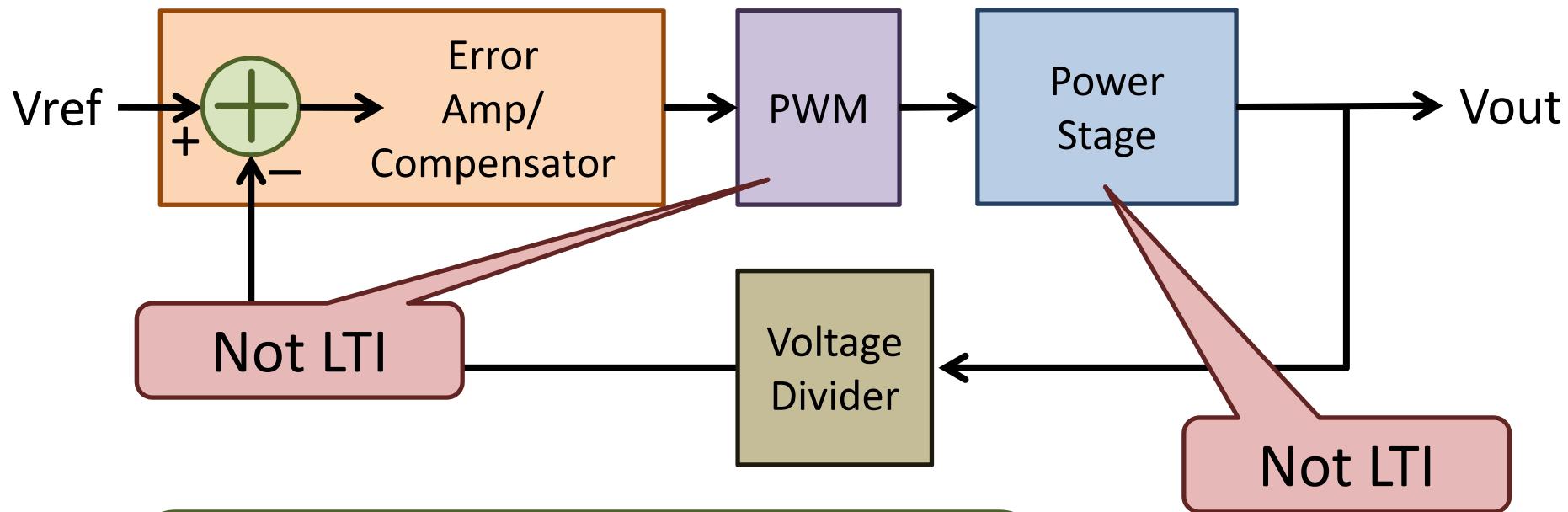


We Need Circuit Models
Valid In The s-Domain




Small Signal Modeling

$$i_D(t) = I_D + \hat{i}_D(t)$$

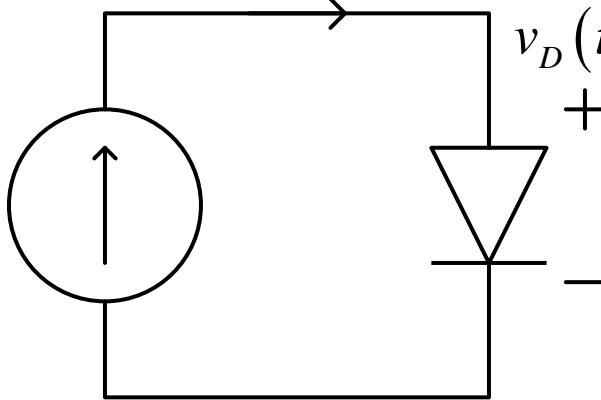


$$v_D(t) = V_D + \hat{v}_D(t)$$

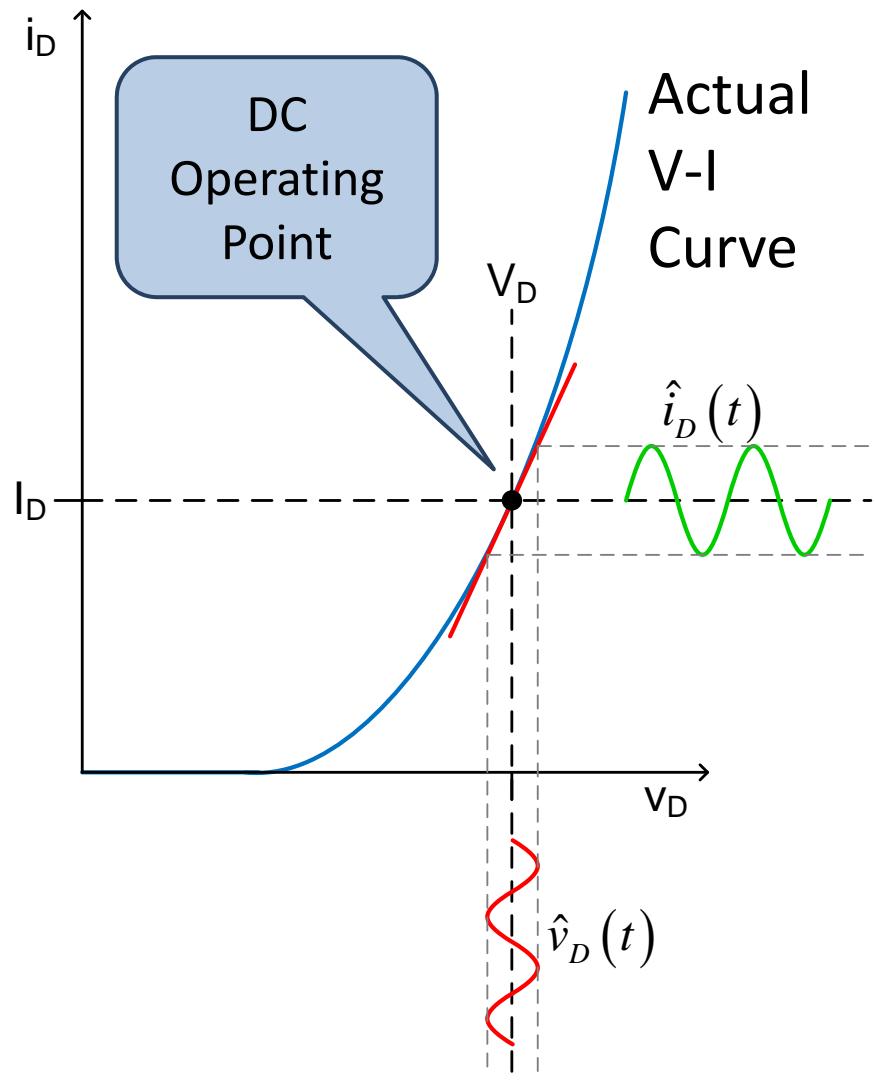


Small Signal Modeling

$$i_D(t) = I_D + \hat{i}_D(t)$$

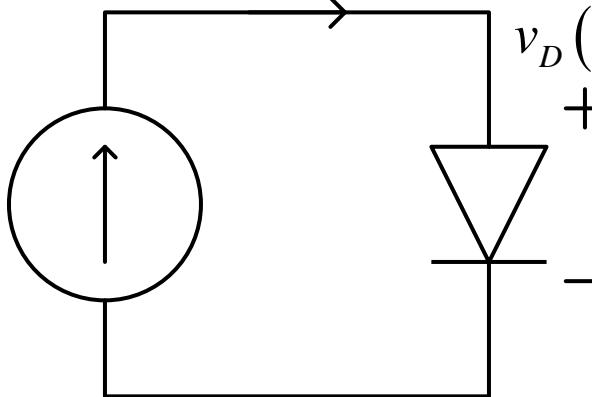


$$v_D(t) = V_D + \hat{v}_D(t)$$

Linearized
Characteristic
 r_e

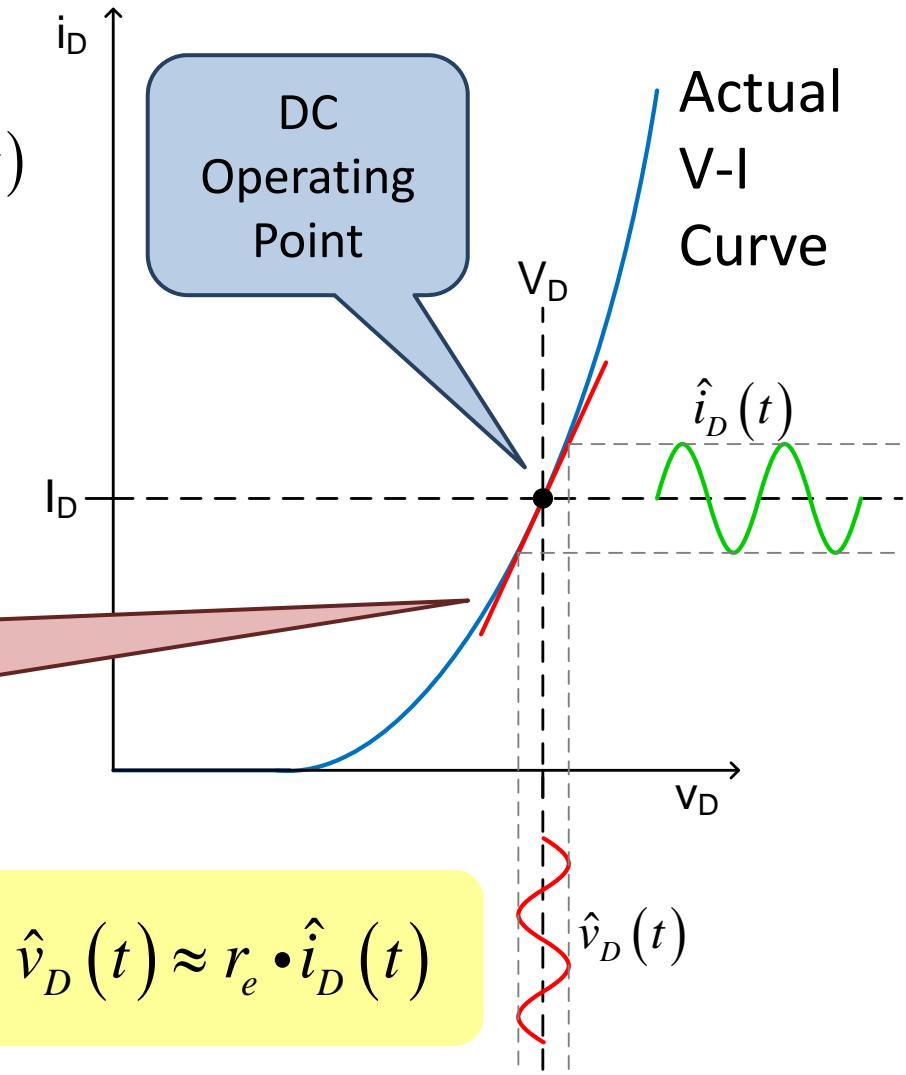

$$\hat{v}_D(t) \approx r_e \cdot \hat{i}_D(t)$$

DC Model

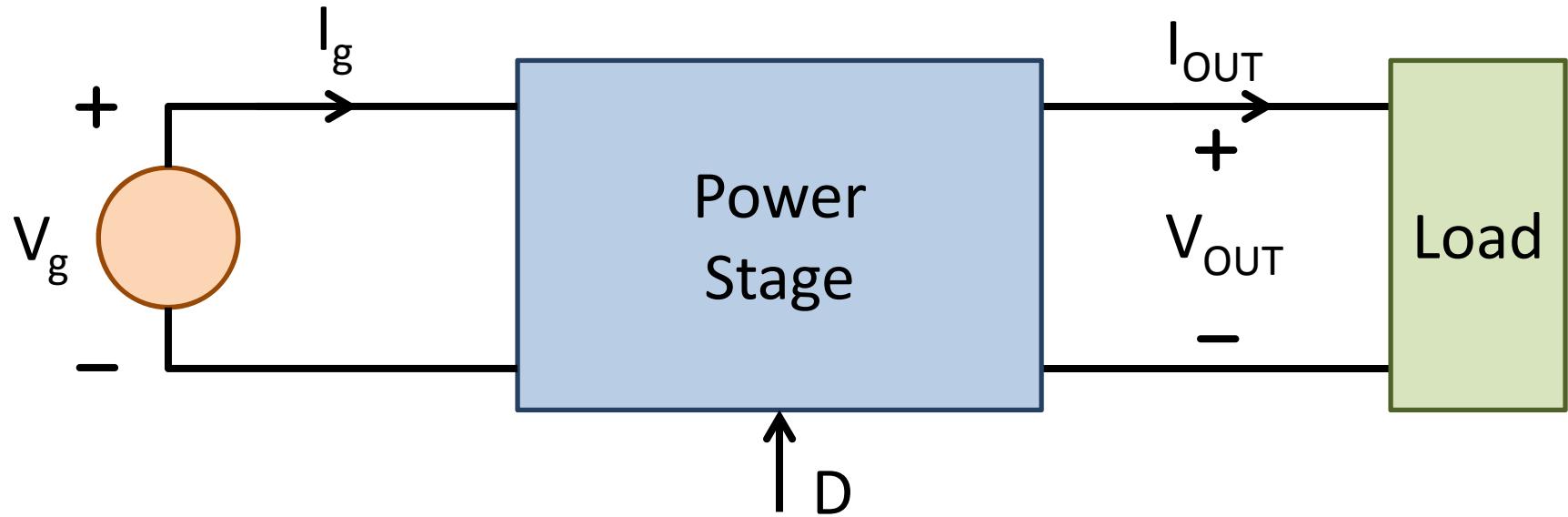

Inputs


- Input Voltage, V_g
 - Control Input, D
 - Load
-
- Resistance, R
 - Current, I_{LOAD}
 - Voltage, V_{LOAD}

Outputs



- Output Voltage, V_{OUT}
- Input Current, I_g



DC Model

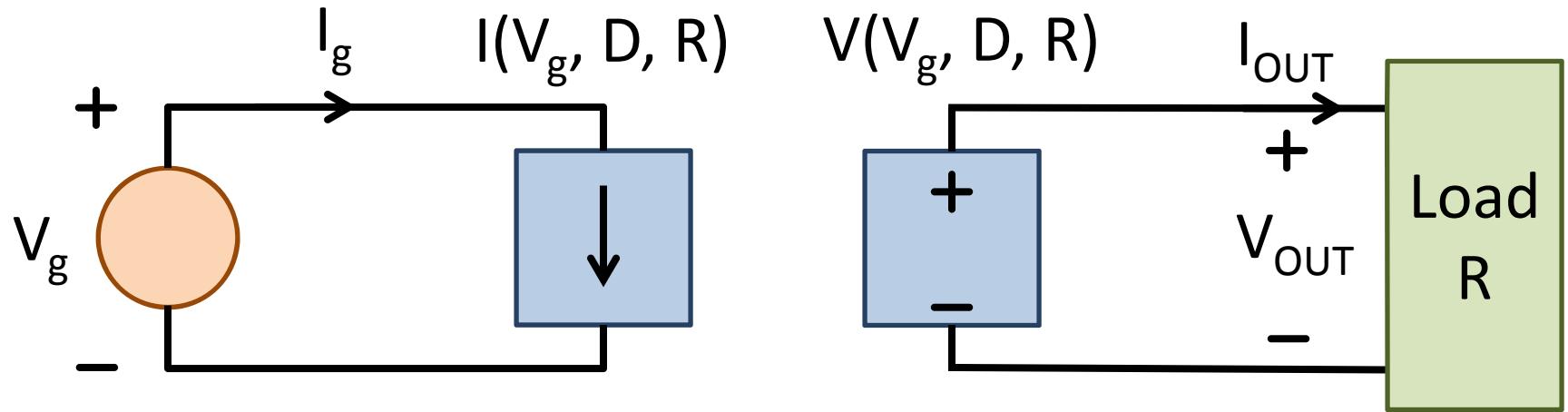

Buck Converter DC Model

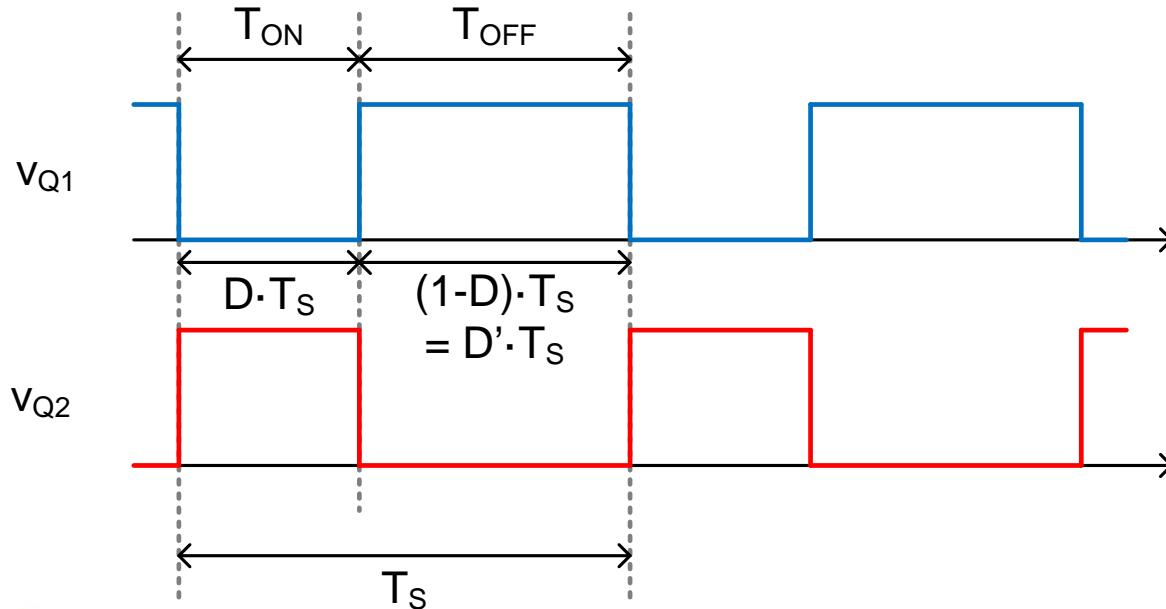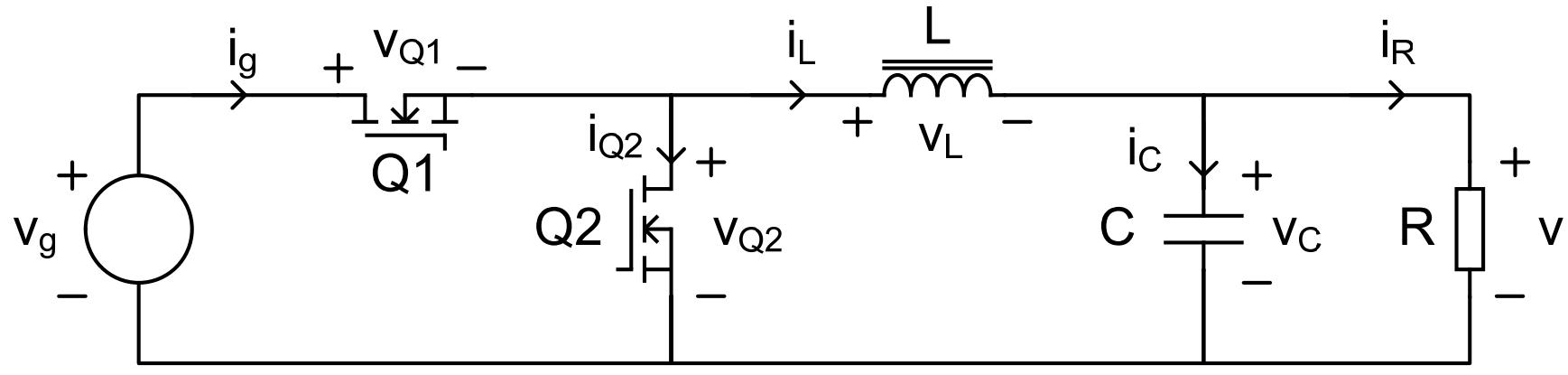

Solving The Output Voltage

$$\langle v_L(t) \rangle_{T_S} = \langle v_L(t) \rangle = \frac{1}{T_S} \cdot \int_0^{T_S} v_L(t) dt = 0$$

Inductor Volt-Second Balance

$$\frac{1}{T_S} \cdot \int_0^{T_S} v_L(t) dt = \frac{1}{T_S} \left(\int_0^{T_{ON}} v_L(t) dt + \int_{T_{ON}}^{T_S} v_L(t) dt \right) = 0$$

$$\int_0^{T_{ON}} (v_g - v_C(t)) dt + \int_{T_{ON}}^{T_S} (-v_C(t)) dt = 0$$

Small Ripple Approximation

$$v_g(t) = V_g + \tilde{v}_g(t)$$

$$v_C(t) = V_C + \tilde{v}_C(t)$$

$$|\tilde{v}_g(t)| \ll V_g$$

$$|\tilde{v}_C(t)| \ll V_C$$

$$v_g(t) = V_g + \tilde{v}_g(t) \approx V_g$$

$$v_C(t) = V_C + \tilde{v}_C(t) \approx V_C$$



Solving The Output Voltage

$$\int_0^{T_{ON}} (V_g - V_C) dt + \int_{T_{ON}}^{T_S} (-V_C) dt = 0$$

$$(V_g - V_C) \cdot T_{ON} - V_C \cdot (T_S - T_{ON}) = 0$$

$$(V_g - V_C) \cdot D \cdot T_S - V_C \cdot (T_S - D \cdot T_S) = 0$$

$$(V_g - V_C) \cdot D - V_C \cdot (1 - D) = 0$$

$$D \cdot V_g - D \cdot V_C - V_C + D \cdot V_C = 0$$

$$D \cdot V_g - V_C = 0$$

$$V_C = D \cdot V_g$$

Solving The Inductor Current

$$\langle i_C(t) \rangle_{T_s} = \langle i_C(t) \rangle = 0$$

Capacitor Charge Balance

$$\frac{1}{T_s} \cdot \int_0^{T_s} i_C(t) dt = \frac{1}{T_s} \cdot \left(\int_0^{T_{on}} i_C(t) dt + \int_{T_{on}}^{T_s} i_C(t) dt \right) = 0$$

$$\int_0^{T_{on}} i_C(t) dt + \int_{T_{on}}^{T_s} i_C(t) dt = 0$$

$$\int_0^{T_{on}} \left(i_L(t) - \frac{1}{R} \cdot v_C(t) \right) dt + \int_{T_{on}}^{T_s} \left(i_L(t) - \frac{1}{R} \cdot v_C(t) \right) dt = 0$$

$$\int_0^{T_s} \left(i_L(t) - \frac{1}{R} \cdot v_C(t) \right) dt = 0$$

Solving The Inductor Current

$$v_C(t) \approx V_C$$

$$i_L(t) = I_L + \tilde{i}_L(t)$$

Small Ripple Approximation

$$|\tilde{i}_L(t)| \ll I_L$$

$$i_L(t) = I_L + \tilde{i}_L(t) \approx I_L$$

$$\int_0^{T_S} \left(I_L - \frac{1}{R} \cdot V_C \right) dt = 0$$

$$\left(I_L - \frac{1}{R} \cdot V_C \right) \cdot T_S = 0$$

$$I_L - \frac{1}{R} \cdot V_C = 0$$

$$I_L = \frac{1}{R} \cdot V_C$$

Solving The Input Current

$$\langle i_g(t) \rangle_{T_S} = \langle i_g(t) \rangle = I_g = \frac{1}{T_S} \cdot \int_0^{T_S} i_g(t) dt$$

$$I_g = \frac{1}{T_S} \cdot \left(\int_0^{T_{ON}} i_g(t) dt + \int_0^{T_{OFF}} i_g(t) dt \right)$$

$$= \frac{1}{T_S} \cdot \left(\int_0^{T_{ON}} i_g(t) dt + \int_0^{T_{OFF}} 0 dt \right) = \frac{1}{T_S} \cdot \int_0^{T_{ON}} i_g(t) dt$$



$$i_g(t) = i_L(t) \approx I_L$$

From The
Small Ripple
Approximation


$$I_g = \frac{1}{T_S} \cdot I_L \cdot T_{ON} = \frac{1}{T_S} \cdot I_L \cdot D \cdot T_S = D \cdot I_L = D \cdot \frac{1}{R} \cdot V_C = D \cdot I_{OUT}$$



Buck Converter DC Model

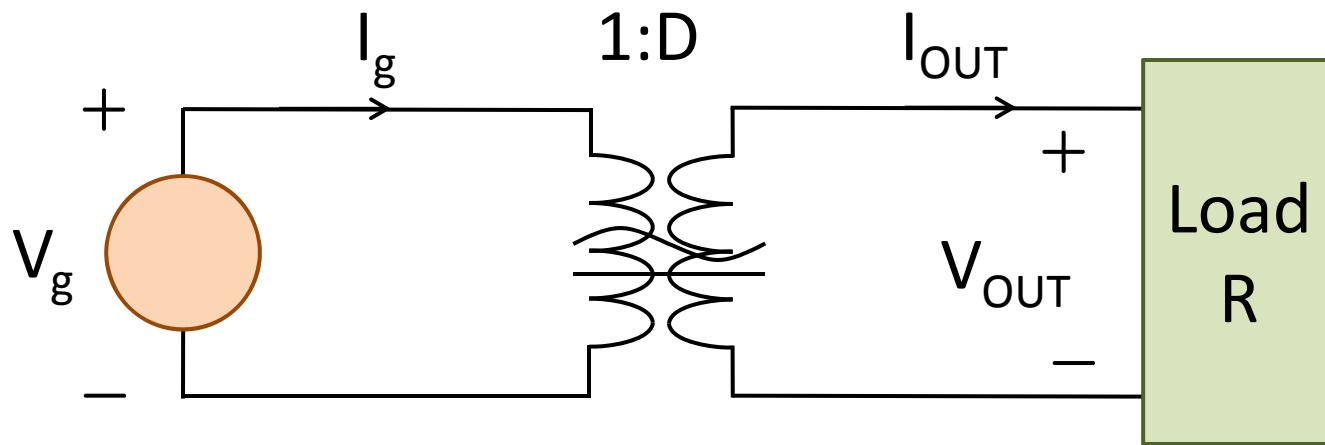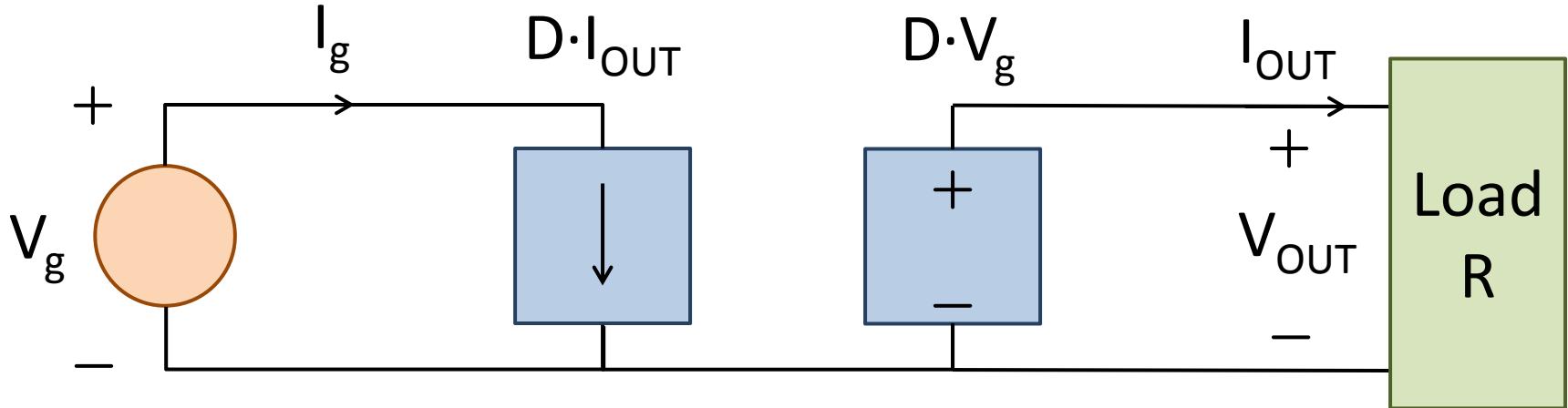

AC (Small Signal) Modeling

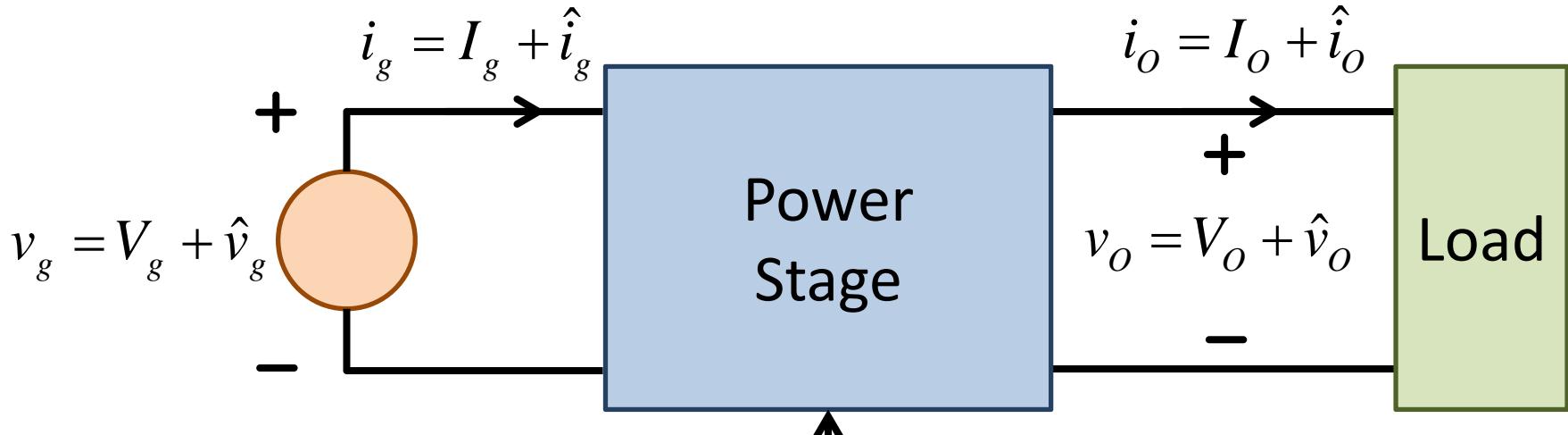


$$|\hat{v}_g| \ll V_g$$

$$|\hat{i}_g| \ll I_g$$

$$|\hat{v}_o| \ll V_o$$

$$|\hat{i}_o| \ll I_o$$


$$|\hat{d}| \ll D$$

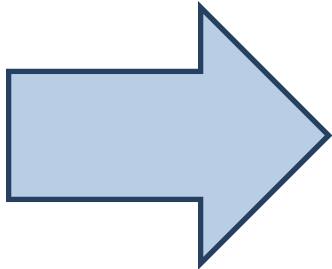

Small
Signal
Modeling

How Small is Small?
Small Enough The
System Remains
Linear


AC Modeling

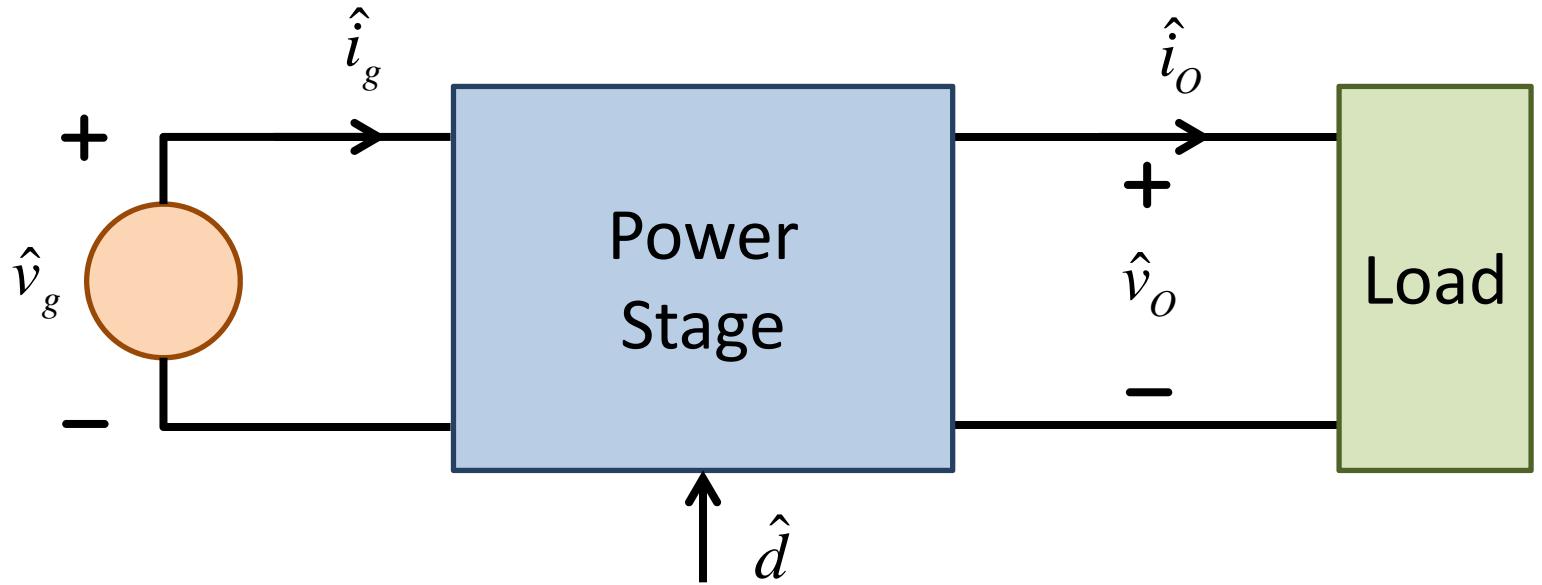

Control To Output
Transfer Function

$$G_{vd} = \left. \frac{\hat{v}_o}{\hat{d}} \right|_{\hat{v}_g=0}$$

AC Modeling

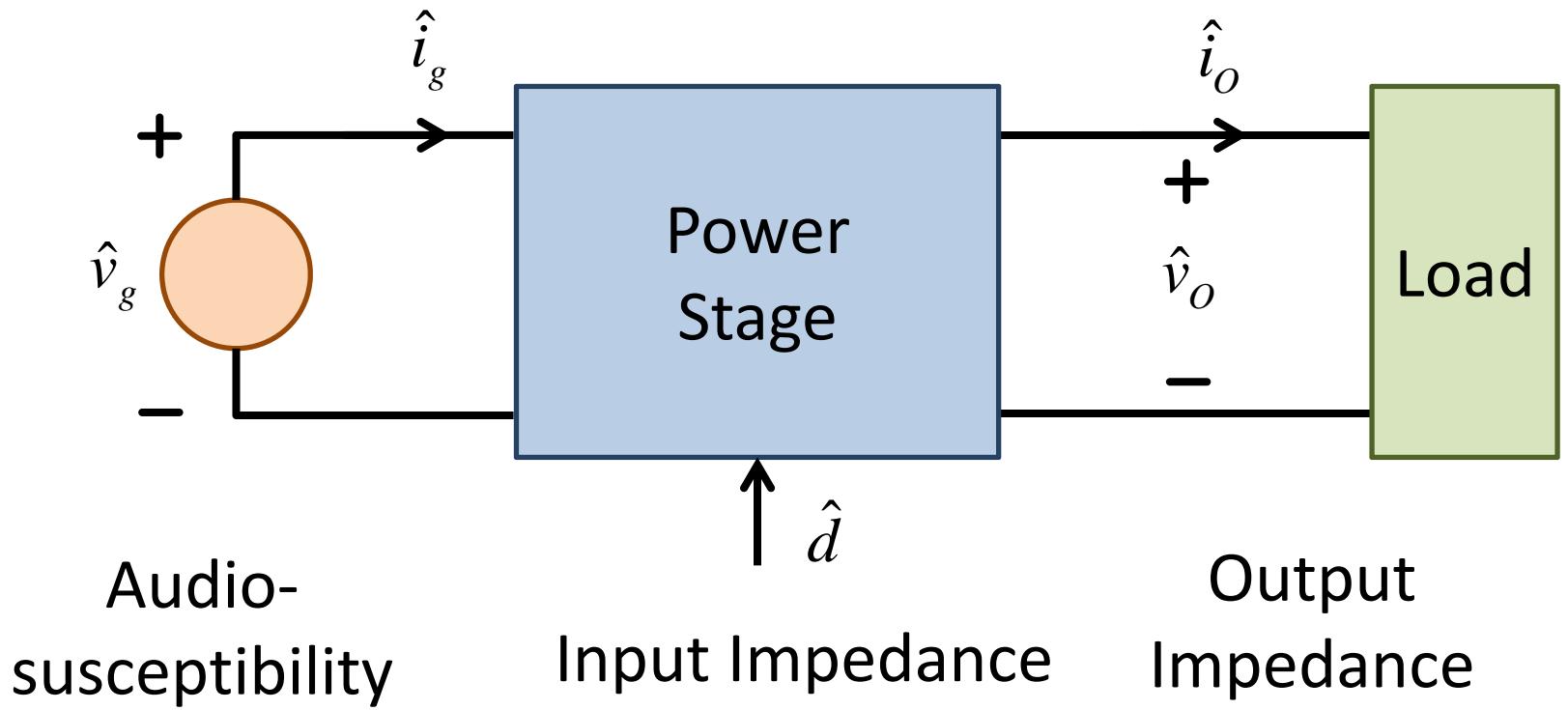


$$G_{vg} = \frac{\hat{v}_o}{\hat{v}_g} \Big|_{\hat{d}=0}$$


$$Z_i = \frac{\hat{v}_g}{\hat{i}_g} \Big|_{\hat{d}=0}$$

$$Z_o = \frac{\hat{v}_o}{\hat{i}_o} \Big|_{\hat{d}=0, \hat{v}_g=0}$$

Averaging

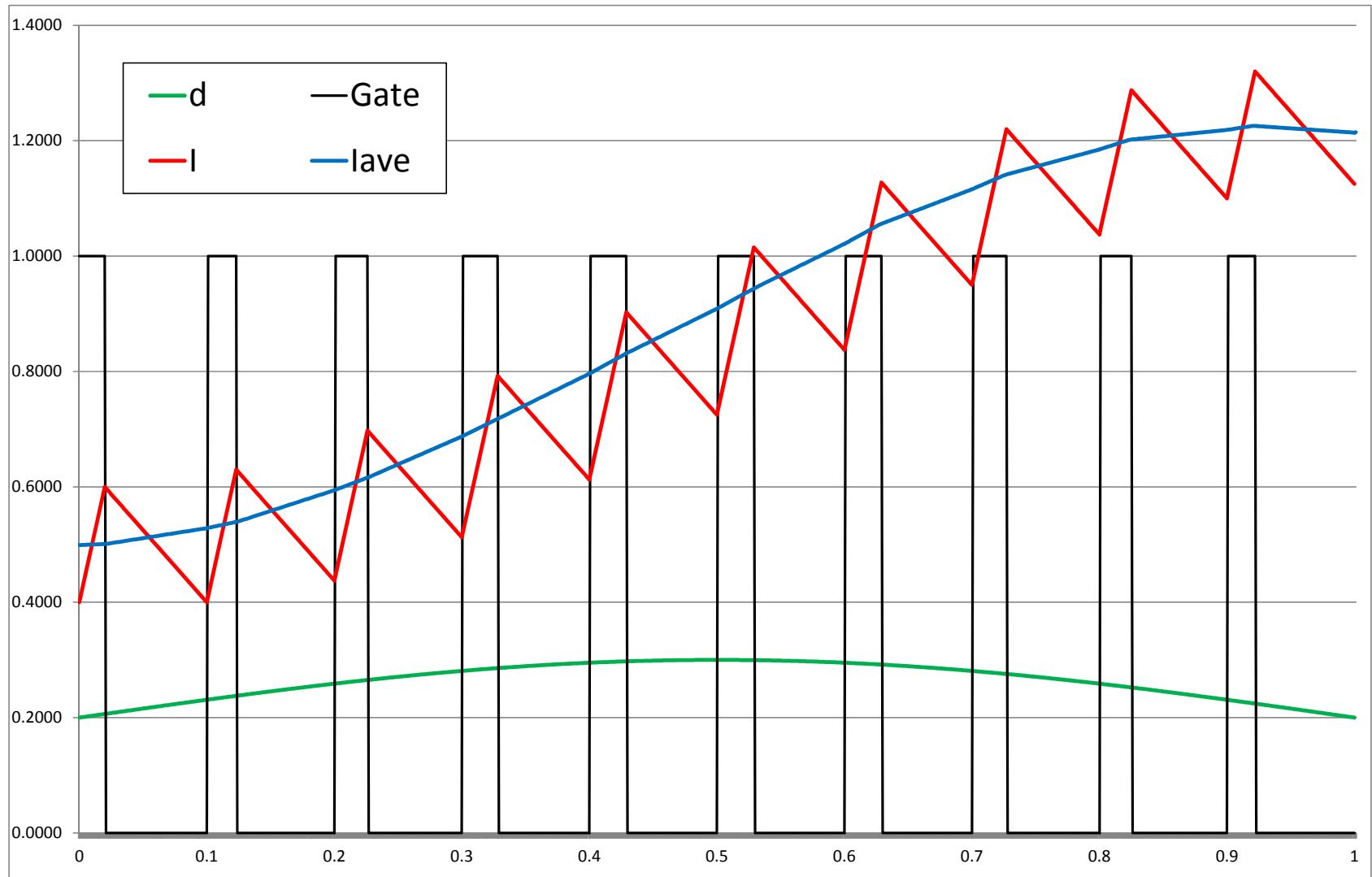



Averaging

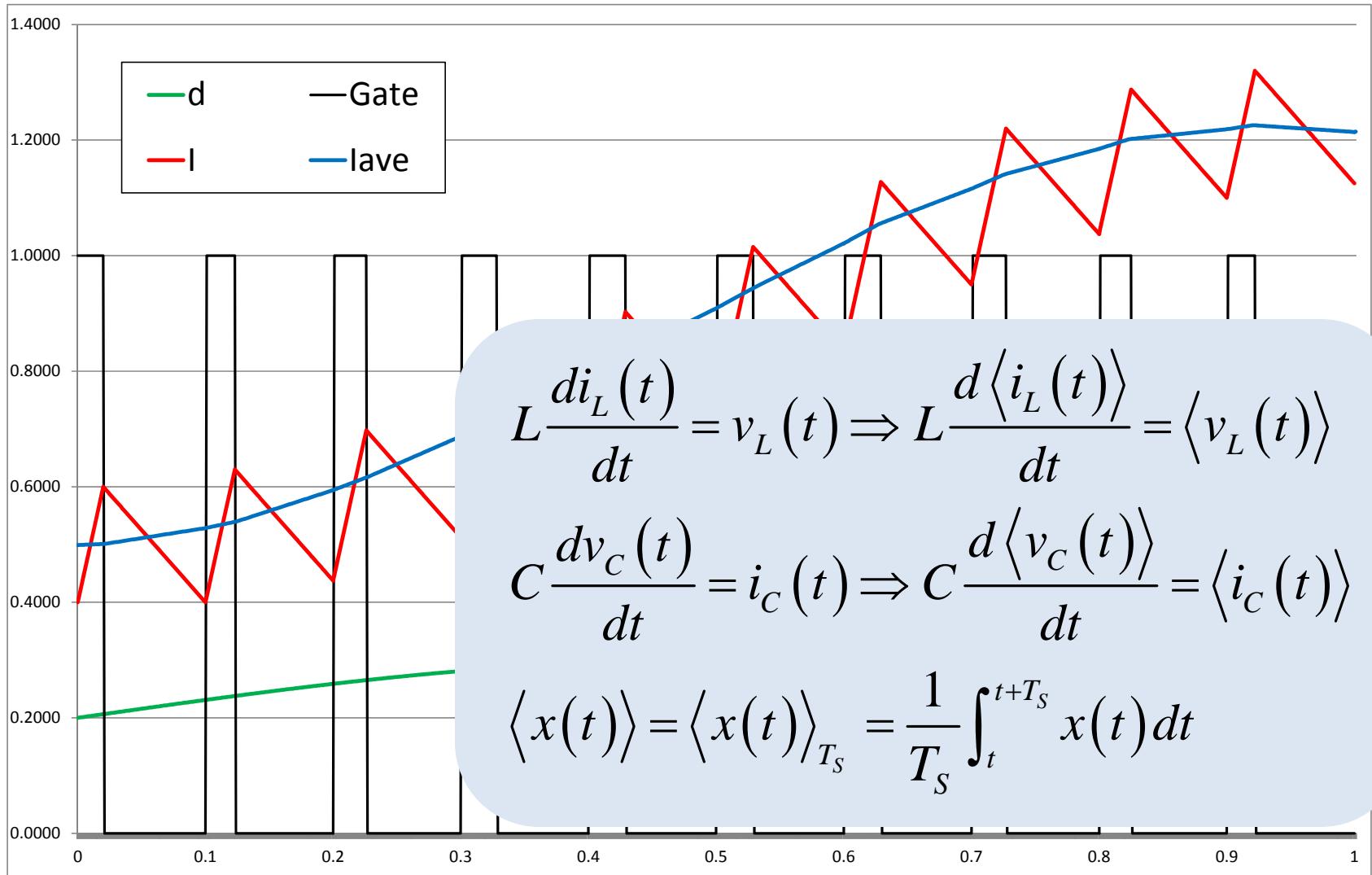

Another View Of Averaging



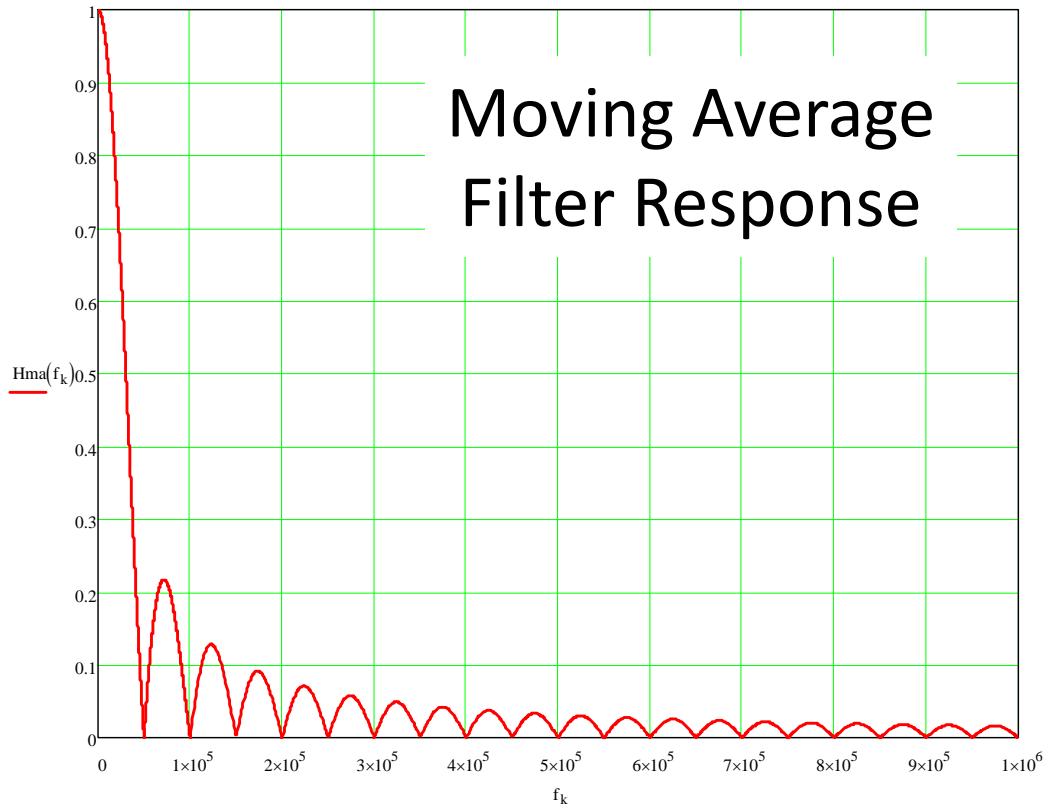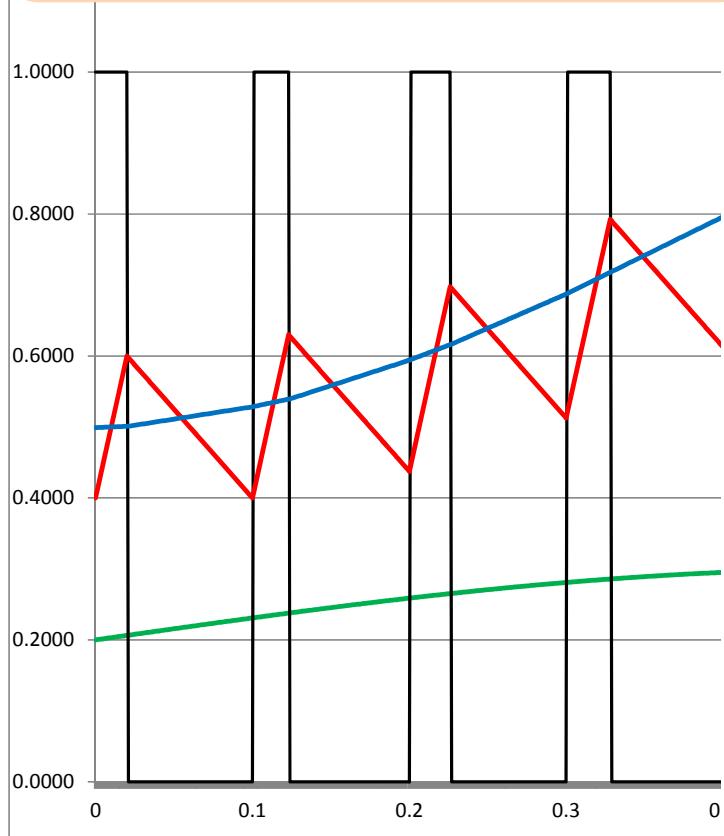
$$\langle x(t) \rangle = \langle x(t) \rangle_{T_S} = \frac{1}{T_S} \cdot \int_t^{t+T_S} x(t) dt$$



Moving Average
Filter Response

Modeling The Buck Converter: On Time

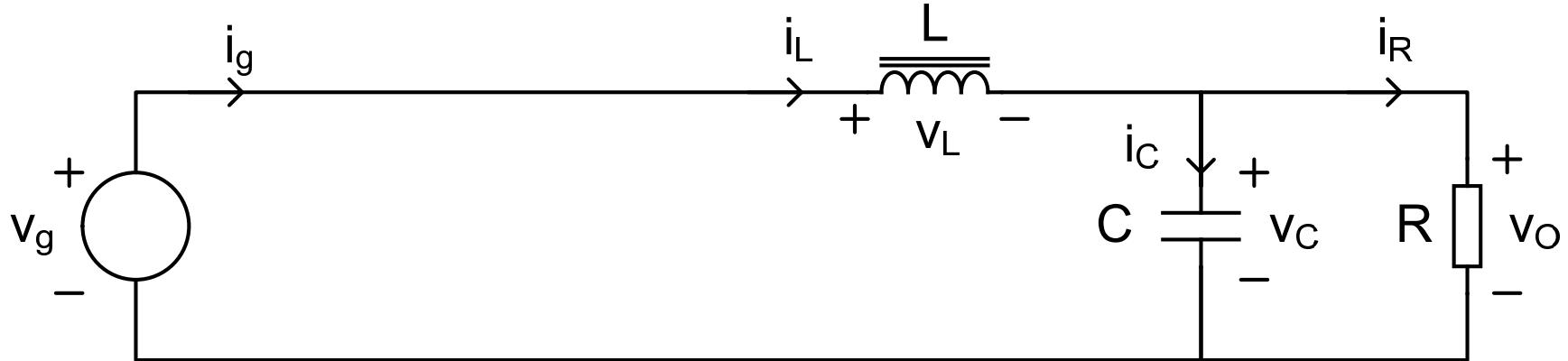


$$v_L(t) = L \frac{di_L(t)}{dt} = v_g(t) - v_o(t) \approx \langle v_g(t) \rangle - \langle v_C(t) \rangle$$

$$i_C(t) = C \frac{dv_C(t)}{dt} = i_L(t) - \frac{1}{R} v_C(t) \approx \langle i_L(t) \rangle - \frac{1}{R} \langle v_C(t) \rangle$$

Small Ripple Approximation

Modeling The Buck Converter: Off Time

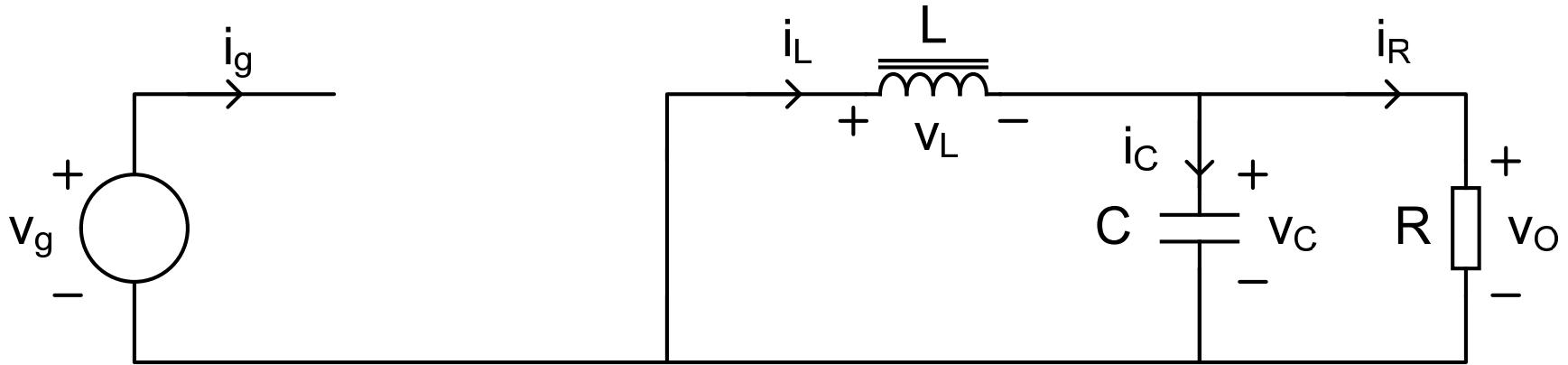

$$v_L(t) = L \frac{di_L(t)}{dt} = -v_C(t) \approx -\langle v_C(t) \rangle$$

$$i_C(t) = C \frac{dv_C(t)}{dt} = i_L(t) - \frac{1}{R} v_C(t) \approx \langle i_L(t) \rangle - \frac{1}{R} \langle v_C(t) \rangle$$

Averaging The Inductor Voltage

$$\begin{aligned}\langle v_L(t) \rangle &= \frac{1}{T_S} \int_t^{t+T_S} v_L(\tau) d\tau \\ &\approx d(t) \cdot (\langle v_g(t) \rangle - \langle v_C(t) \rangle) + d'(t) \cdot (-\langle v_C(t) \rangle) \\ &= d(t) \cdot (\langle v_g(t) \rangle - \langle v_C(t) \rangle) + (1 - d(t)) \cdot (-\langle v_C(t) \rangle) \\ &= d(t) \cdot \langle v_g(t) \rangle - d(t) \cdot \langle v_C(t) \rangle - \langle v_C(t) \rangle + d(t) \cdot \langle v_C(t) \rangle \\ &= d(t) \cdot \langle v_g(t) \rangle - \langle v_C(t) \rangle\end{aligned}$$

$$\langle v_L(t) \rangle = L \frac{d \langle i_L(t) \rangle}{dt} = d(t) \cdot \langle v_g(t) \rangle - \langle v_C(t) \rangle$$



Averaging The Capacitor Current

$$\begin{aligned}\langle i_c(t) \rangle &= d(t) \cdot \left(\langle i_L(t) \rangle - \frac{1}{R} \cdot \langle v_C(t) \rangle \right) + d'(t) \cdot \left(\langle i_L(t) \rangle - \frac{1}{R} \cdot \langle v_C(t) \rangle \right) \\ &= \langle i_L(t) \rangle - \frac{1}{R} \cdot \langle v_C(t) \rangle\end{aligned}$$

$$\langle i_c(t) \rangle = C \frac{d \langle v_C(t) \rangle}{dt} = \langle i_L(t) \rangle - \frac{1}{R} \cdot \langle v_C(t) \rangle$$

Averaging The Input Current

$$\begin{aligned}\langle i_g(t) \rangle &= d(t) \cdot \langle i_L(t) \rangle + d'(t) \cdot 0 \\ &= d(t) \cdot \langle i_L(t) \rangle\end{aligned}$$



Perturb And Linearize

DC Operating Point

$$V_g \quad V_C = D \cdot V_g$$

$$I_L = \frac{1}{R} \cdot V_C \quad I_g = D \cdot I_L$$

Input Perturbation

$$\langle v_g(t) \rangle = V_g + \hat{v}_g(t)$$

$$d(t) = D + \hat{d}(t)$$

Resulting Output Perturbation

$$\langle i_L(t) \rangle = I_L + \hat{i}_L(t)$$

$$\langle v_C(t) \rangle = V_C + \hat{v}_C(t)$$

$$\langle i_g(t) \rangle = I_g + \hat{i}_g(t)$$

Small Signal Constraint

$$|\hat{v}_g(t)| \ll |V_g| \quad |\hat{i}_L(t)| \ll |I_L|$$

$$|\hat{d}(t)| \ll |D| \quad |\hat{v}_C(t)| \ll |V_C|$$

$$|\hat{i}_g(t)| \ll |I_g|$$

Perturb And Linearize

$$L \frac{d\langle i_L(t) \rangle}{dt} = d(t) \cdot \langle v_g t \rangle - \langle v_C(t) \rangle \quad \text{Averaged Differential Equation}$$

Substitute DC Plus Perturbation For Average Values:

$$L \frac{d(I_L + \hat{i}_L(t))}{dt} = (D + \hat{d}(t)) \cdot (V_g + \hat{v}_g(t)) - (V_C + \hat{v}_C(t))$$

Expand:

$$\begin{aligned} L \frac{dI_L}{dt} + L \frac{d\hat{i}_L(t)}{dt} &= D \cdot V_g + D \cdot \hat{v}_g(t) + V_g \cdot \hat{d}(t) + \hat{d}(t) \cdot \hat{v}_g(t) \\ &\quad - V_C - \hat{v}_C(t) \end{aligned}$$



Perturb And Linearize

Collect Terms:

$$L \frac{dI_L}{dt} + L \frac{d\hat{i}_L(t)}{dt} = D \cdot V_g - V_C$$

DC Terms Equal Zero

$$+ D \cdot \hat{v}_g(t) + V_g \cdot \hat{d}(t) - \hat{v}_C(t)$$

$$+ \hat{d}(t) \cdot \hat{v}_g(t)$$

Discard 2nd Order Terms

This Leaves A First Order Equation:

$$L \frac{d\hat{i}_L(t)}{dt} = +D \cdot \hat{v}_g(t) + V_g \cdot \hat{d}(t) - \hat{v}_C(t)$$



Perturb And Linearize

$$C \frac{d\langle v_c(t) \rangle}{dt} = \langle i_L(t) \rangle - \frac{1}{R} \cdot \langle v_c(t) \rangle \quad \text{Averaged Differential Equation}$$

Substitute DC Plus Perturbation For Average Values:

$$C \frac{d(V_c + \hat{v}_c(t))}{dt} = I_L + \hat{i}_L(t) - \frac{1}{R} \cdot (V_c + \hat{v}_c(t))$$

Expand:

DC Terms Equal Zero

$$C \frac{dV_c}{dt} + C \frac{d\hat{v}_c(t)}{dt} = I_L - \frac{1}{R} \cdot V_c + \hat{i}_L(t) - \frac{1}{R} \cdot \hat{v}_c(t)$$

$$C \frac{d\hat{v}_c(t)}{dt} = \hat{i}_L(t) - \frac{1}{R} \cdot \hat{v}_c(t)$$



Perturb And Linearize

$$\langle i_g(t) \rangle = d(t) \cdot \langle i_L(t) \rangle$$

$$\begin{aligned} I_g + \hat{i}_g(t) &= (D + \hat{d}(t)) \cdot (I_L + \hat{i}_L(t)) \\ &= D \cdot I_L + D \cdot \hat{i}_L(t) + I_L \cdot \hat{d}(t) + \hat{d}(t) \cdot \hat{i}_L(t) \end{aligned}$$


$$\hat{i}_g(t) = D \cdot \hat{i}_L(t) + I_L \cdot \hat{d}(t) + \cancel{\hat{d}(t) \cdot \hat{i}_L(t)}$$

$$\hat{i}_g(t) = D \cdot \hat{i}_L(t) + I_L \cdot \hat{d}(t)$$




Construct The Model
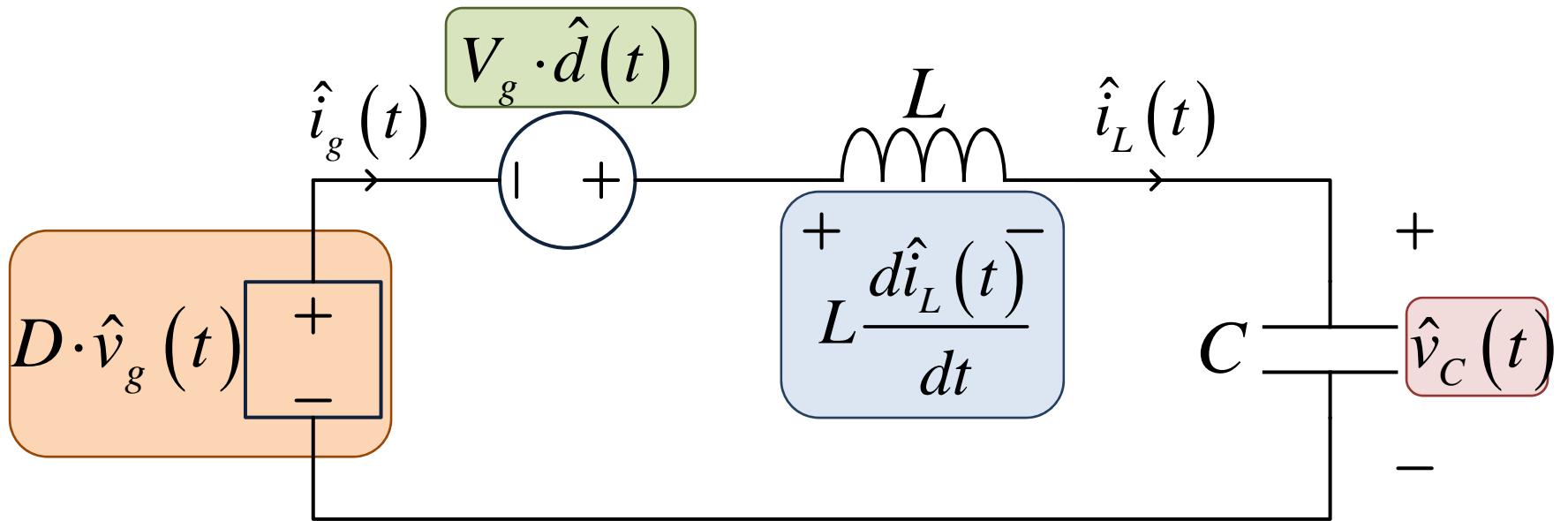
$$L \frac{d\hat{i}_L(t)}{dt} = +D \cdot \hat{v}_g(t) + V_g \cdot \hat{d}(t) - \hat{v}_C(t)$$




Construct The Model
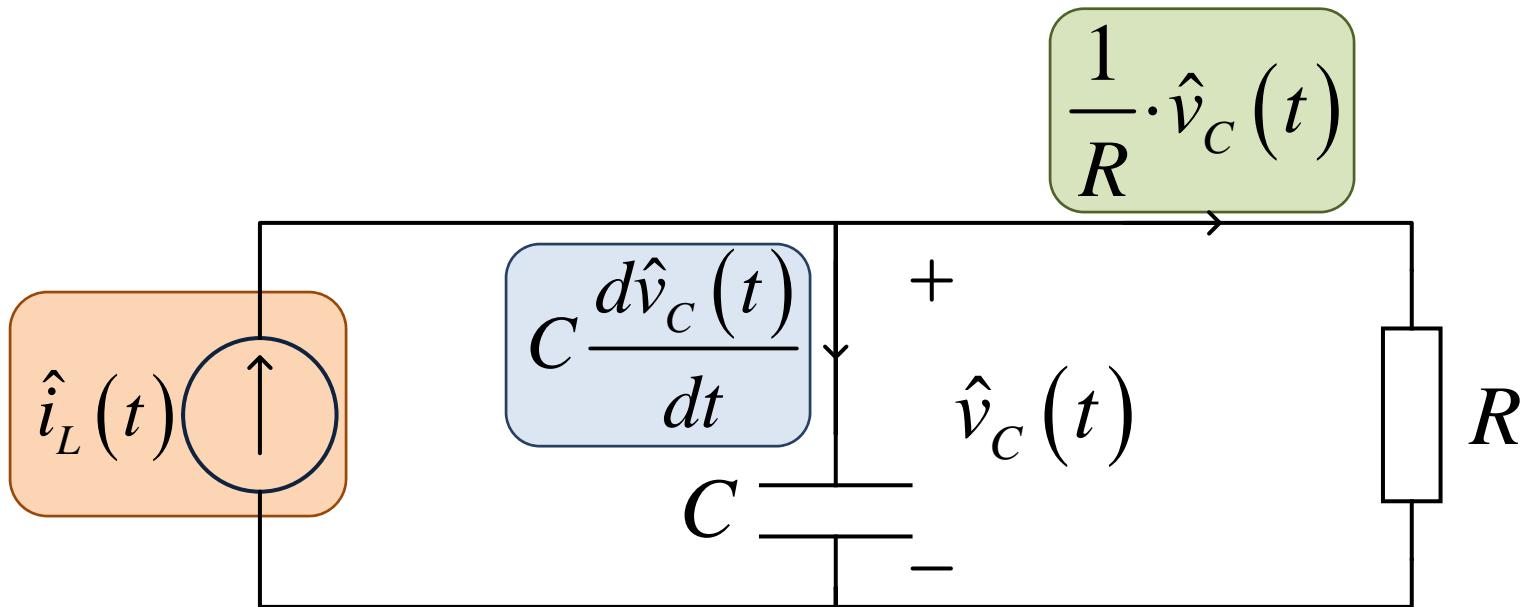
$$C \frac{d\hat{v}_C(t)}{dt} = \hat{i}_L(t) - \frac{1}{R} \cdot \hat{v}_C(t)$$





Construct The Model
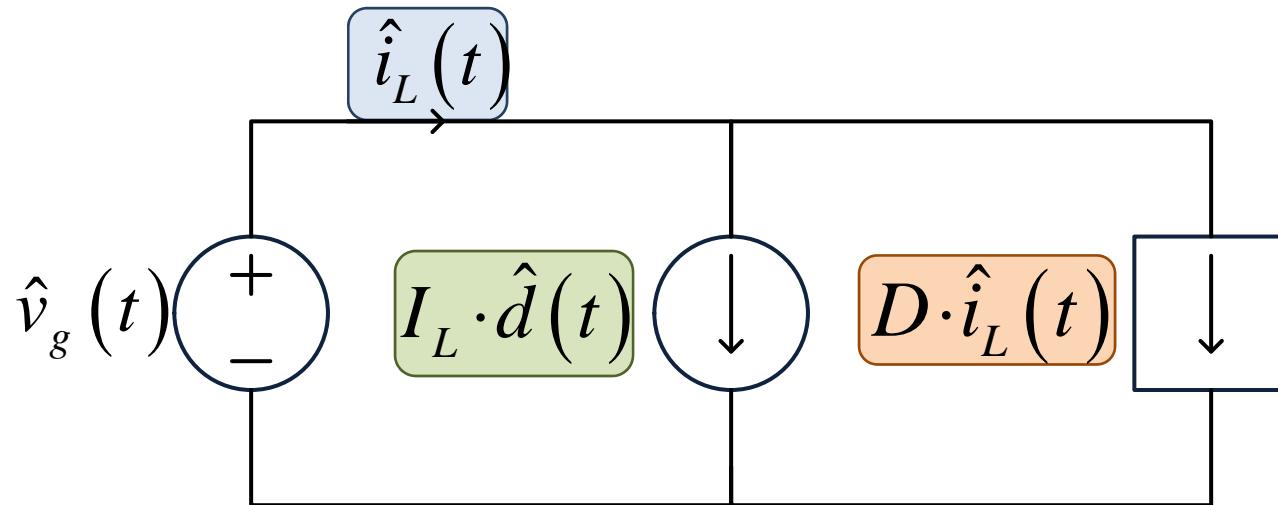
$$\hat{i}_g(t) = D \cdot \hat{i}_L(t) + I_L \cdot \hat{d}(t)$$




Construct The Model

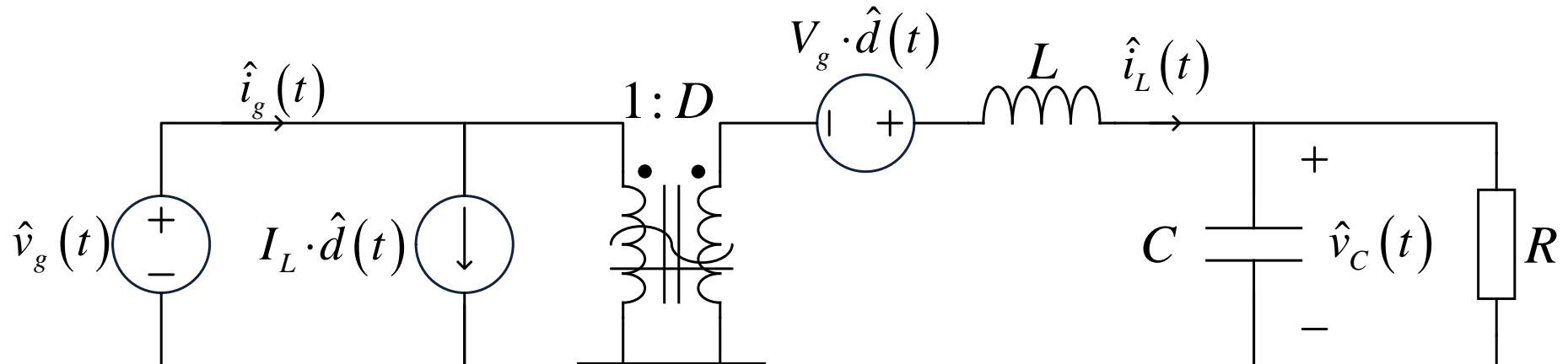
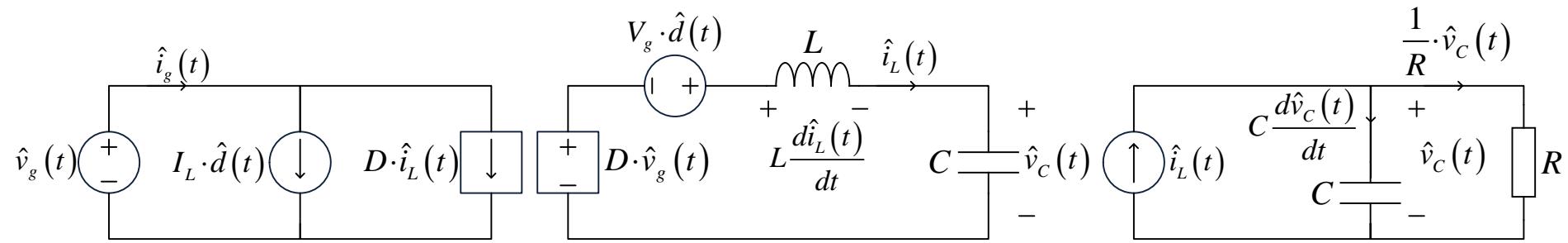


Control-To-Output Transfer Function

$$G_{vd}(s) = \left. \frac{\hat{v}_c(s)}{\hat{d}(s)} \right|_{\hat{v}_g=0}$$

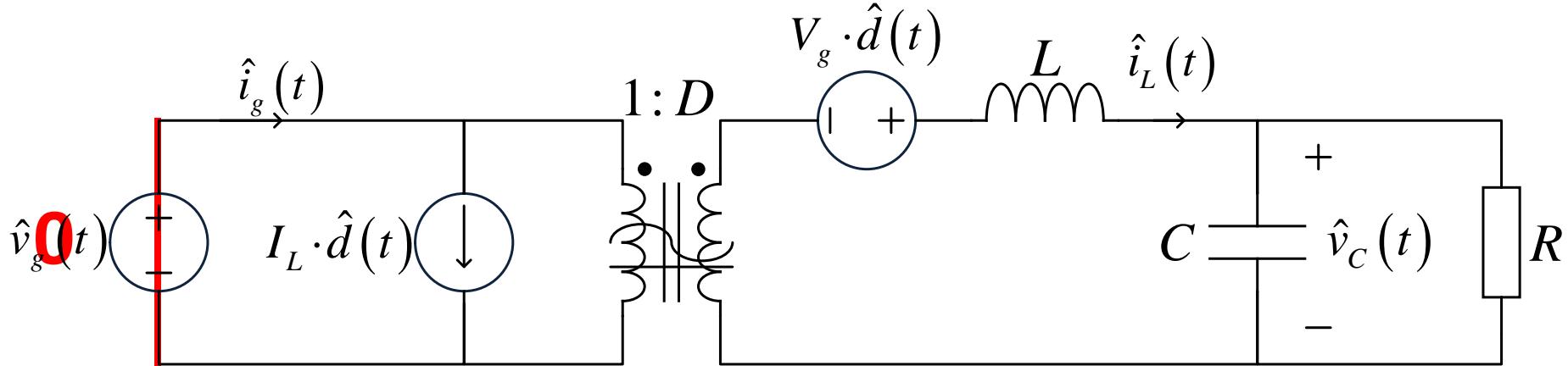


Control-To-Output Transfer Function

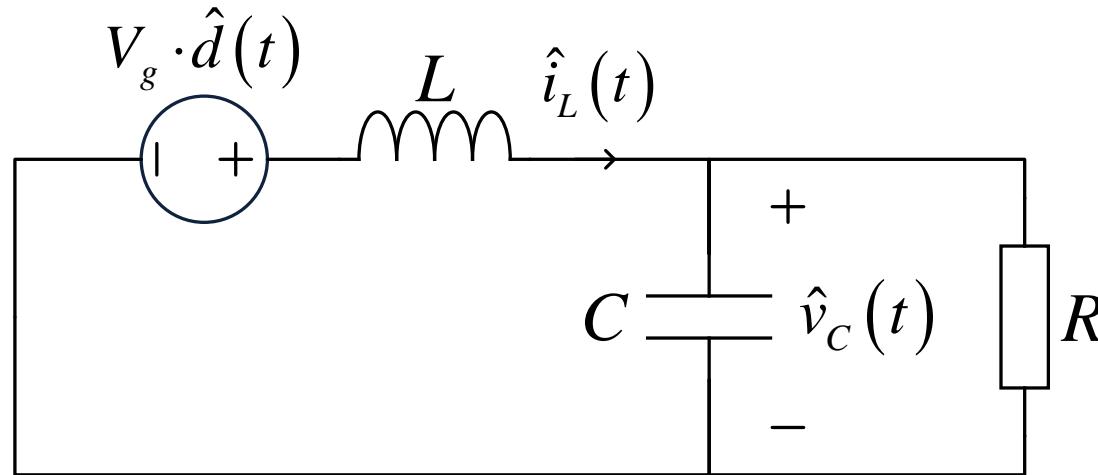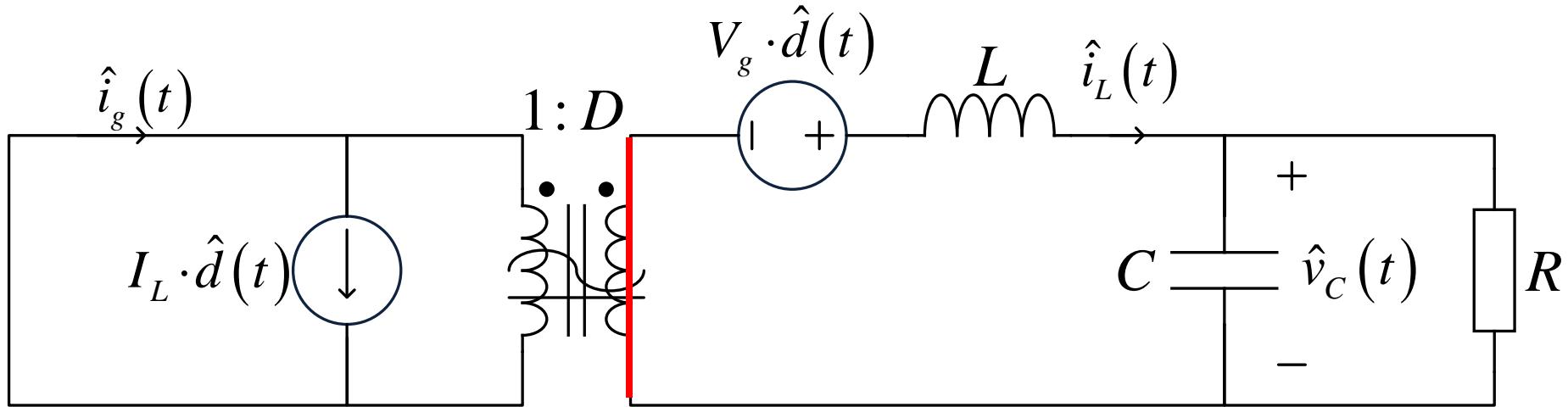

Control-To-Output Transfer Function
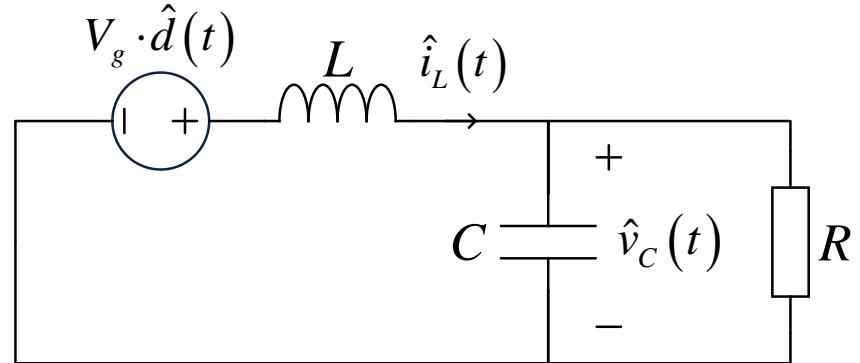
$$\hat{v}_c(s) = \frac{R \parallel \frac{1}{s \cdot C}}{s \cdot L + R \parallel \frac{1}{s \cdot C}} \cdot V_g \cdot \hat{d}(s)$$




$$G_{vd}(s) = \frac{\hat{v}_c(s)}{\hat{d}(s)} = \frac{1}{1 + \frac{L}{R} \cdot s + L \cdot C \cdot s^2} \cdot V_g = \frac{1}{1 + \frac{1}{Q} \cdot \frac{s}{\omega_0} + \left(\frac{s}{\omega_0}\right)^2} \cdot V_g$$

$$\omega_0^2 = \frac{1}{L \cdot C} \quad Q = R \cdot \sqrt{\frac{C}{L}} = \frac{1}{2 \cdot \zeta}$$



Input To Output Transfer Function

$$G_{vg}(s) = \left. \frac{\hat{v}_c(s)}{\hat{v}_g(s)} \right|_{\hat{d}=0}$$

“Audiosusceptibility”

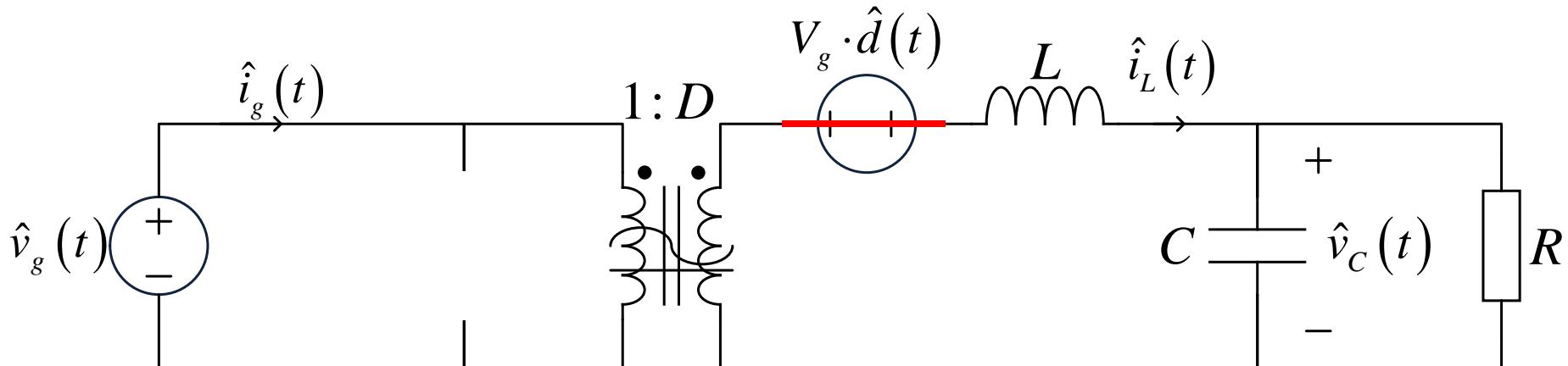


Input To Output Transfer Function

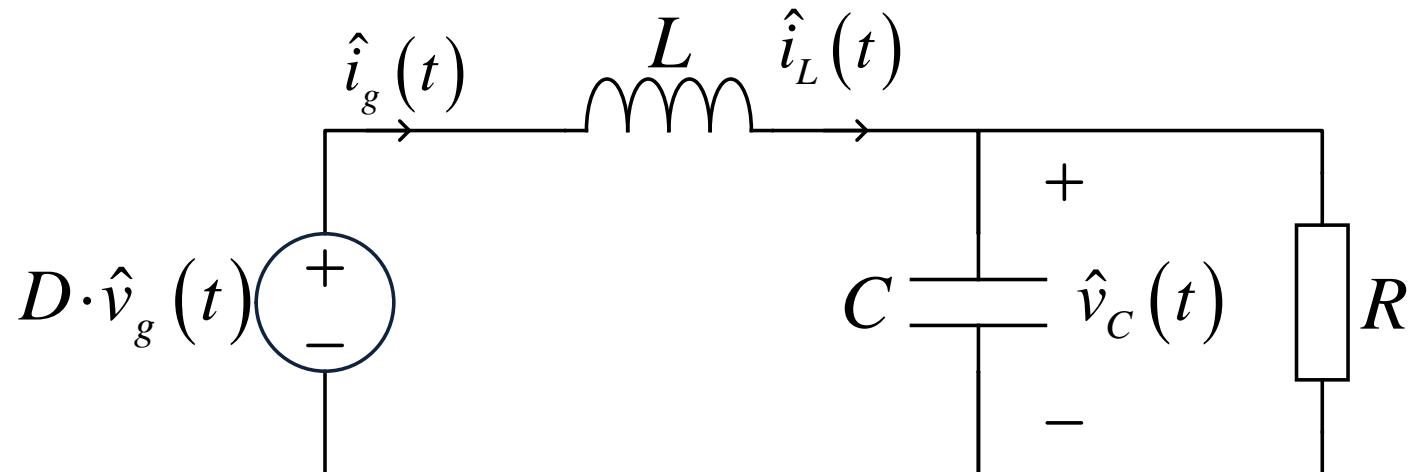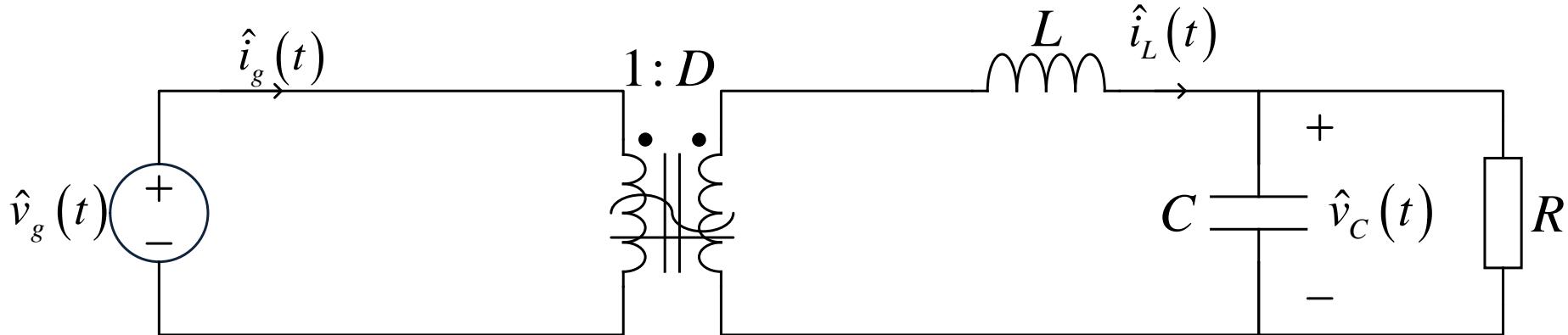

Input To Output Transfer Function

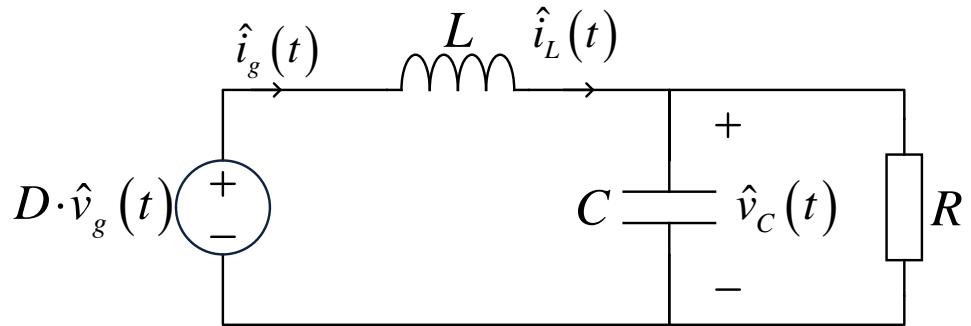
$$\hat{v}_c(s) = \frac{R \parallel \frac{1}{s \cdot C}}{s \cdot L + R \parallel \frac{1}{s \cdot C}} \cdot D \cdot \hat{v}_g$$





$$G_{vd}(s) = \frac{\hat{v}_c(s)}{\hat{v}_g} = \frac{D}{1 + \frac{L}{R} \cdot s + L \cdot C \cdot s^2} = \frac{D}{1 + \frac{1}{Q} \cdot \frac{s}{\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$

Input Impedance

$$Z_i(s) = \left. \frac{\hat{v}_g(s)}{\hat{i}_g(s)} \right|_{\hat{d}=0}$$

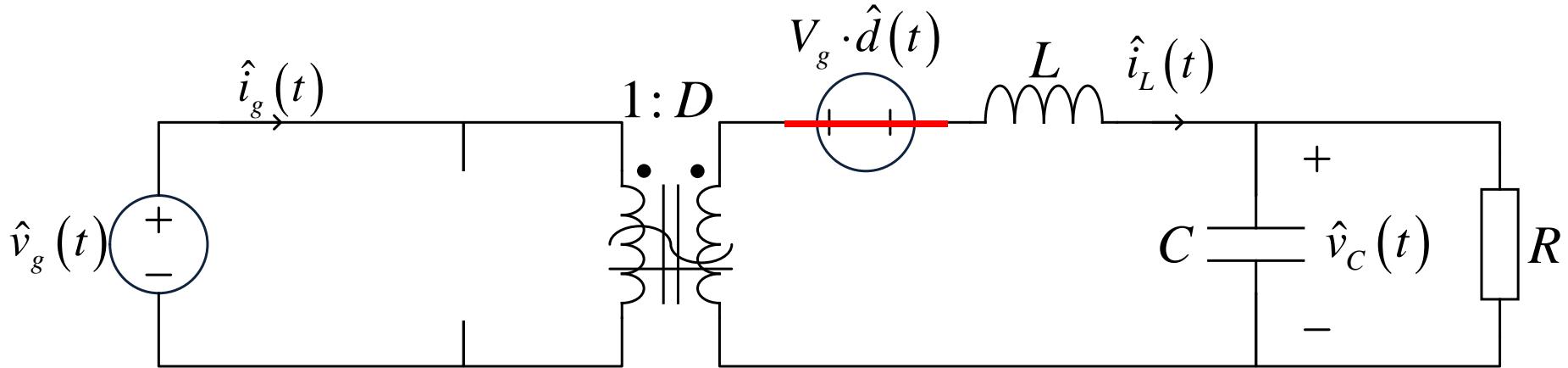


Input Impedance

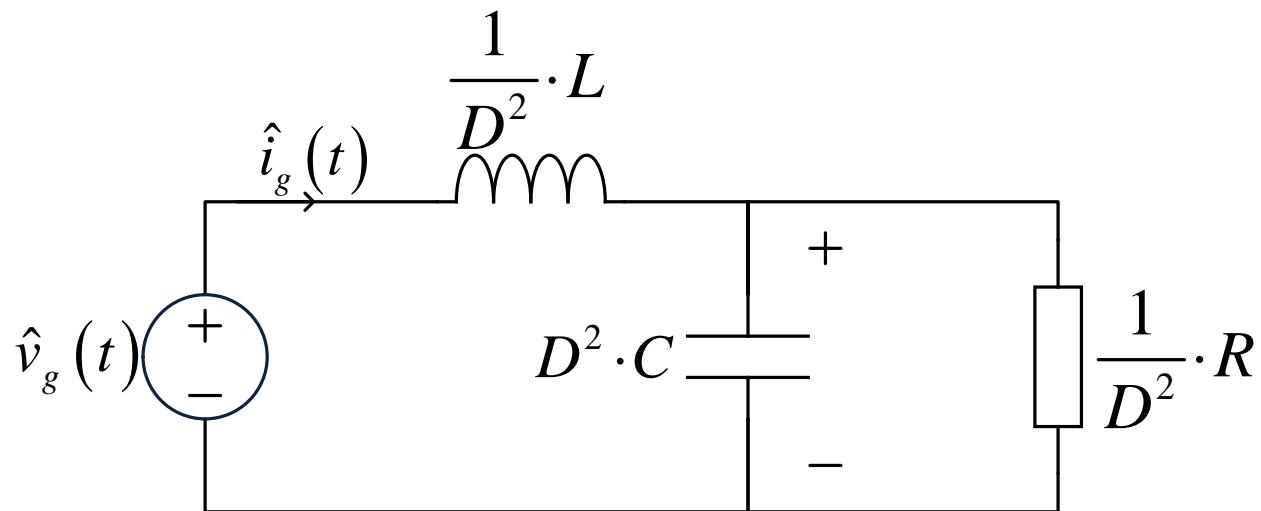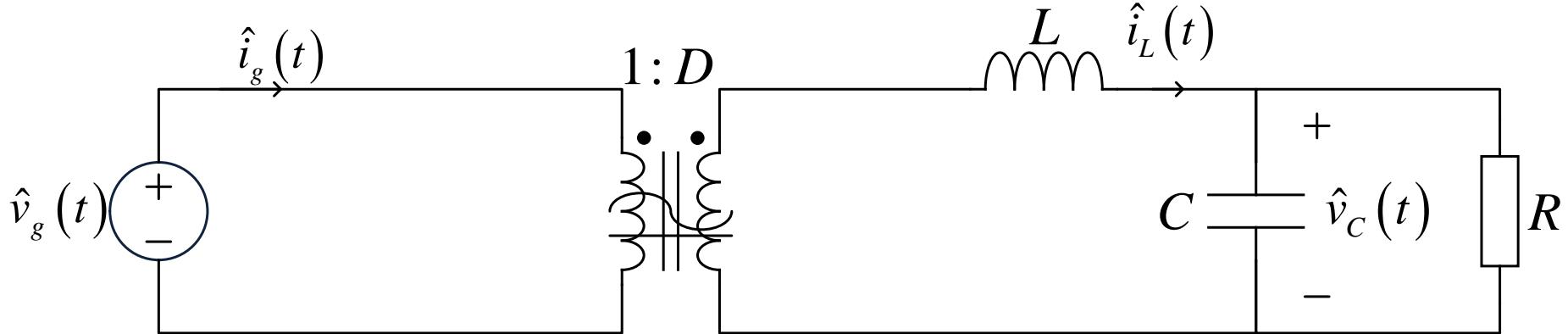

Input Impedance
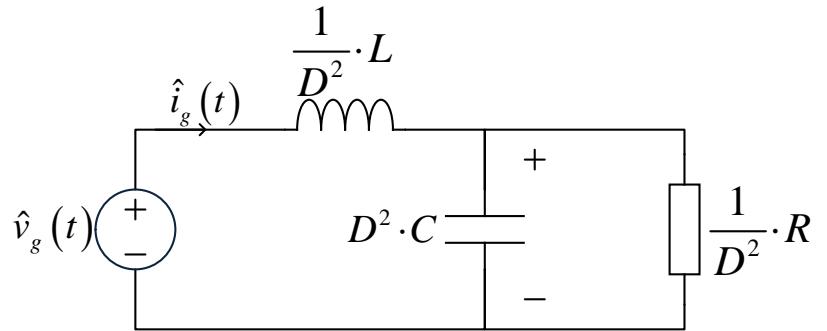
$$\hat{i}_g(s) = \frac{\hat{v}_g(s)}{s \cdot \frac{L}{D^2} + \frac{R}{D^2} \parallel \frac{1}{s \cdot D^2 \cdot C}}$$





$$Z_i(s) = \frac{\hat{v}_g(s)}{\hat{i}_g(s)} = s \cdot \frac{L}{D^2} + \frac{R}{D^2} \parallel \frac{1}{s \cdot D^2 \cdot C}$$

$$Z_i(s) = \frac{R}{D^2} \cdot \frac{1 + s \cdot \frac{L}{R} + s^2 \cdot L \cdot C}{1 + s \cdot R \cdot C} = \frac{R}{D^2} \cdot \frac{1 + \frac{1}{Q} \cdot \frac{s}{\omega_0} + \left(\frac{s}{\omega_0} \right)^2}{1 + s \cdot R \cdot C}$$




Boost And Buck-Boost Models

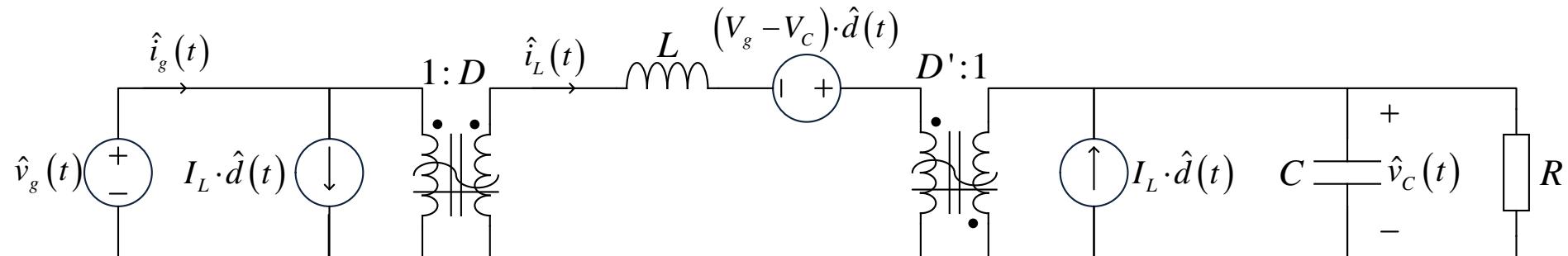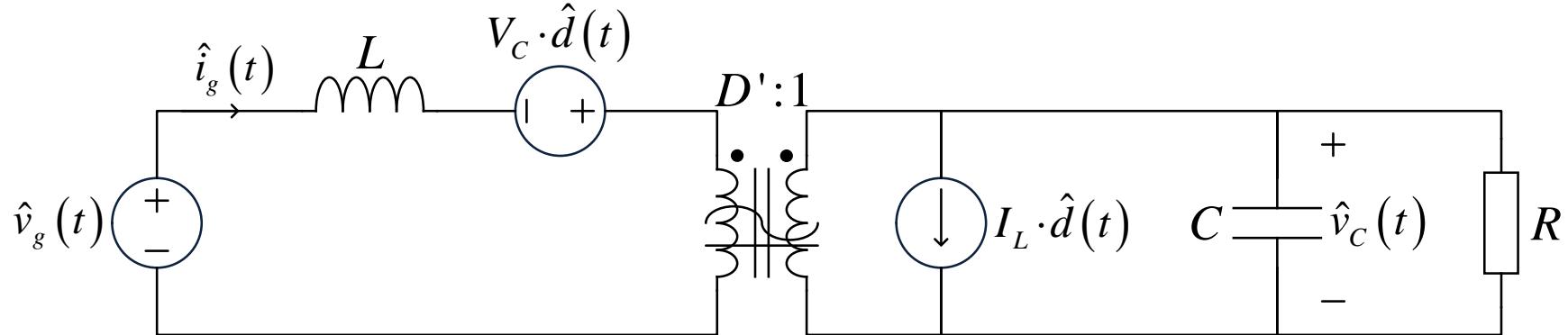


Re-drawn from "Fundamentals of Power Electronics", 2nd ed.,
Erickson and Maksimovic, Figure 7.17


Flyback Example

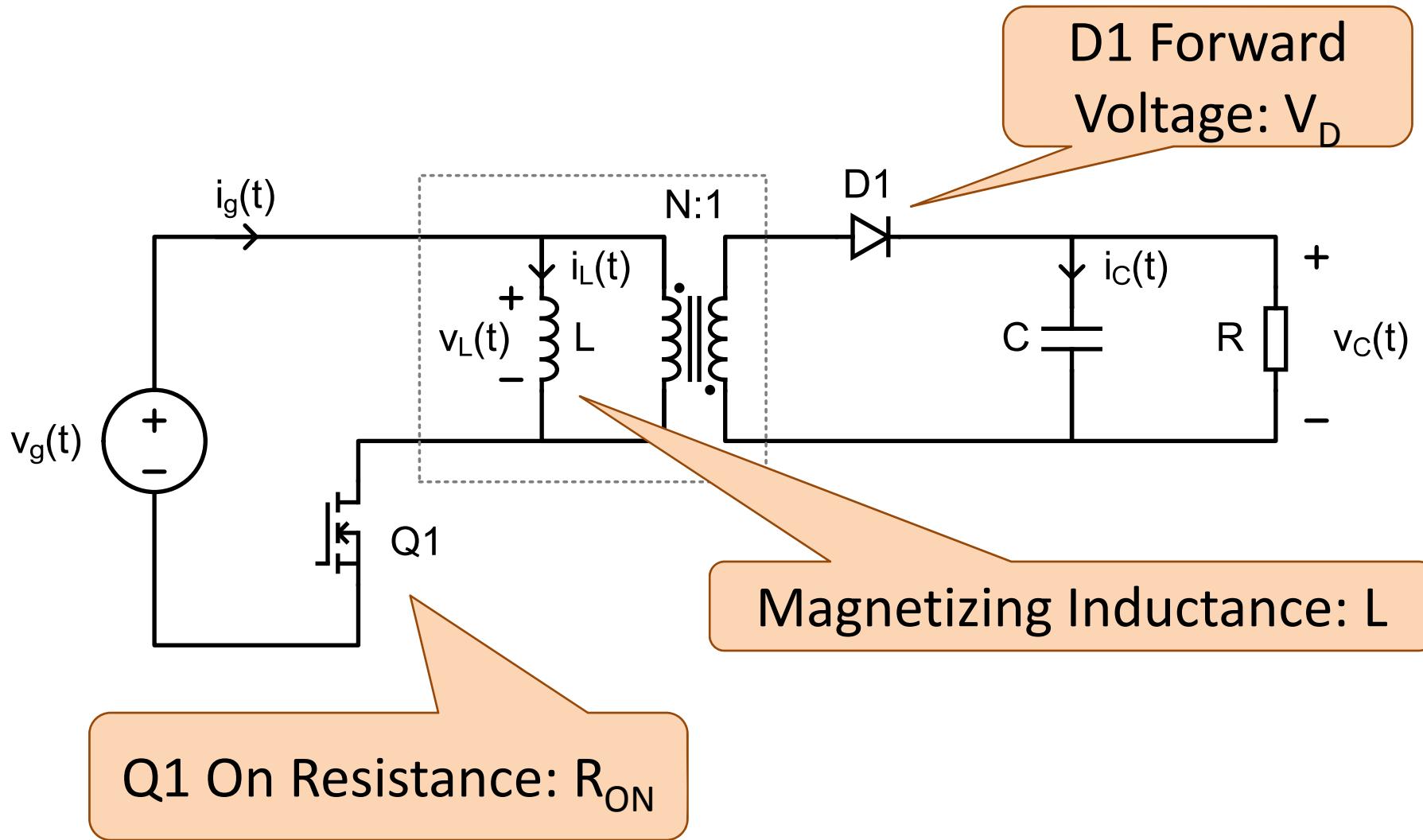


On-Time Circuit

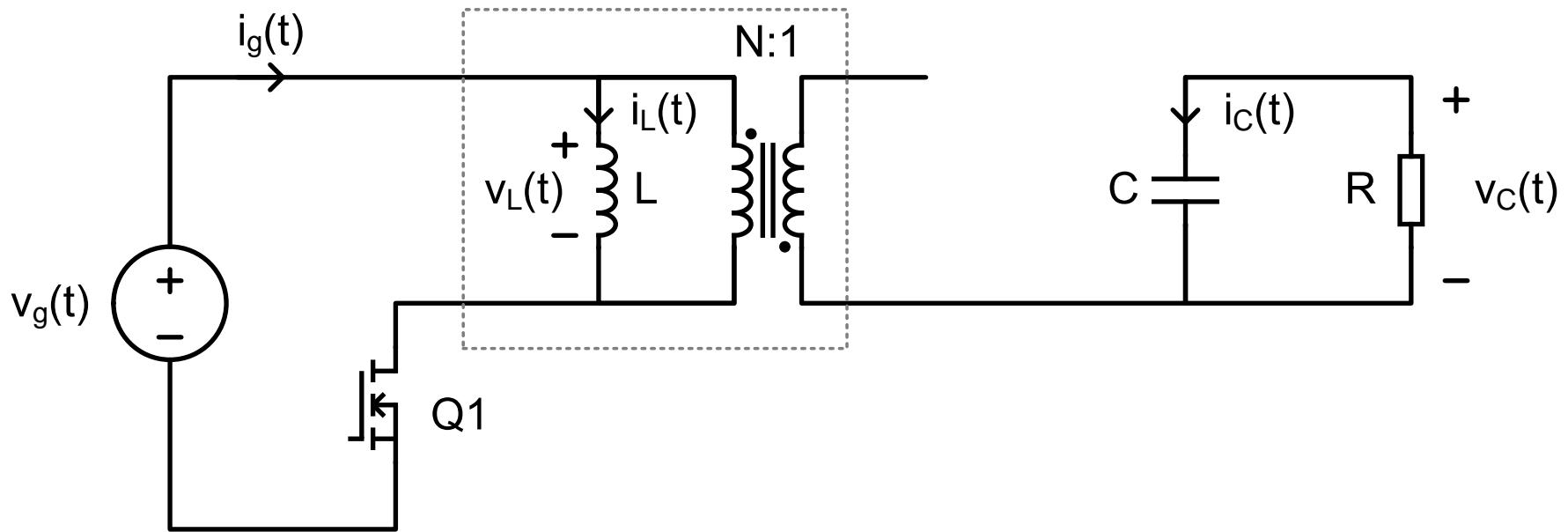


Off Time Circuit

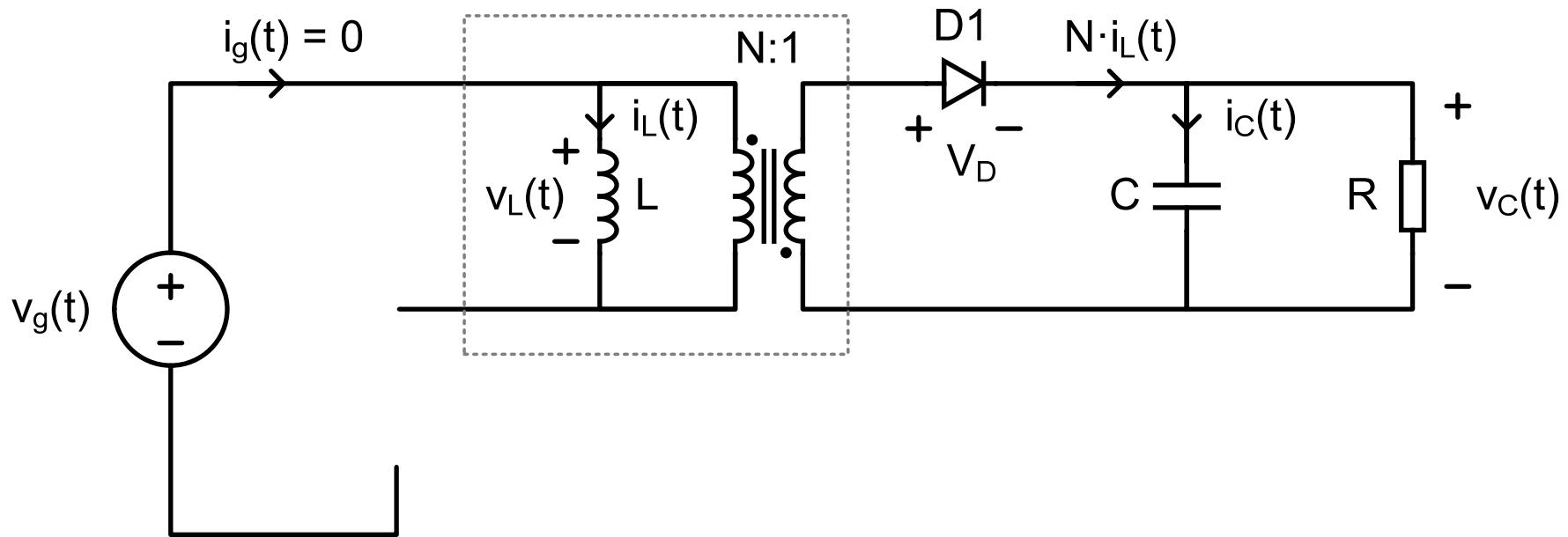

Sketching The Inductor Waveforms

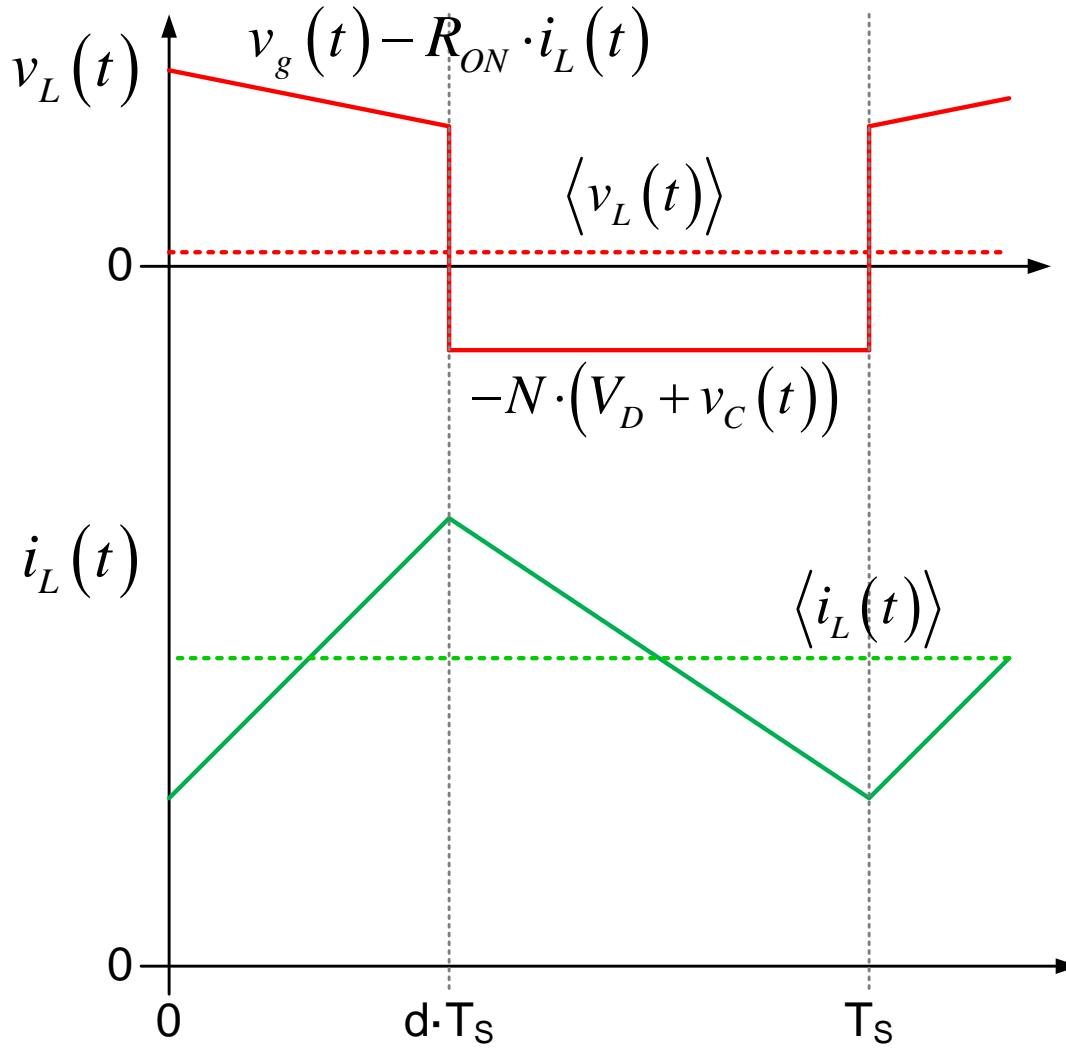

Sketching The Capacitor Waveforms

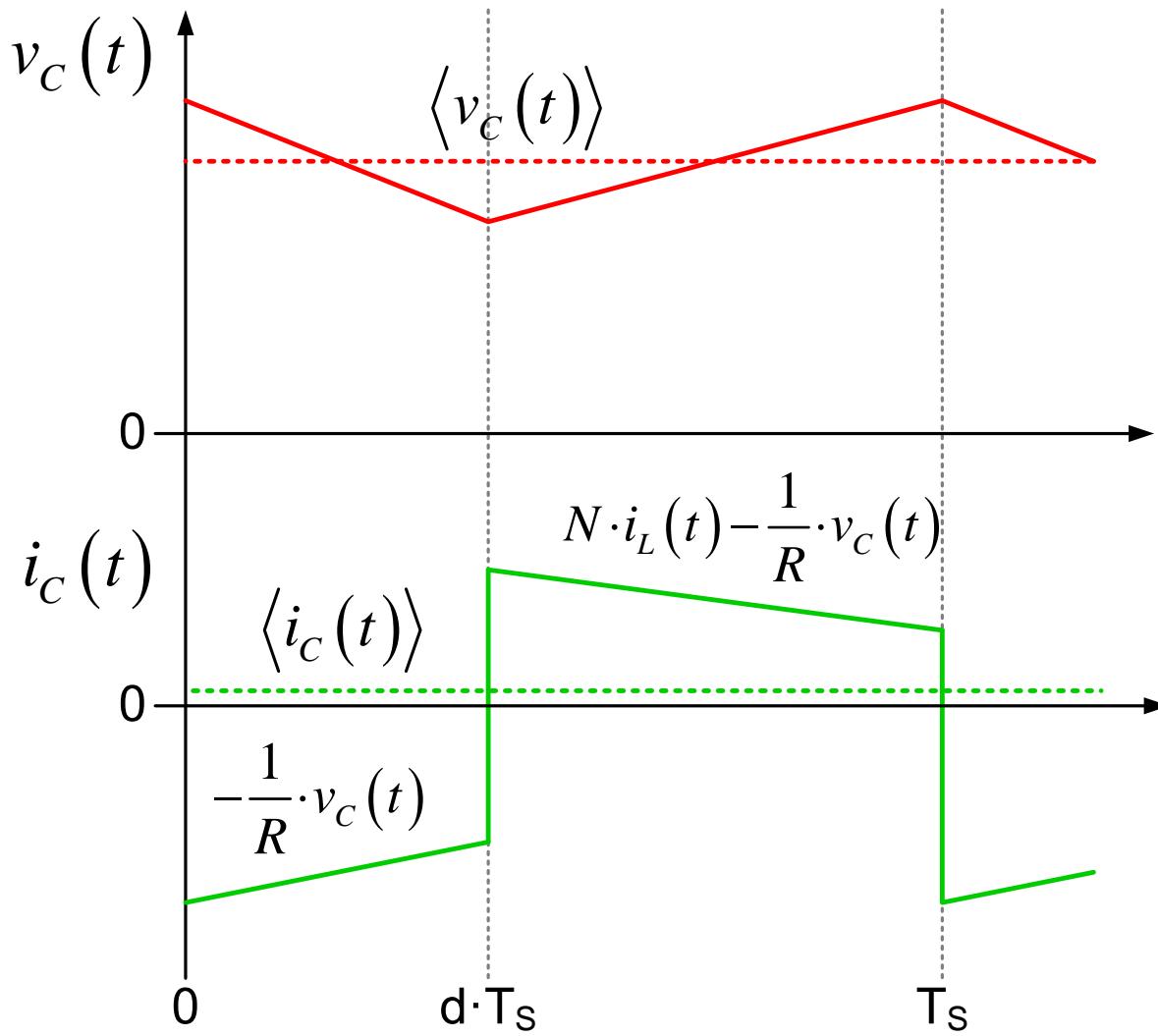

Averaging The Circuit Equations

On Time

$$v_L(t) = v_g(t) - R_{ON} \cdot i_L(t)$$

$$i_C(t) = -\frac{1}{R} \cdot v_C(t)$$

$$i_g(t) = i_L(t)$$

$$v_L(t) = \langle v_g(t) \rangle - R_{ON} \cdot \langle i_L(t) \rangle$$

$$i_C(t) = -\frac{1}{R} \cdot \langle v_C(t) \rangle$$

$$i_g(t) = \langle i_L(t) \rangle$$

Off Time

$$v_L(t) = -N \cdot (V_D + v_c(t))$$

$$i_C(t) = N \cdot i_L(t) - \frac{1}{R} \cdot v_C(t)$$

$$i_g(t) = 0$$

$$v_L(t) = -N \cdot (V_D + \langle v_c(t) \rangle)$$

$$i_C(t) = N \cdot \langle i_L(t) \rangle - \frac{1}{R} \cdot \langle v_C(t) \rangle$$

$$i_g(t) = 0$$



Averaging The Inductor Voltage

$$\begin{aligned}\langle v_L(t) \rangle &= d(t) \cdot \left(\langle v_g(t) \rangle - R_{ON} \cdot \langle i_L(t) \rangle \right) \\ &\quad + d'(t) \cdot \left(-N \cdot \left(V_D + \langle v_c(t) \rangle \right) \right) \\ &= d(t) \cdot \langle v_g(t) \rangle - d(t) \cdot R_{ON} \cdot \langle i_L(t) \rangle \\ &\quad - d'(t) \cdot N \cdot \langle v_c(t) \rangle - d'(t) \cdot N \cdot V_D\end{aligned}$$

$$\begin{aligned}L \cdot \frac{d \langle i_L(t) \rangle}{dt} &= \langle v_L(t) \rangle \\ &= d(t) \cdot \langle v_g(t) \rangle - d(t) \cdot R_{ON} \cdot \langle i_L(t) \rangle \\ &\quad - d'(t) \cdot N \cdot \langle v_c(t) \rangle - d'(t) \cdot N \cdot V_D\end{aligned}$$



Averaging The Capacitor Current

$$\begin{aligned}\langle i_C(t) \rangle &= d(t) \cdot \left(-\frac{1}{R} \cdot \langle v_C(t) \rangle \right) \\ &\quad + d'(t) \cdot \left(N \cdot \langle i_L(t) \rangle - \frac{1}{R} \cdot \langle v_C(t) \rangle \right) \\ &= d'(t) \cdot N \cdot \langle i_L(t) \rangle - \frac{1}{R} \cdot \langle v_C(t) \rangle\end{aligned}$$

$$\begin{aligned}C \cdot \frac{d \langle v_c(t) \rangle}{dt} &= \langle i_C(t) \rangle \\ &= d'(t) \cdot N \cdot \langle i_L(t) \rangle - \frac{1}{R} \cdot \langle v_C(t) \rangle\end{aligned}$$



Averaging The Input Current/ Perturbation

$$\begin{aligned}\langle i_g(t) \rangle &= d(t) \cdot \langle i_L(t) \rangle + d'(t) \cdot 0 \\ &= d(t) \cdot \langle i_L(t) \rangle\end{aligned}$$

Perturbing The Inputs

$$d(t) = D + \hat{d}(t)$$

$$d'(t) = 1 - d(t) = 1 - D - \hat{d}(t)$$

$$\langle V_g(t) \rangle = V_g + \hat{v}_g(t)$$

Perturbed Circuit Variables

$$\langle i_L(t) \rangle = I_L + \hat{i}_L(t)$$

$$\langle v_C(t) \rangle = V_C + \hat{v}_C(t)$$

$$\langle i_g(t) \rangle = I_g + \hat{i}_g(t)$$

Substitute Expressions Into Averaged Differential Equations

Averaging The Inductor Voltage

$$\begin{aligned} L \cdot \frac{d \langle i_L(t) \rangle}{dt} &= \langle v_L(t) \rangle \\ &= d(t) \cdot \langle v_g(t) \rangle - d(t) \cdot R_{ON} \cdot \langle i_L(t) \rangle \\ &\quad - d'(t) \cdot N \cdot \langle v_c(t) \rangle - d'(t) \cdot N \cdot V_D \end{aligned}$$

$$\begin{aligned} L \cdot \frac{d(I_L + \hat{i}_L(t))}{dt} &= (D + \hat{d}(t)) \cdot (V_g + \hat{v}_g(t)) - (D + \hat{d}(t)) \cdot R_{ON} \cdot (I_L + \hat{i}_L(t)) \\ &\quad - (1 - D - \hat{d}(t)) \cdot N \cdot (V_C + \hat{v}_C(t)) - (1 - D - \hat{d}(t)) \cdot N \cdot V_D \end{aligned}$$



Averaging The Inductor Voltage

$$L \cdot \frac{d(I_L)}{dt} + L \cdot \frac{d(\hat{i}_L(t))}{dt} = D \cdot V_g + D \cdot \hat{v}_g(t) + V_g \cdot \hat{d}(t) + \hat{d}(t) \cdot \hat{v}_g(t)$$

$$-D \cdot R_{ON} \cdot I_L - D \cdot R_{ON} \cdot \hat{i}_L(t) - R_{ON} v I_L \cdot \hat{d}(t) - R_{ON} \cdot \hat{d}(t) \cdot \hat{i}_L(t)$$

$$-N \cdot V_C - N \cdot \hat{v}_C(t) + D \cdot N \cdot V_C + D \cdot N \cdot \hat{v}_C(t) + N \cdot V_C \cdot \hat{d}(t) + N \cdot \hat{v}_C(t) \cdot \hat{d}(t)$$

$$-N \cdot V_D + D \cdot N \cdot V_D + N \cdot V_D \cdot \hat{d}(t)$$

Averaging The Inductor Voltage

$$\begin{aligned}
 L \cdot \frac{d(I_L)}{dt} + L \cdot \frac{d(\hat{i}_L(t))}{dt} = & D \cdot V_g - D \cdot R_{ON} \cdot I_L - N \cdot V_C + D \cdot N \cdot V_C - N \cdot V_D + D \cdot N \cdot V_D \\
 & + D \cdot \hat{v}_g(t) \\
 & + V_g \cdot \hat{d}(t) - R_{ON} \cdot I_L \cdot \hat{d}(t) + N \cdot V_C \cdot \hat{d}(t) + N \cdot V_D \cdot \hat{d}(t) \\
 & - D \cdot R_{ON} \cdot \hat{i}_L(t) \\
 & - N \cdot \hat{v}_C(t) + D \cdot N \cdot \hat{v}_C(t) \\
 & + \hat{d}(t) \cdot \hat{v}_g(t) - R_{ON} \cdot \hat{d}(t) \cdot \hat{i}_L(t) + N \cdot \hat{v}_C(t) \cdot \hat{d}(t)
 \end{aligned}$$

Averaging The Inductor Voltage

$$L \cdot \frac{d(I_L)}{dt} = 0$$

$$= D \cdot V_g - D \cdot R_{ON} \cdot I_L - N \cdot V_C + D \cdot N \cdot V_C - N \cdot V_D + D \cdot N \cdot V_D$$

$$= D \cdot (V_g - R_{ON} \cdot I_L) - (1 - D) \cdot N \cdot V_C - (1 - D) \cdot N \cdot V_D$$

$$D' \cdot N \cdot V_C = D \cdot (V_g - R_{ON} \cdot I_L) - D' \cdot N \cdot V_D$$

$$V_C = \frac{D}{D'} \cdot \frac{1}{N} \cdot (V_g - R_{ON} \cdot I_L) - V_D$$


Get The Same Result By Inductor
Volt-Second Balance Calculation

Averaging The Inductor Voltage

$$\begin{aligned} L \frac{d\langle i_L(t) \rangle}{dt} &= D \cdot \hat{v}_g(t) \\ &+ V_g \cdot \hat{d}(t) - R_{ON} \cdot I_L \cdot \hat{d}(t) + N \cdot V_C \cdot \hat{d}(t) + N \cdot V_D \cdot \hat{d}(t) \\ &- D \cdot R_{ON} \cdot \hat{i}_L(t) \\ &- N \cdot \hat{v}_C(t) + D \cdot N \cdot \hat{v}_C(t) \\ &= D \cdot \hat{v}_g(t) \\ &+ (V_g - R_{ON} \cdot I_L + N \cdot (V_C + V_D)) \cdot \hat{d}(t) \\ &- D \cdot R_{ON} \cdot \hat{i}_L(t) \\ &- (1 - D) \cdot N \cdot \hat{v}_C(t) \end{aligned}$$

Construct The Model
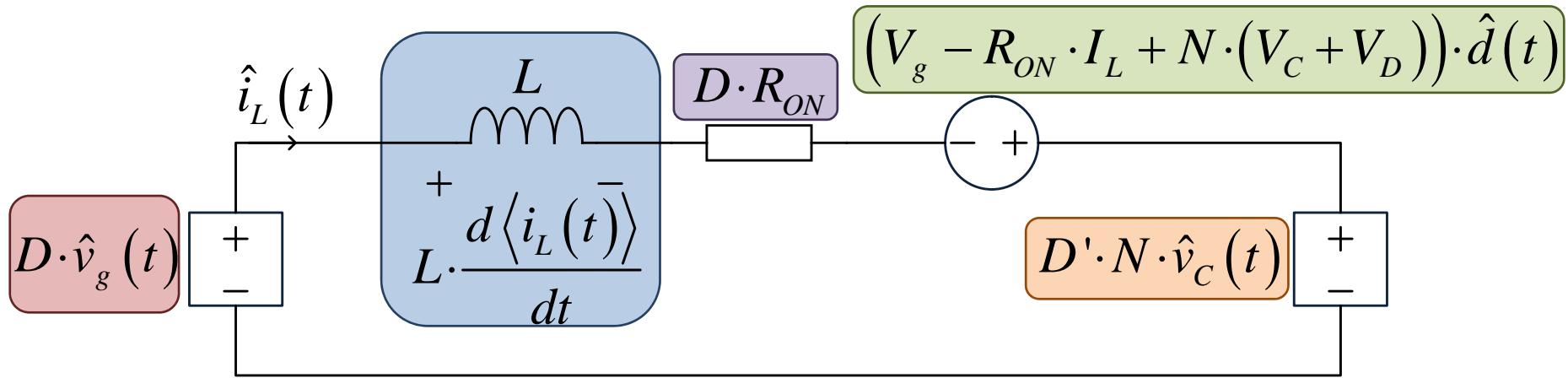
$$L \cdot \frac{d\langle i_L(t) \rangle}{dt} = D \cdot \hat{v}_g(t) + \left(V_g - R_{ON} \cdot I_L + N \cdot (V_C + V_D) \right) \cdot \hat{d}(t)$$
$$- D \cdot R_{ON} \cdot \hat{i}_L(t) - D' \cdot N \cdot \hat{v}_C(t)$$



Averaging The Capacitor Current

$$C \frac{d\langle v_c(t) \rangle}{dt} = d'(t) \cdot N \cdot \langle i_L(t) \rangle - \frac{1}{R} \cdot \langle v_C(t) \rangle$$

$$C \frac{d(V_C + \hat{v}_C(t))}{dt} = (1 - D - \hat{d}(t)) \cdot N \cdot (I_L + \hat{i}_L(t)) - \frac{1}{R} \cdot (V_C + \hat{v}_C(t))$$

$$C \frac{d(V_C)}{dt} + C \frac{d(\hat{v}_C(t))}{dt} = N \cdot I_L + N \cdot \hat{i}_L(t) - D \cdot N \cdot I_L - D \cdot N \cdot \hat{i}_L(t)$$

$$-N \cdot I_L \cdot \hat{d}(t) - \cancel{N \cdot \hat{i}_L(t) \cdot \hat{d}(t)}$$

$$-\frac{1}{R} \cdot V_C - \frac{1}{R} \cdot \hat{v}_C(t)$$

!

Averaging The Capacitor Current

$$C \frac{d(V_C)}{dt} + C \frac{d(\hat{v}_C(t))}{dt} = N \cdot I_L - D \cdot N \cdot I_L - \frac{1}{R} \cdot V_C$$

$$+ N \cdot \hat{i}_L(t) - D \cdot N \cdot \hat{i}_L(t)$$

$$- N \cdot I_L \cdot \hat{d}(t)$$

$$- \frac{1}{R} \cdot \hat{v}_C(t)$$

$$C \frac{d(\hat{v}_C(t))}{dt} = D' \cdot N \cdot \hat{i}_L(t) - N \cdot I_L \cdot \hat{d}(t) - \frac{1}{R} \cdot \hat{v}_C(t)$$



Averaging The Capacitor Current

$$C \frac{d(V_C)}{dt} = D' \cdot N \cdot I_L - \frac{1}{R} \cdot V = 0$$

$$D' \cdot N \cdot I_L = \frac{1}{R} \cdot V_C$$


$$I_L = \frac{1}{D'} \cdot \frac{1}{N \cdot R} \cdot V_C$$



Get The Same Result By Capacitor Charge Balance Calculation

Constructing The Model
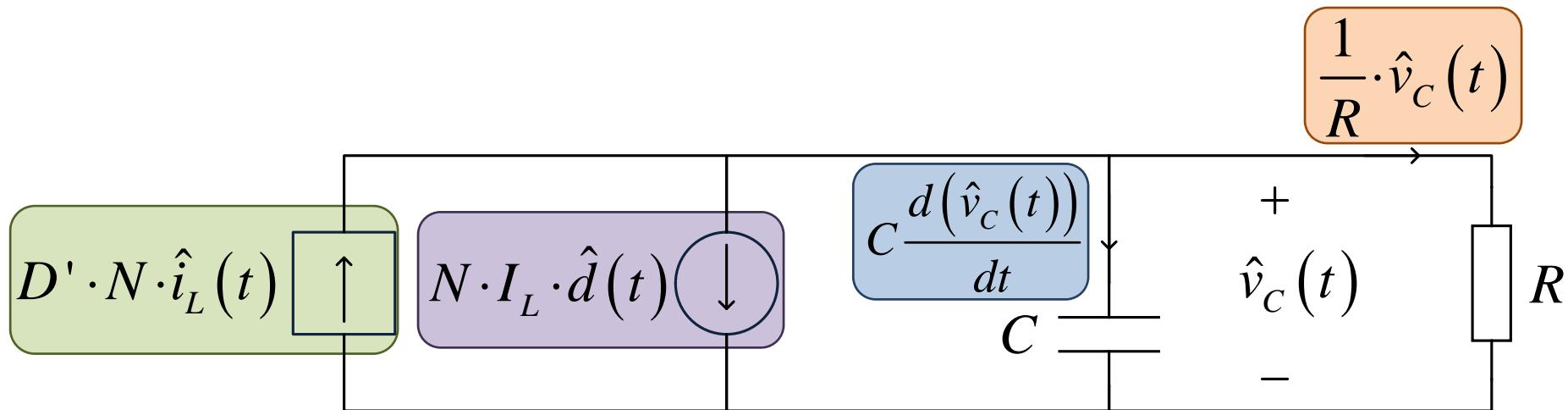
$$C \frac{d(\hat{v}_c(t))}{dt} = D' \cdot N \cdot \hat{i}_L(t) - N \cdot I_L \cdot \hat{d}(t) - \frac{1}{R} \cdot \hat{v}_c(t)$$



Averaging The Input Current

$$\langle i_g(t) \rangle = d(t) \cdot \langle i_L(t) \rangle$$

$$\begin{aligned} I_g + \hat{i}_g(t) &= (D + \hat{d}(t)) \cdot (I_L + \hat{i}_L(t)) \\ &= D \cdot I_L + D \cdot \hat{i}_L(t) + I_L \cdot \hat{d}(t) + \hat{d}(t) \cdot \hat{i}_L(t) \end{aligned}$$


$$I_g = D \cdot I_L$$

$$\hat{i}_g(t) = D \cdot \hat{i}_L(t) + I_L \cdot \hat{d}(t)$$





Constructing The Model


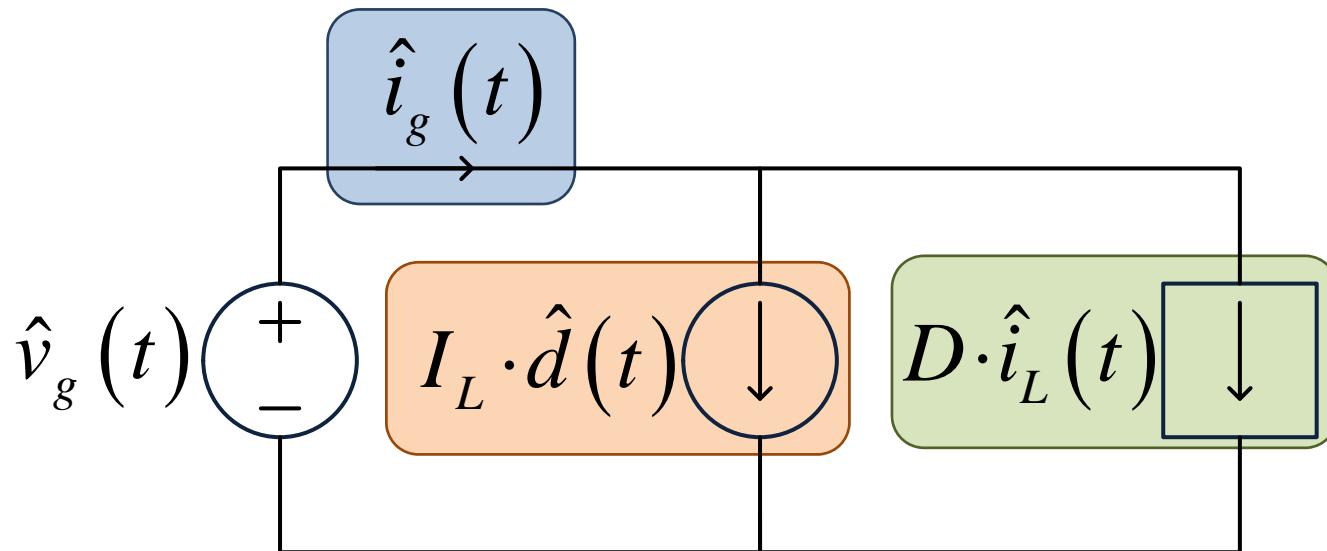
$$\hat{i}_g(t) = D \cdot \hat{i}_L(t) + I_L \cdot \hat{d}(t)$$




Completing The Flyback Model

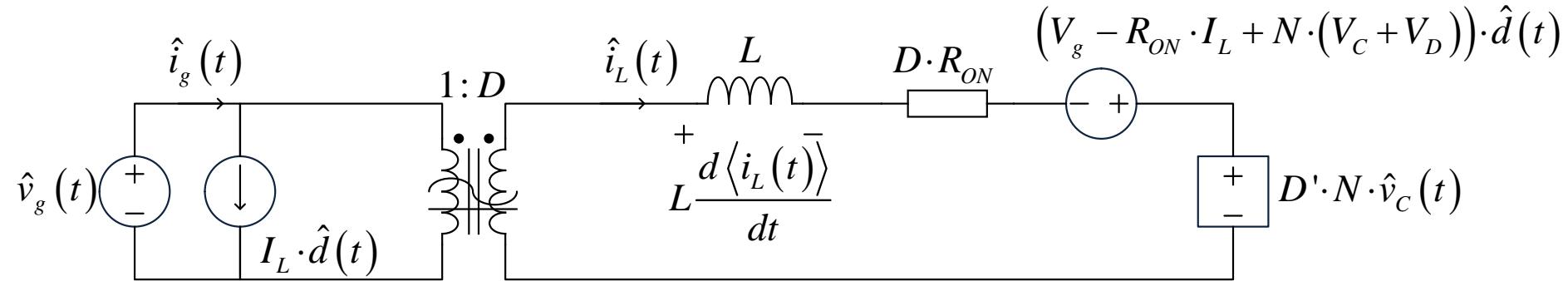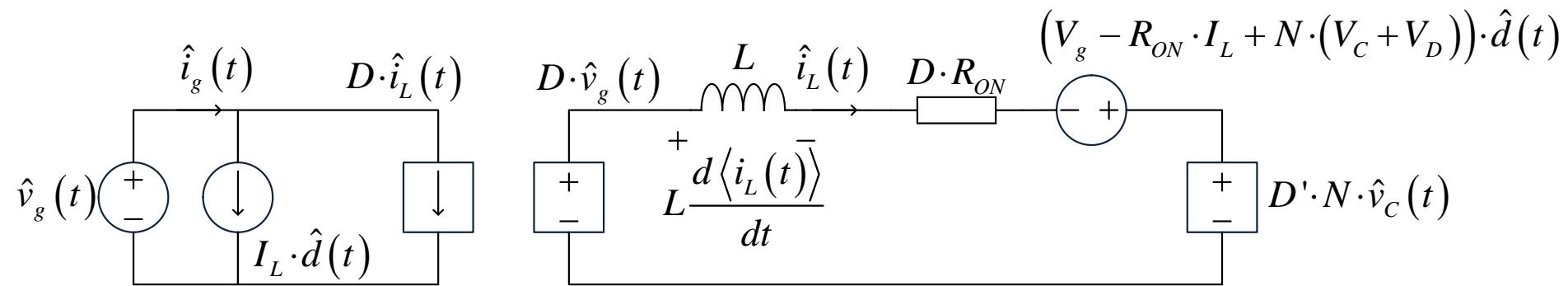


Completing The Flyback Model

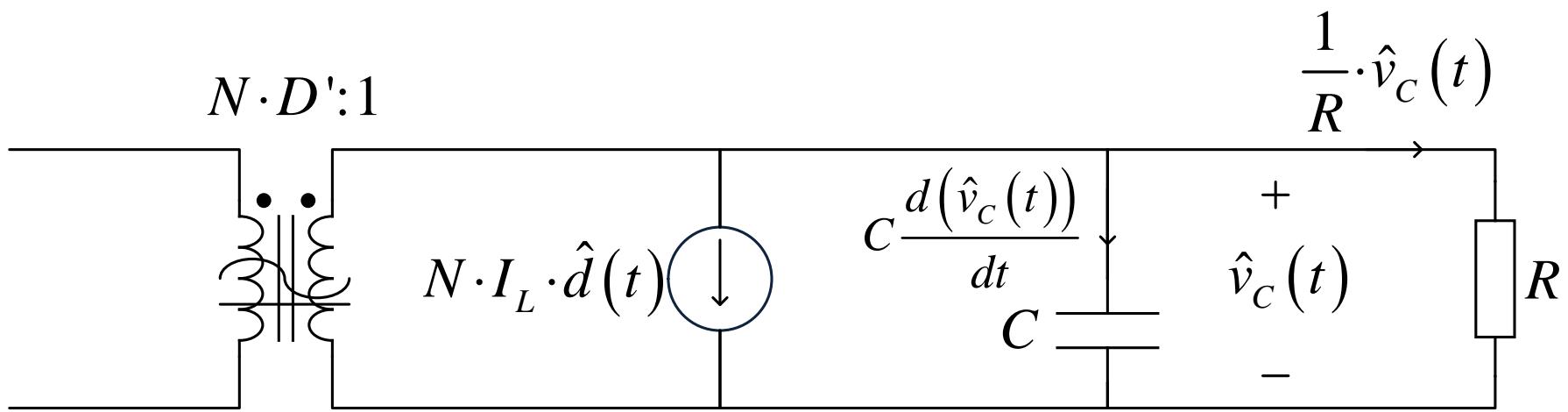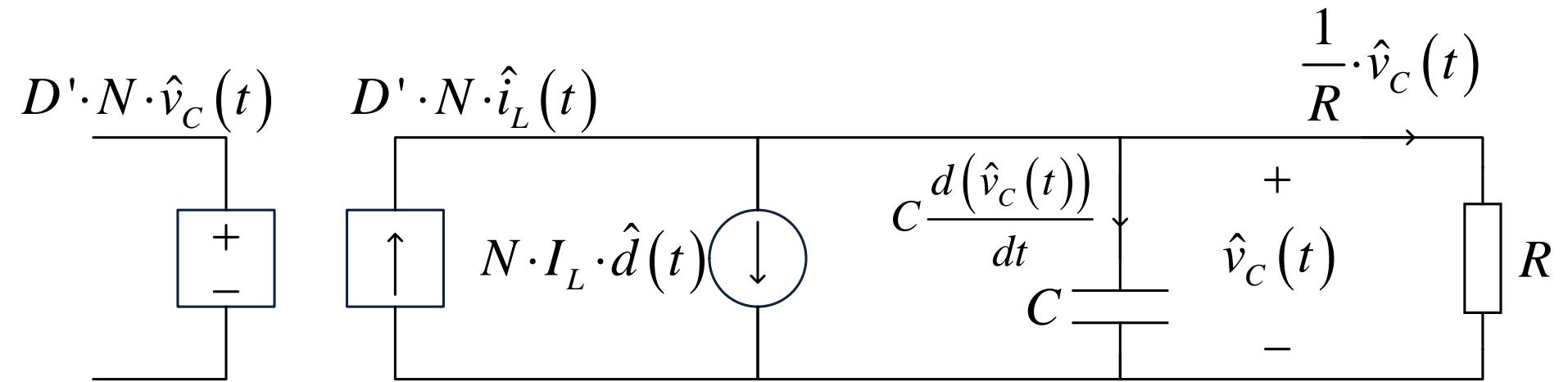

Complete Flyback Model

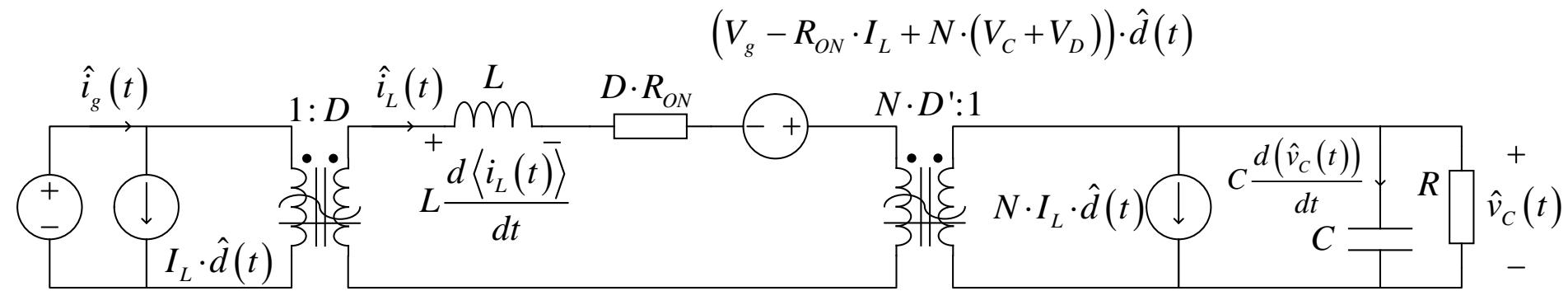


Complete Flyback Model

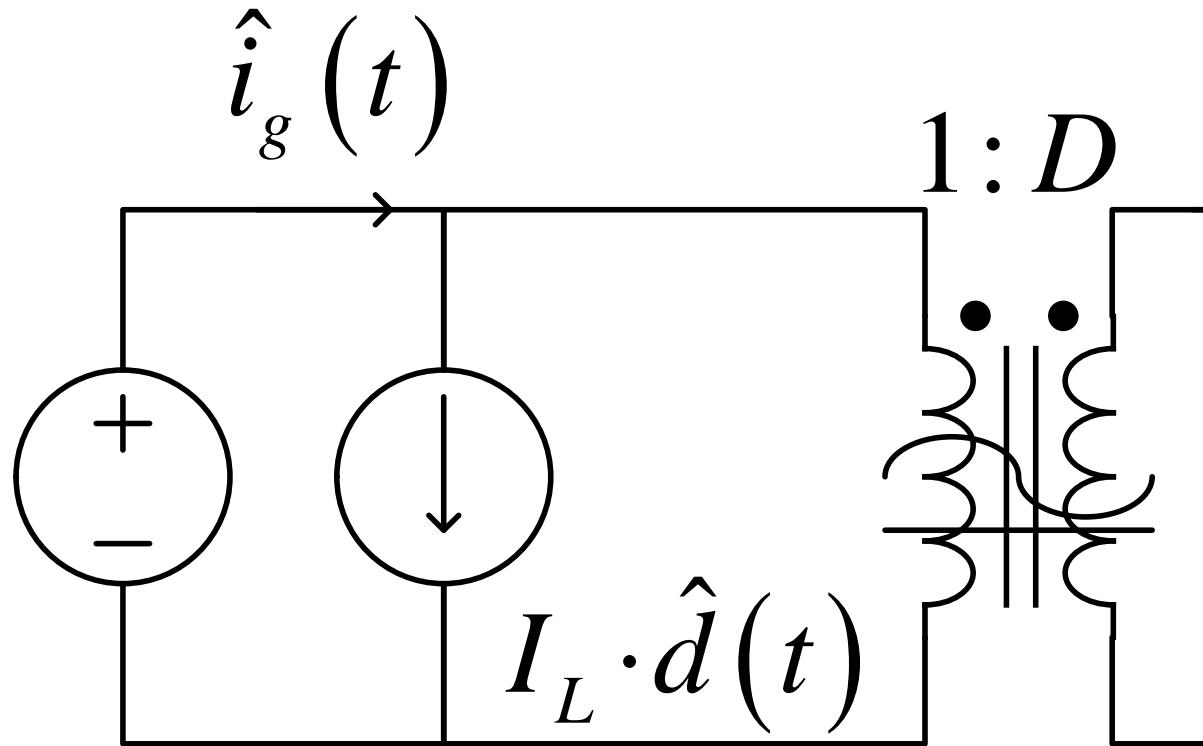


Complete Flyback Model

+

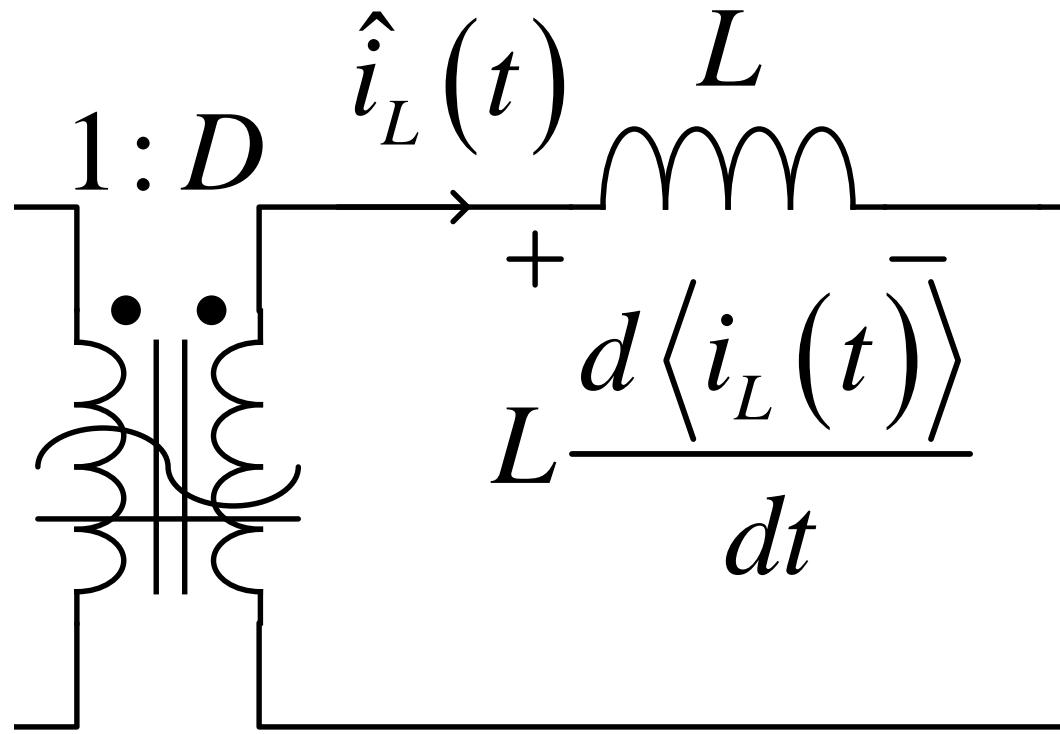


Complete Flyback Model
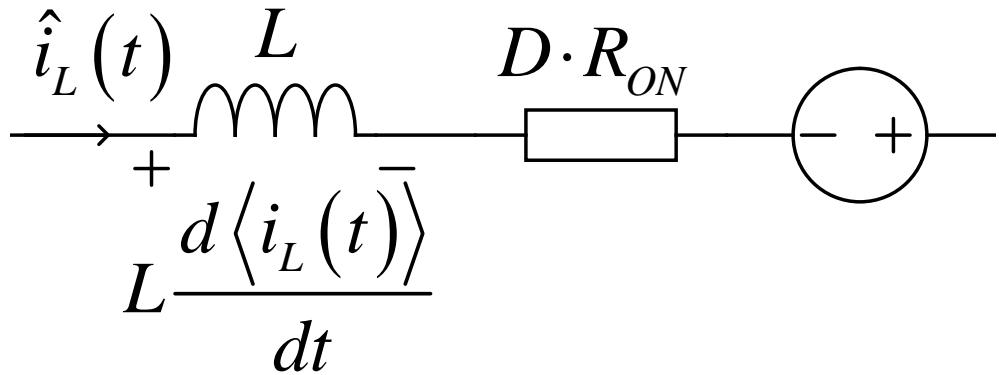
$$(V_g - R_{ON} \cdot I_L + N \cdot (V_C + V_D)) \cdot \hat{d}(t)$$




Complete Flyback Model

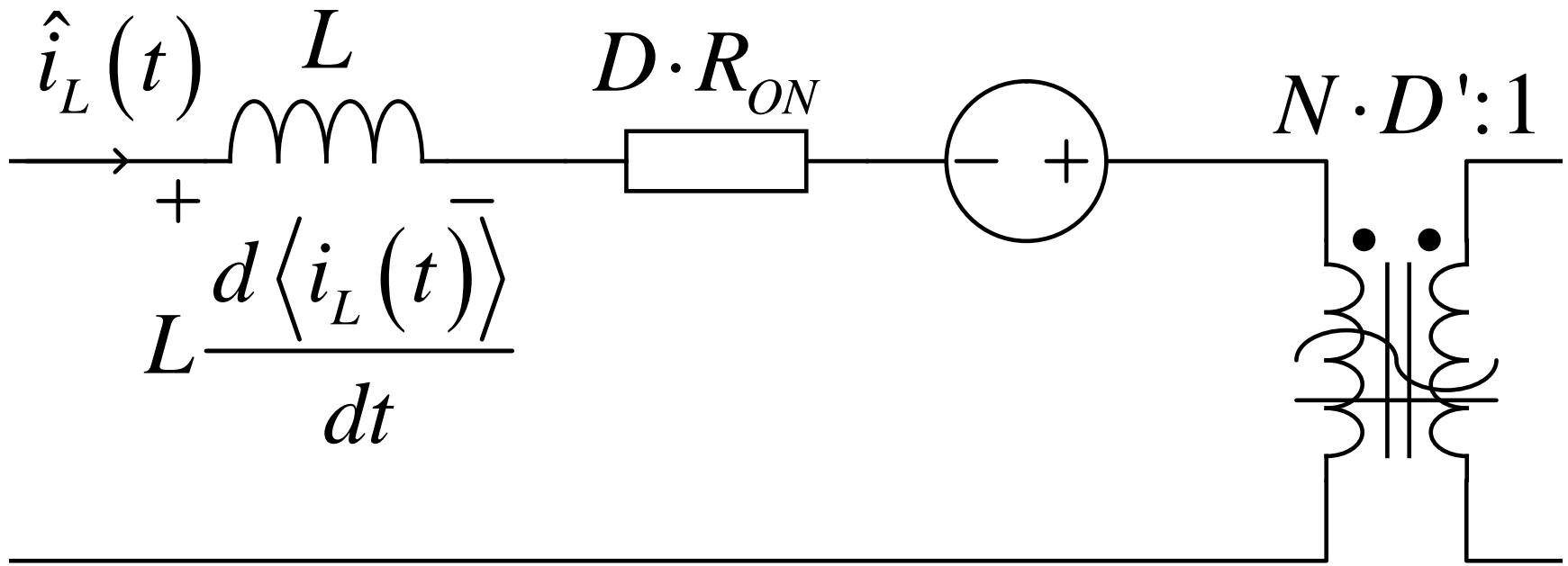


Complete Flyback Model

+

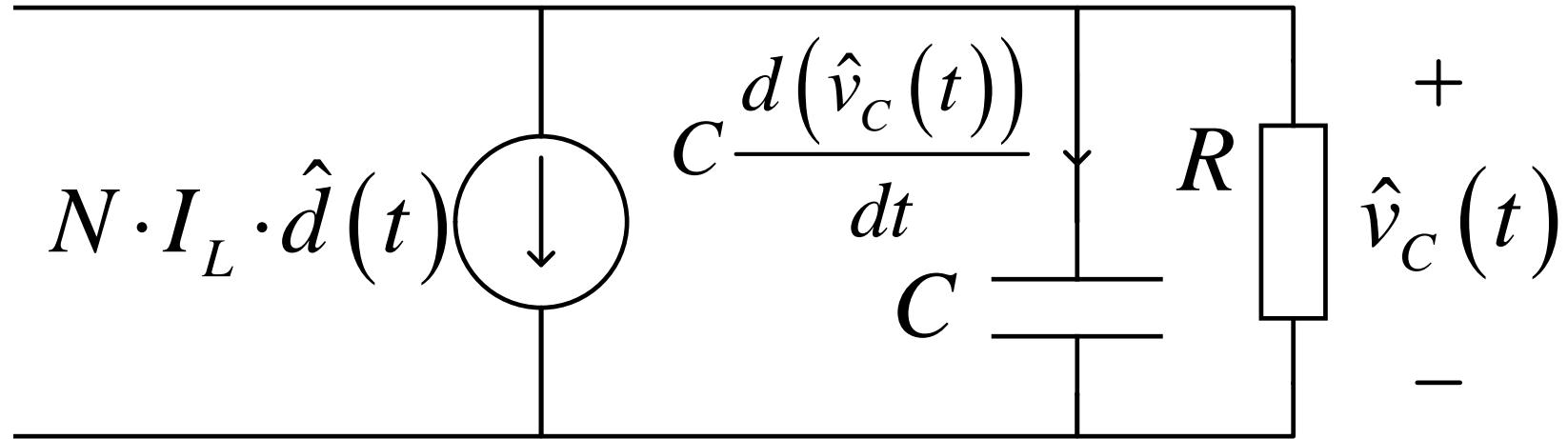


Control-To-Output Transfer Function

$$G_{vd}(s) = \left. \frac{\hat{v}_c(s)}{\hat{d}(s)} \right|_{\hat{v}_g=0}$$

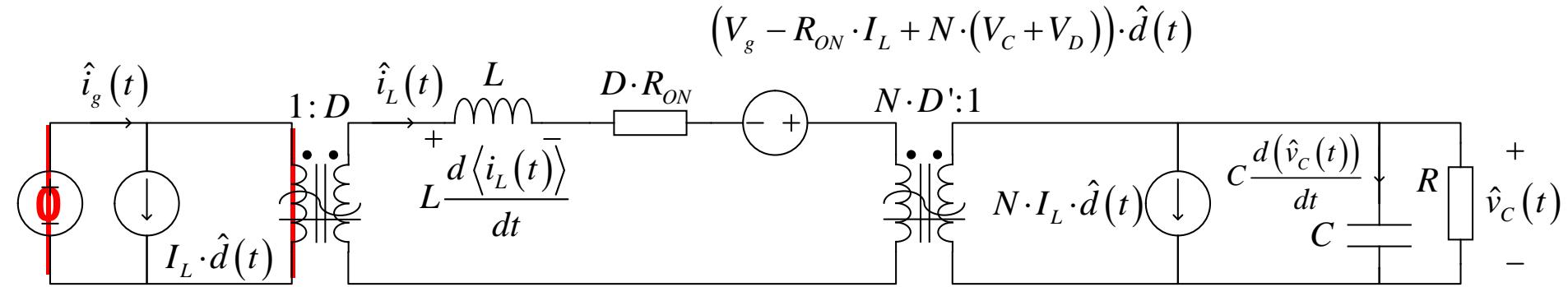



Control-To-Output Transfer Function

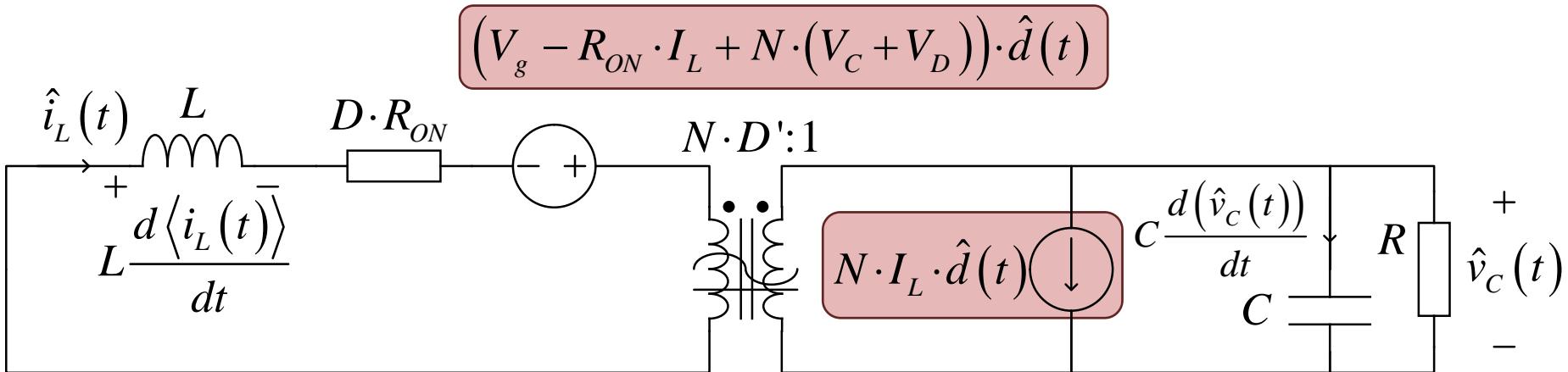

Still Have Two dhat Terms

Solve By Using Superposition



Control-To-Output Transfer Function

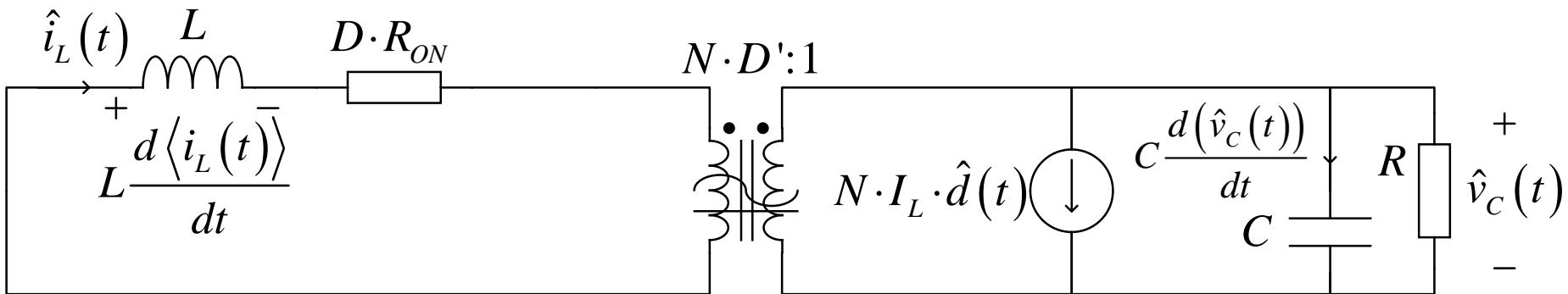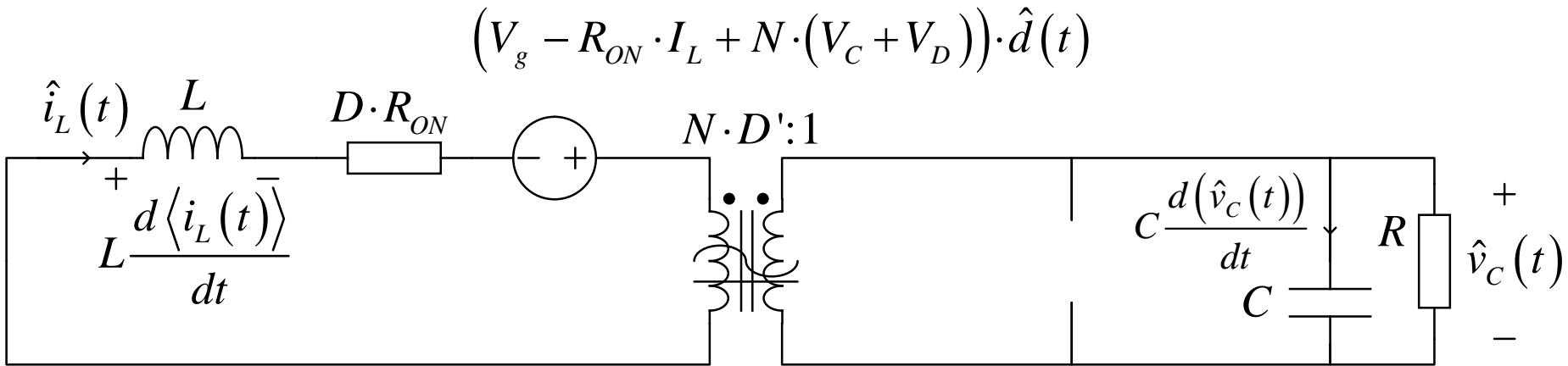

Control-To-Output Transfer Function

$$\rightarrow V' = V_g - R_{ON} \cdot I_L + N \cdot (V_C + V_D)$$
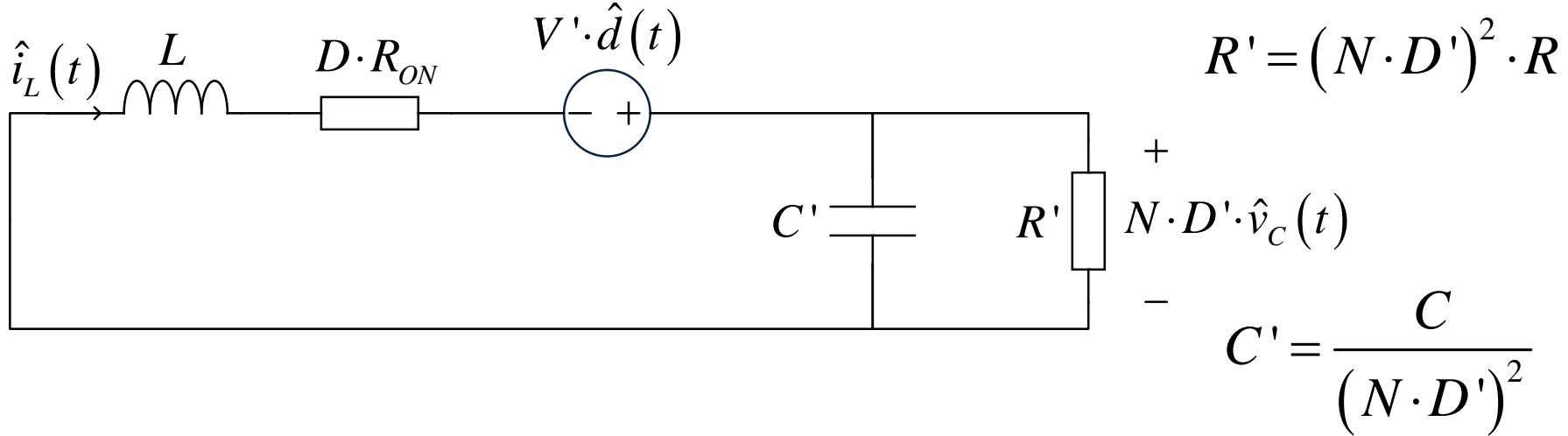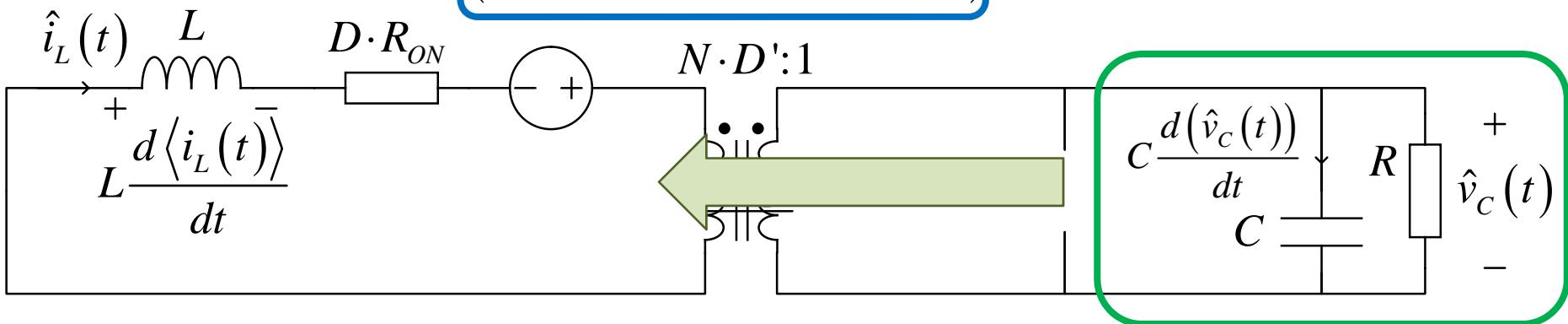
$$(V_g - R_{ON} \cdot I_L + N \cdot (V_C + V_D)) \cdot \hat{d}(t)$$




$$C' = \frac{C}{(N \cdot D')^2}$$

$$R' = (N \cdot D')^2 \cdot R$$

Control-To-Output Transfer Function

$$N \cdot D' \cdot \hat{v}_C(s) = \frac{R' \parallel \frac{1}{s \cdot C'}}{s \cdot L + D \cdot R_{ON} + R' \parallel \frac{1}{s \cdot C'}} \cdot V' \cdot \hat{d}(t)$$
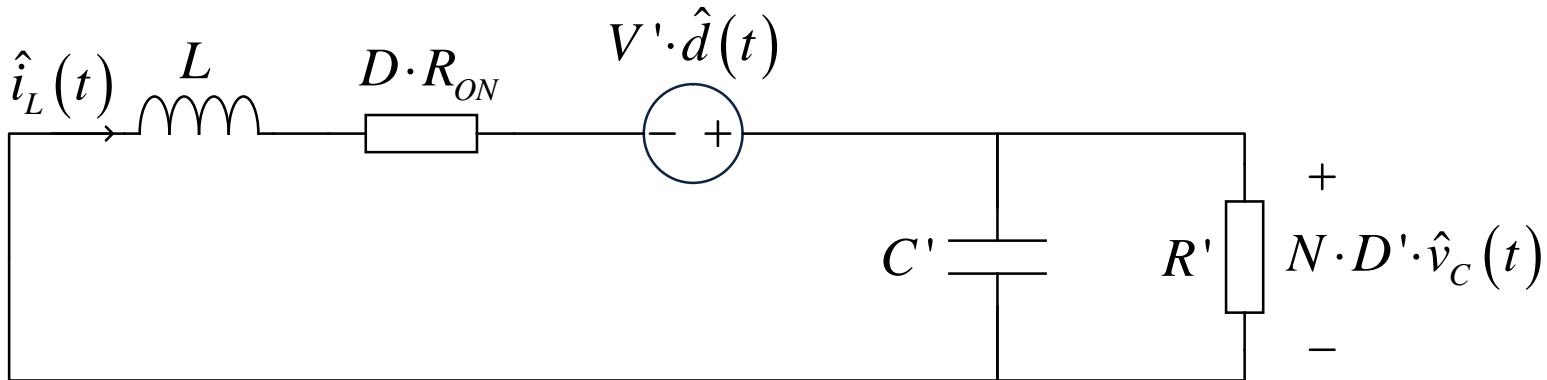
$$G_{vd1}(s) = \frac{\hat{v}_C(s)}{\hat{d}(t)} = \frac{V'}{N \cdot D'} \cdot \frac{R' \parallel \frac{1}{s \cdot C'}}{s \cdot L + D \cdot R_{ON} + R' \parallel \frac{1}{s \cdot C'}}$$



Control-To-Output Transfer Function

$$\begin{aligned} R' \parallel \frac{1}{s \cdot C'} &= \frac{R' \cdot \frac{1}{s \cdot C'}}{R' + \frac{1}{s \cdot C'}} \cdot \frac{s \cdot C'}{s \cdot C'} = \frac{R'}{1 + s \cdot R' \cdot C'} \\ \frac{R' \parallel \frac{1}{s \cdot C'}}{s \cdot L + D \cdot R_{ON} + R' \parallel \frac{1}{s \cdot C'}} &= \frac{\frac{R'}{1 + s \cdot R' \cdot C'}}{s \cdot L + D \cdot R_{ON} + \frac{R'}{1 + s \cdot R' \cdot C'}} \cdot \frac{1 + s \cdot R' \cdot C'}{1 + s \cdot R' \cdot C'} \\ &= \frac{R'}{s \cdot L + s^2 \cdot R' \cdot C' \cdot L + D \cdot R_{ON} + s \cdot D \cdot R_{ON} \cdot R' \cdot C' + R'} \\ &= \frac{R'}{R' + D \cdot R_{ON} + s \cdot L + s \cdot D \cdot R_{ON} \cdot R' \cdot C' + s^2 \cdot R' \cdot C' \cdot L} \cdot \frac{\frac{1}{R'}}{\frac{1}{R'}} \\ &= \frac{1}{1 + \frac{D \cdot R_{ON}}{R'} + s \cdot \left(\frac{L}{R'} + D \cdot R_{ON} \cdot C' \right) + s^2 \cdot C' \cdot L} \end{aligned}$$

Control-To-Output Transfer Function


$$\frac{R' \parallel \frac{1}{s \cdot C'}}{\frac{1}{s \cdot L + D \cdot R_{ON} + R' \parallel \frac{1}{s \cdot C'}}} = \frac{1}{1 + \frac{D \cdot R_{ON}}{R'} + s \cdot \left(\frac{L}{R'} + D \cdot R_{ON} \cdot C' \right) + s^2 \cdot C' \cdot L}$$
$$R' = (N \cdot D')^2 \cdot R \quad C' = \frac{C}{(N \cdot D')^2}$$
$$= \frac{1}{1 + \frac{D \cdot R_{ON}}{(N \cdot D')^2 \cdot R} + s \cdot \left(\frac{L}{(N \cdot D')^2 \cdot R} + D \cdot R_{ON} \cdot \frac{C}{(N \cdot D')^2} \right) + s^2 \cdot \frac{C}{(N \cdot D')^2} \cdot L}$$

Control-To-Output Transfer Function


$$G_{vd1}(s) = \frac{V'}{N \cdot D'} \cdot \frac{1}{1 + \frac{D \cdot R_{ON}}{(N \cdot D')^2 \cdot R} + s \cdot \left(\frac{L}{(N \cdot D')^2 \cdot R} + \frac{D \cdot R_{ON} \cdot C}{(N \cdot D')^2} \right) + s^2 \cdot \frac{L \cdot C}{(N \cdot D')^2}}$$

$$V' = V_g - R_{ON} \cdot I_L + N \cdot (V_C + V_D)$$

Control-To-Output Transfer Function

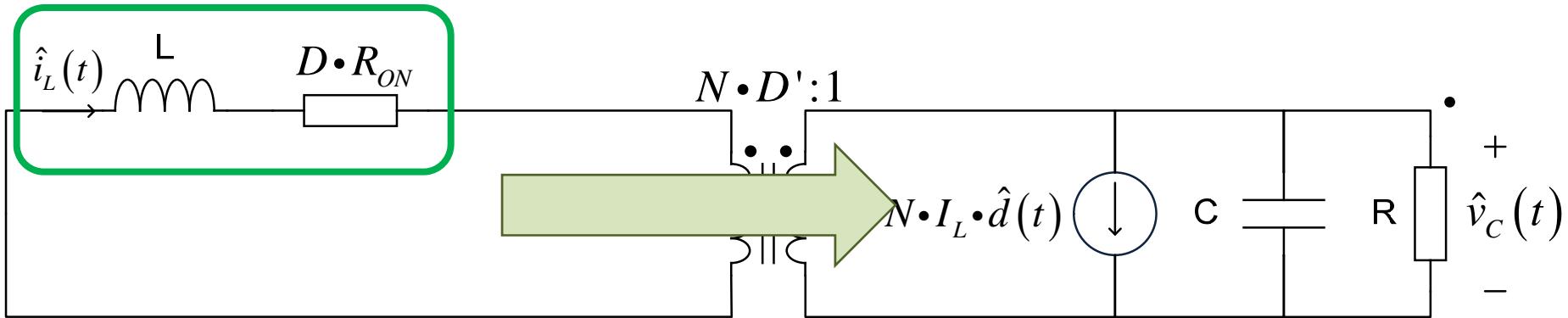

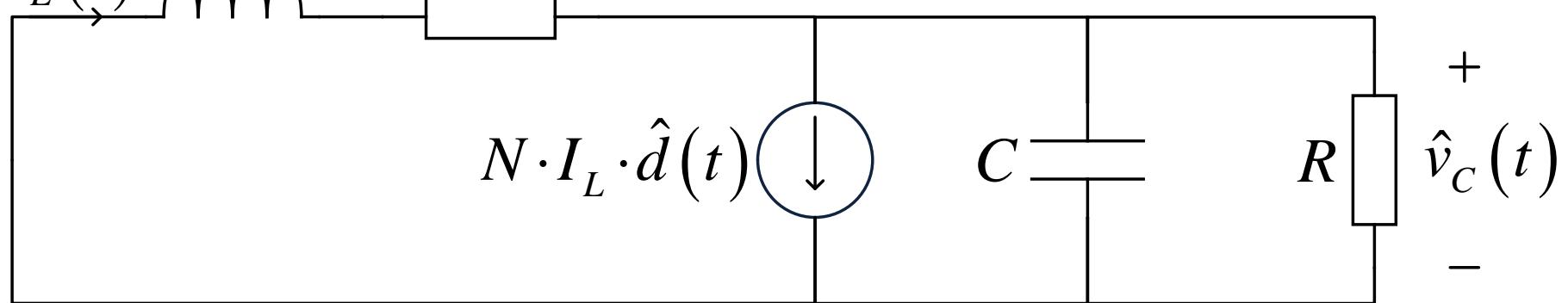
$$L' = \frac{L}{(N \cdot D')^2}$$
$$\hat{i}_L(t)$$
$$R' = \frac{D \cdot R_{ON}}{(N \cdot D')^2}$$



Control-To-Output Transfer Function

$$\hat{v}_c(t) = -N \cdot I_L \cdot \hat{d}(t) \cdot \left[(s \cdot L' + R') \parallel \left(\frac{1}{s \cdot C} \right) \parallel R \right]$$
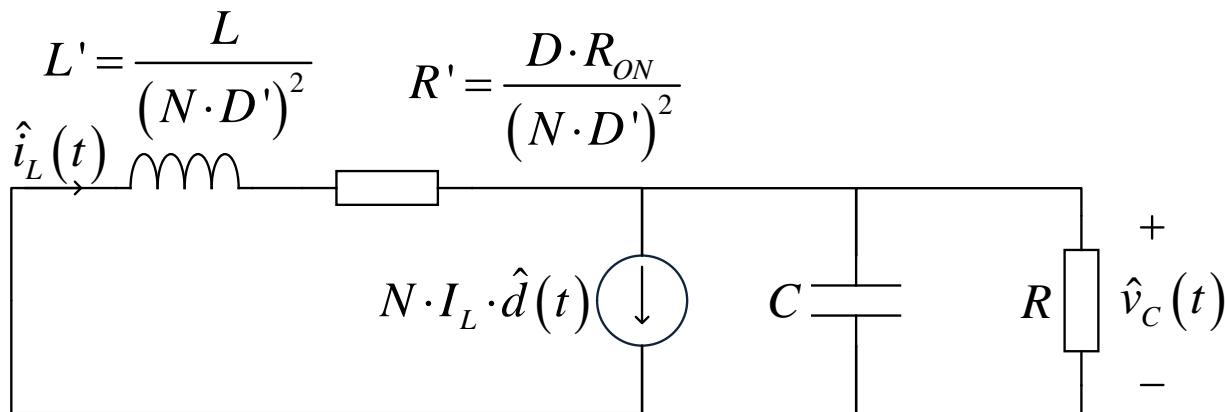
$$= -N \cdot I_L \cdot \hat{d}(t) \cdot \frac{1}{\frac{1}{s \cdot L' + R'} + \frac{1}{\frac{1}{s \cdot C}} + \frac{1}{R}}$$



Control-To-Output Transfer Function

$$\begin{aligned} \frac{1}{\frac{1}{s \cdot L' + R'} + \frac{1}{R} + \frac{1}{s \cdot C}} &= \frac{1}{\frac{1}{s \cdot L' + R'} + s \cdot C + \frac{1}{R}} \\ &= \frac{1}{\frac{1}{s \cdot L' + R'} + \frac{1 + s \cdot R \cdot C}{R}} \\ &= \frac{1}{\frac{R + (s \cdot L' + R') \cdot (1 + s \cdot R \cdot C)}{R \cdot (s \cdot L' + R')}} \\ &= \frac{R \cdot (s \cdot L' + R')}{R + s \cdot L' + R' + s \cdot R \cdot C \cdot R' + s^2 \cdot R \cdot L' \cdot C} \end{aligned}$$

Control-To-Output Transfer Function

$$\frac{\frac{1}{s \cdot L' + R'}}{\frac{1}{s \cdot L' + R'} + \frac{1}{s \cdot C}} = \frac{R \cdot (s \cdot L' + R')}{R + R' + s \cdot L' + s \cdot R \cdot C \cdot R' + s^2 \cdot R \cdot L' \cdot C} \cdot \frac{\frac{1}{R}}{\frac{1}{R}}$$
$$= \frac{s \cdot L' + R'}{1 + \frac{R'}{R} + s \cdot \left(\frac{L'}{R} + R' \cdot C \right) + s^2 \cdot L' \cdot C}$$
$$L' = \frac{L}{(N \cdot D')^2} \quad R' = \frac{D \cdot R_{ON}}{(N \cdot D')^2}$$

Control-To-Output Transfer Function

$$\begin{aligned} &= \frac{s \cdot \frac{L}{(N \cdot D')^2} + \frac{D \cdot R_{ON}}{(N \cdot D')^2}}{1 + \frac{D \cdot R_{ON}}{(N \cdot D')^2} + s \cdot \left(\frac{\frac{L}{(N \cdot D')^2}}{R} + \frac{D \cdot R_{ON}}{(N \cdot D')^2} \cdot C \right) + s^2 \cdot \frac{L}{(N \cdot D')^2} \cdot C} \\ &= \frac{\frac{1}{(N \cdot D')^2} \cdot (s \cdot L + D \cdot R_{ON})}{1 + \frac{D \cdot R_{ON}}{(N \cdot D')^2 \cdot R} + s \cdot \left(\frac{L}{(N \cdot D')^2 \cdot R} + \frac{D \cdot R_{ON} \cdot C}{(N \cdot D')^2} \right) + s^2 \cdot \frac{L \cdot C}{(N \cdot D')^2}} \end{aligned}$$

Control-To-Output Transfer Function

$$G_{vd2}(s) = \frac{\hat{v}_c(t)}{\hat{d}(t)}$$

$$= -N \cdot I_L \cdot \frac{\frac{1}{(N \cdot D')^2} \cdot (s \cdot L + D \cdot R_{ON})}{1 + \frac{D \cdot R_{ON}}{(N \cdot D')^2 \cdot R} + s \cdot \left(\frac{L}{(N \cdot D')^2 \cdot R} + \frac{D \cdot R_{ON} \cdot C}{(N \cdot D')^2} \right) + s^2 \cdot \frac{L \cdot C}{(N \cdot D')^2}}$$

Control-To-Output Transfer Function

$$G_{vd}(s) = G_{vd1}(s) + G_{vd2}(s)$$

$$G_{vd}(s) = \frac{\text{num}\left(G_{vd}(s)\right)}{\text{den}\left(G_{vd}(s)\right)} = \frac{\text{num}\left(G_{vd1}(s)\right)}{\text{den}\left(G_{vd1}(s)\right)} + \frac{\text{num}\left(G_{vd2}(s)\right)}{\text{den}\left(G_{vd2}(s)\right)}$$

$$\text{den}\left(G_{vd1}(s)\right) = \text{den}\left(G_{vd2}(s)\right) = \text{den}\left(G_{vd}(s)\right)$$

$$G_{vd}(s) = \frac{\text{num}\left(G_{vd}(s)\right)}{\text{den}\left(G_{vd}(s)\right)} = \frac{\text{num}\left(G_{vd1}(s)\right) + \text{num}\left(G_{vd2}(s)\right)}{\text{den}\left(G_{vd}(s)\right)}$$

Control-To-Output Transfer Function

$$num(G_{vd1}(s)) = \frac{V'}{N \cdot D'}$$

$$num(G_{vd2}(s)) = -N \cdot I_L \cdot \frac{1}{(N \cdot D')^2} \cdot (s \cdot L + D \cdot R_{ON})$$

$$num(G_{vd1}(s)) + num(G_{vd2}(s)) = \frac{V'}{N \cdot D'} - N \cdot I_L \cdot \frac{1}{(N \cdot D')^2} \cdot (s \cdot L + D \cdot R_{ON})$$

Control-To-Output Transfer Function

$$\begin{aligned}
 num(G_{vd1}(s)) + num(G_{vd2}(s)) &= \frac{V' \cdot N \cdot D'}{(N \cdot D')^2} - \frac{N \cdot I_L \cdot (s \cdot L + D \cdot R_{ON})}{(N \cdot D')^2} \\
 &= \frac{V' \cdot N \cdot D' - N \cdot D \cdot R_{ON} \cdot I_L - s \cdot N \cdot I_L \cdot L}{(N \cdot D')^2} \\
 &= \frac{V' \cdot N \cdot D' - N \cdot D \cdot R_{ON} \cdot I_L}{(N \cdot D')^2} \cdot \left(1 - s \cdot \frac{N \cdot I_L \cdot L}{V' \cdot N \cdot D' - N \cdot D \cdot R_{ON} \cdot I_L} \right) \\
 &= \frac{V' \cdot D' - D \cdot R_{ON} \cdot I_L}{N \cdot D'^2} \cdot \boxed{\left(1 - s \cdot \frac{N \cdot I_L \cdot L}{V' \cdot N \cdot D' - N \cdot D \cdot R_{ON} \cdot I_L} \right)}
 \end{aligned}$$

!

Control To Output Transfer Function

Quick check on the algebra: Are the units correct?

$$1 - s \cdot \frac{N \cdot I_L \cdot L}{V' \cdot N \cdot D' - N \cdot D \cdot R_{ON} \cdot I_L}$$

$$\Rightarrow \frac{\frac{1}{\nu} \cdot A \cdot \frac{\nu \cdot s}{A}}{\frac{s}{\nu - \Omega \cdot A}} \Rightarrow \frac{\nu}{\nu} \Rightarrow \text{Dimensionless}$$

Control-To-Output Transfer Function !

$$G_{vd}(s) = \frac{\frac{V' \cdot D' - D \cdot R_{ON} \cdot I_L}{N \cdot D'^2} \cdot \left(1 - s \cdot \frac{N \cdot I_L \cdot L}{V' \cdot N \cdot D' - N \cdot D \cdot R_{ON} \cdot I_L} \right)}{1 + \frac{D \cdot R_{ON}}{(N \cdot D')^2 \cdot R} + s \cdot \left(\frac{L}{(N \cdot D')^2 \cdot R} + \frac{D \cdot R_{ON} \cdot C}{(N \cdot D')^2} \right) + s^2 \cdot \frac{L \cdot C}{(N \cdot D')^2}}$$

$$V' = V_g - R_{ON} \cdot I_L + N \cdot (V_C + V_D)$$




Averaging Summary

- Write Circuit Differential Equations For Each State In Terms Of Averaged Values
- Average Over One Switching Cycle
 - Inductor Current
 - Capacitor Voltages
- Perturb And Linearize
 - DC Terms Are Zero
 - Discard 2nd And Higher Order Terms
- Construct The Circuit Model





Averaged Switch Modeling

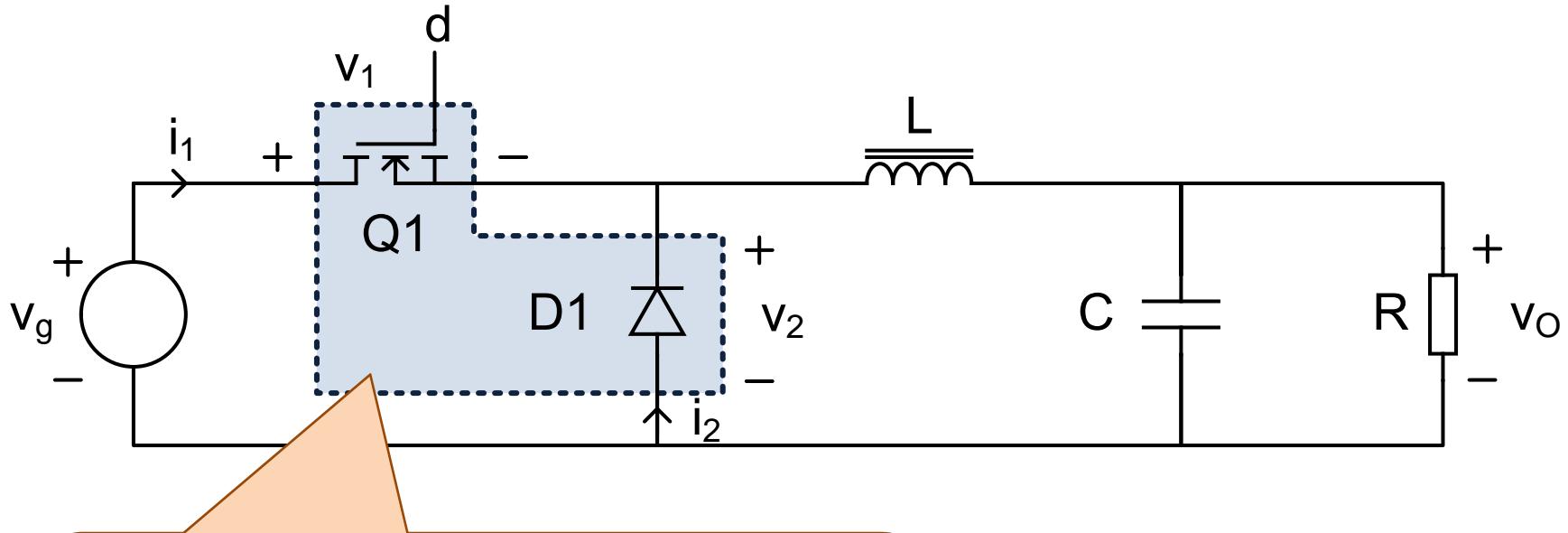


Two Port Switch Network
Includes All Nonlinear
And Time Varying Elements

Everything
Else Is
LTI


Boost And Buck-Boost Switch Networks

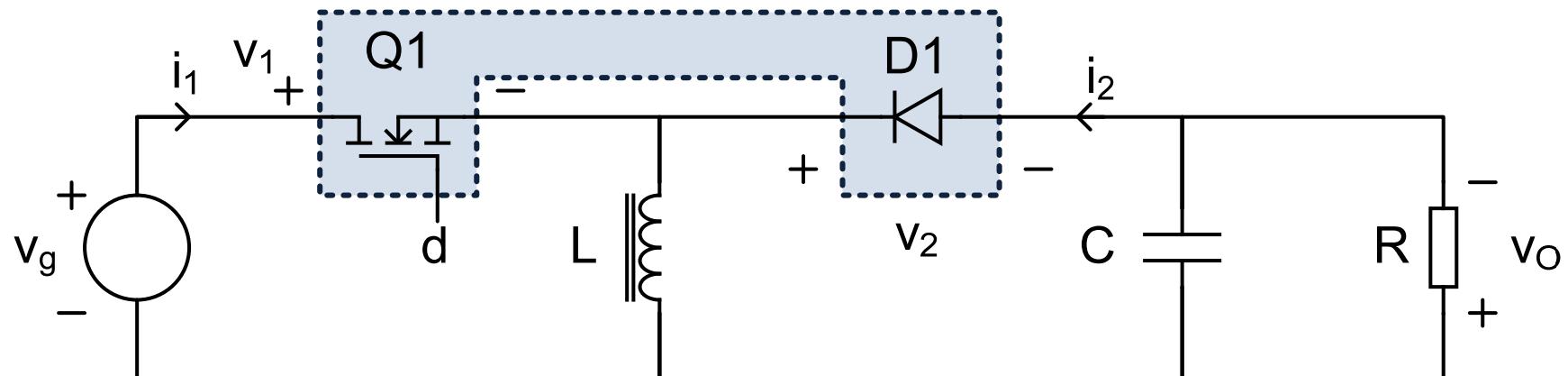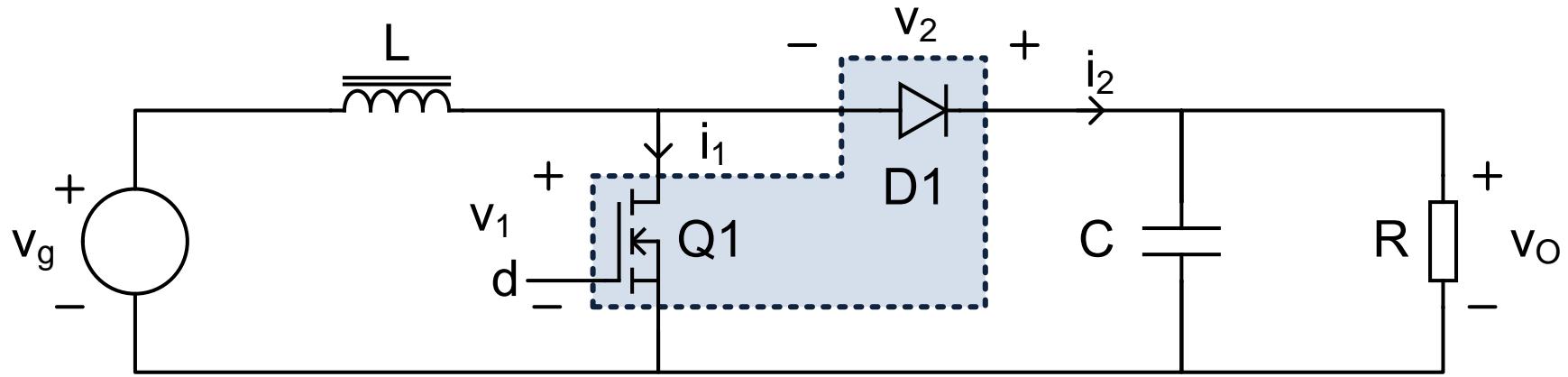


Averaged Switch Modeling

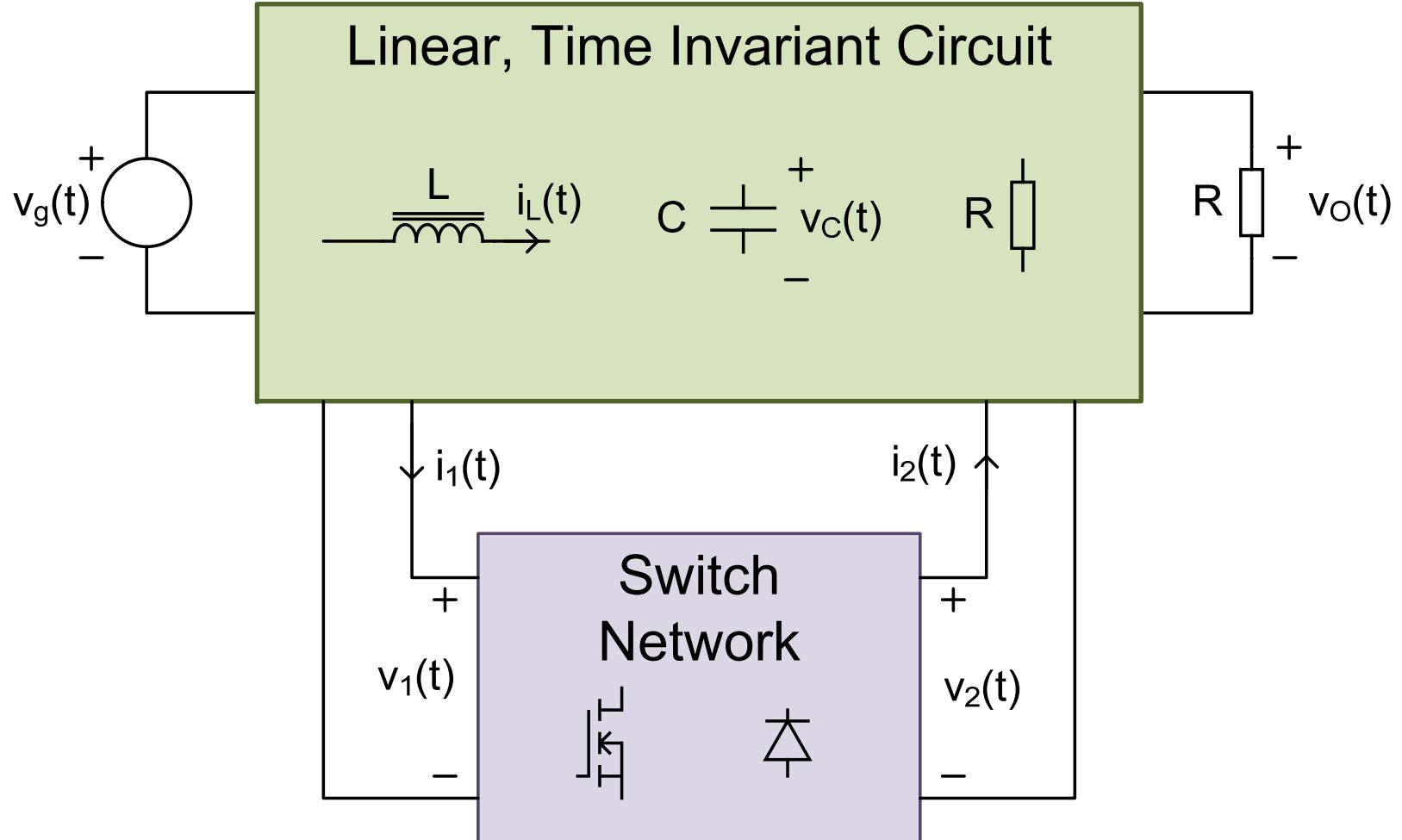


Averaged Switch Modeling

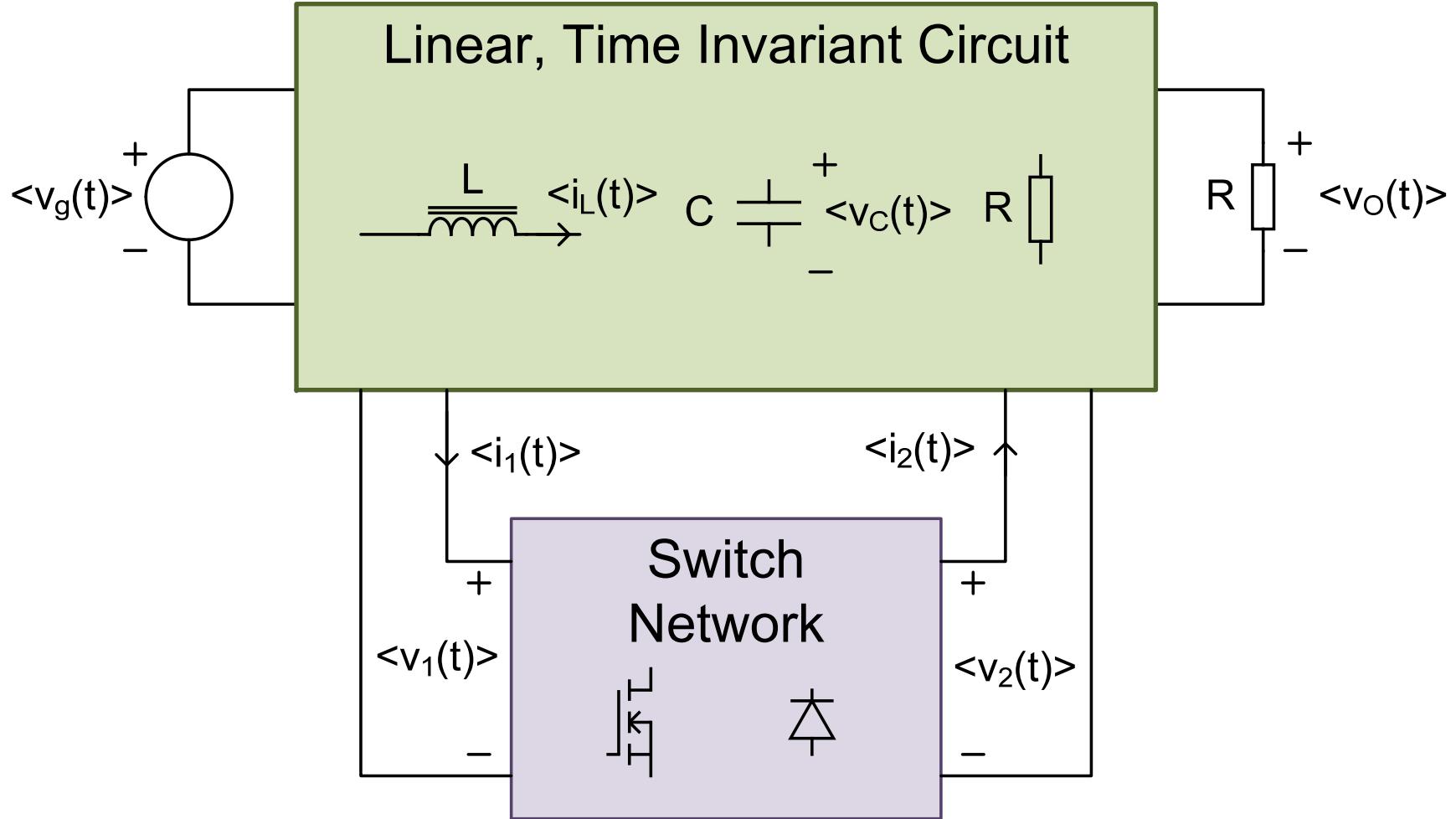

Averaged Switch Modeling

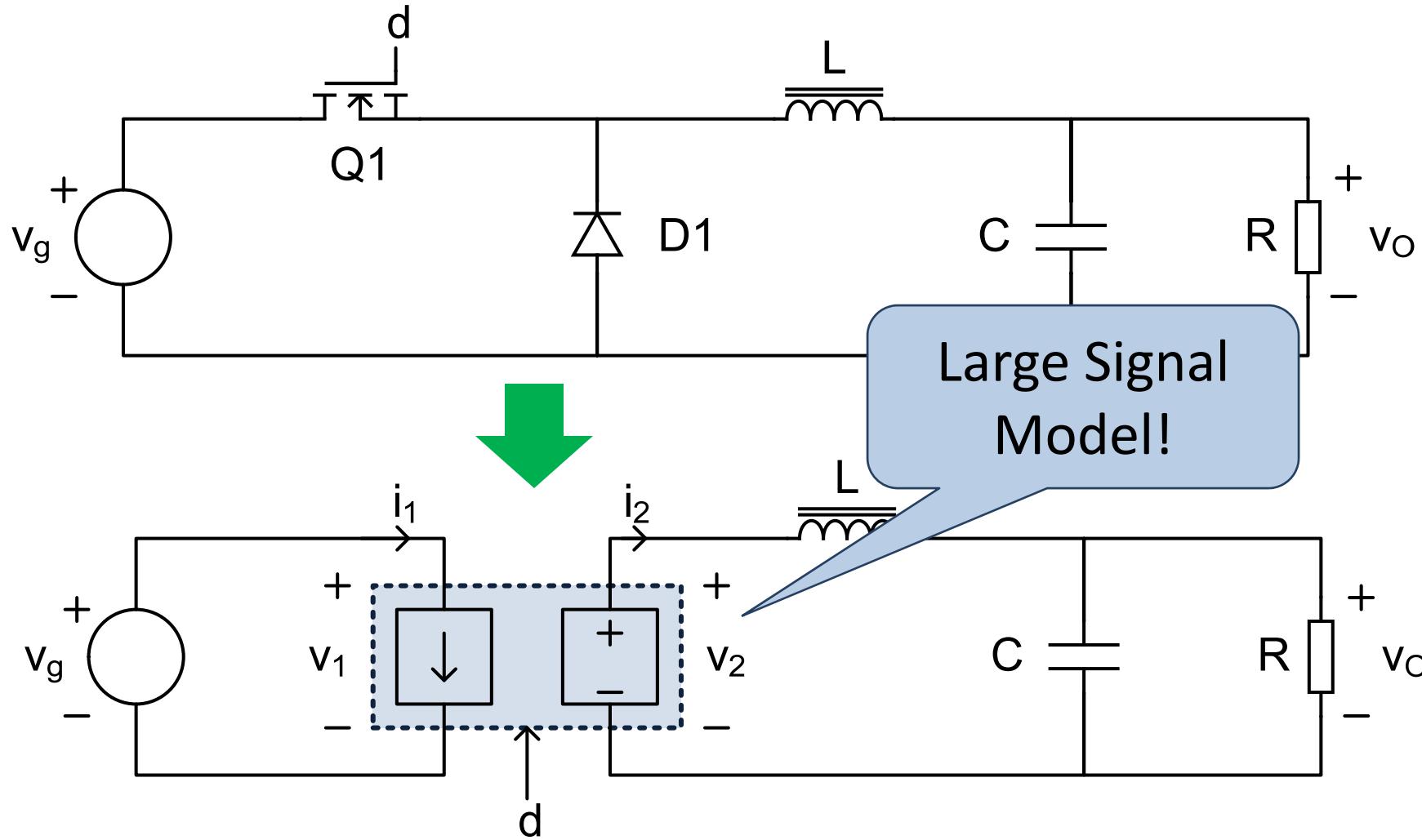

Averaged Switch Modeling

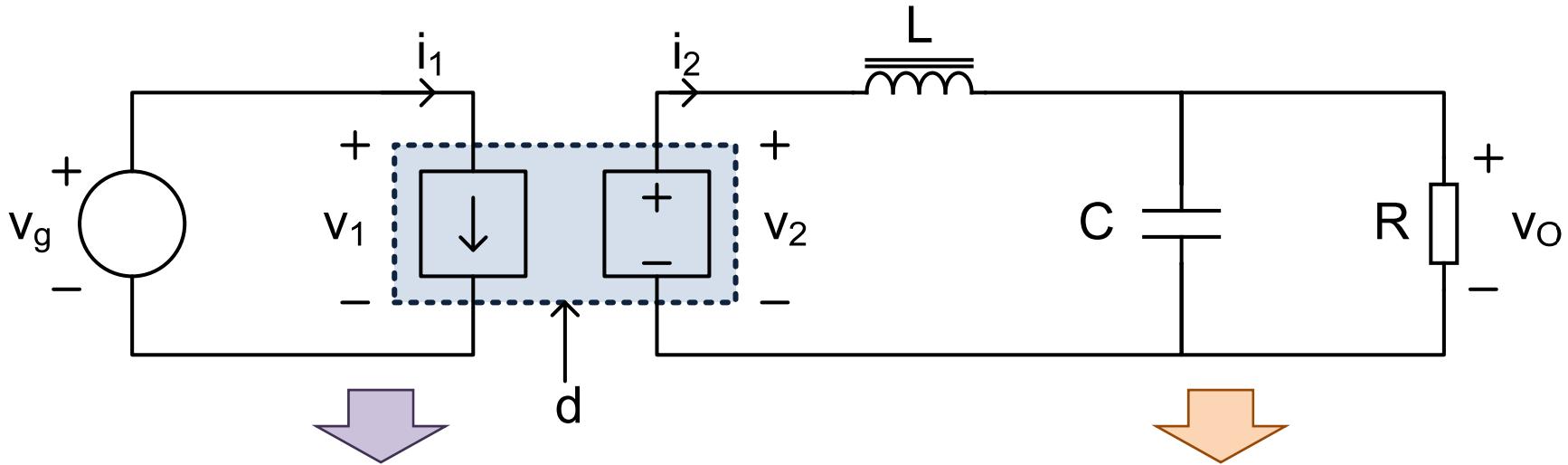

Circuit Simulation

Time Domain

(e.g. Transient Response)

Frequency Domain

(e.g. Bode Plots)

Linearization


Small Signal

Analytical Models

⇒ Transfer Functions




Buck Converter Model: Define Switch Network And Ports

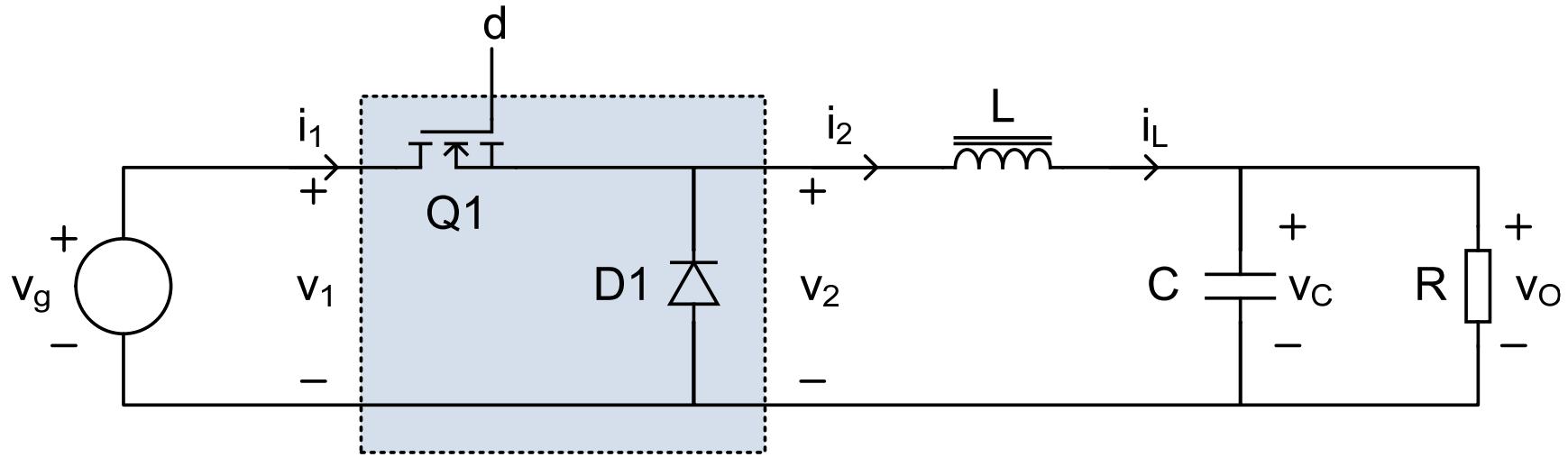


Port 1: v_1, i_1

Port 2: v_2, i_2

Buck Converter Model: Sketch Waveforms

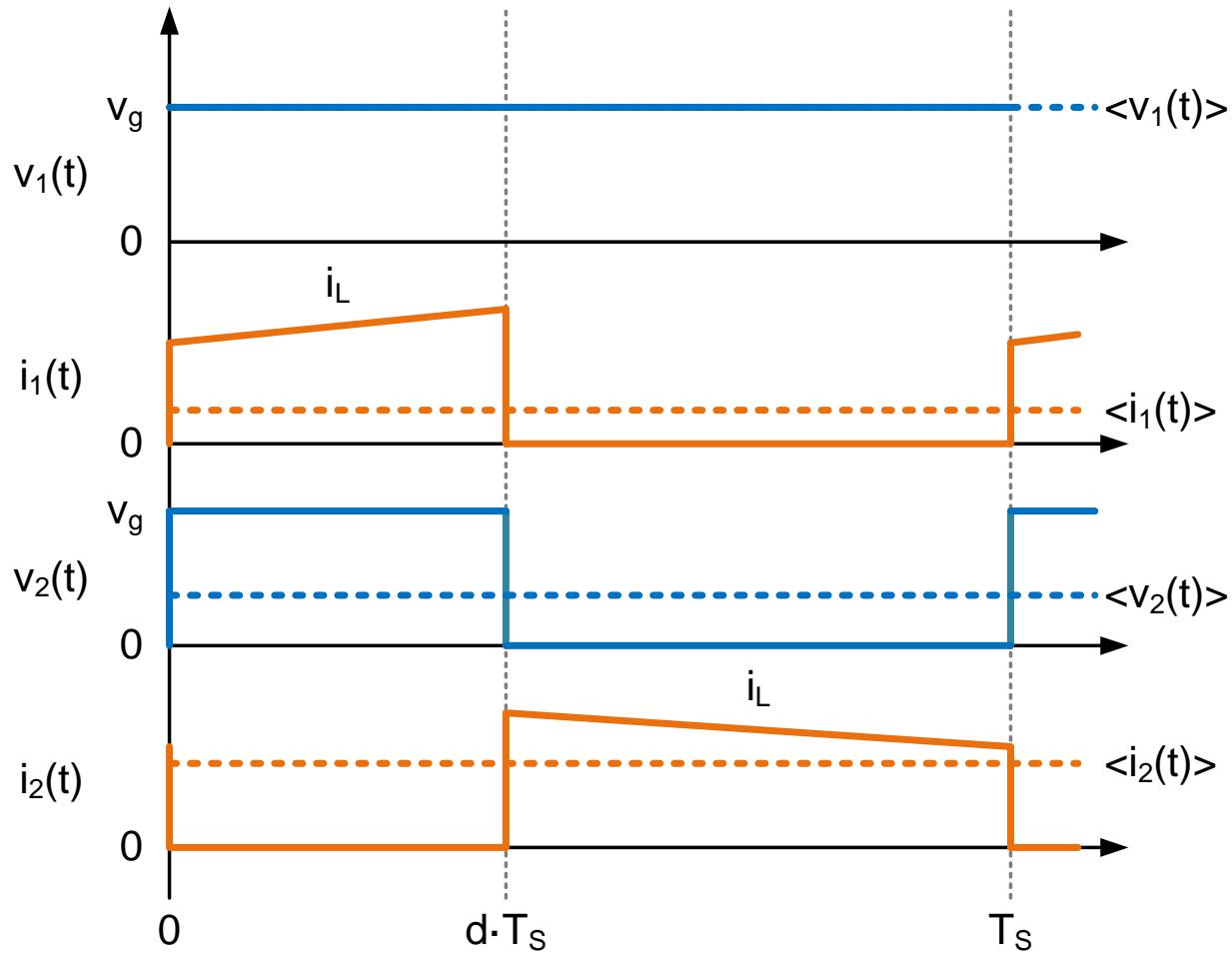

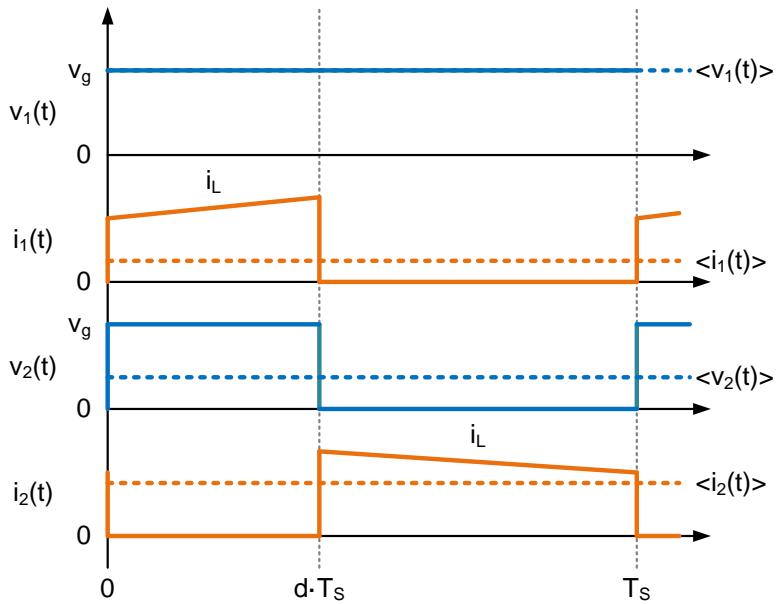Buck Converter Model: Average Switch Network Variables



$$\begin{aligned}\langle v_1(t) \rangle &= d \cdot \langle v_g(t) \rangle + d' \cdot \langle v_g(t) \rangle \\ &= \langle v_g(t) \rangle\end{aligned}$$

$$\begin{aligned}\langle i_1(t) \rangle &= d \cdot \langle i_L(t) \rangle + d' \cdot 0 \\ &= d \cdot \langle i_L(t) \rangle\end{aligned}$$

$$\begin{aligned}\langle v_2(t) \rangle &= d \cdot \langle v_g(t) \rangle + d' \cdot 0 \\ &= d \cdot \langle v_g(t) \rangle\end{aligned}$$

$$\begin{aligned}\langle i_2(t) \rangle &= d \cdot \langle i_L(t) \rangle + d' \cdot \langle i_L(t) \rangle \\ &= \langle i_L(t) \rangle\end{aligned}$$

Buck Converter Model: Eliminate Non-Switch Variables

$$\langle v_1(t) \rangle = d \cdot \langle v_g(t) \rangle + d' \cdot \langle v_g(t) \rangle$$

$$= \langle v_g(t) \rangle$$

$$\langle i_1(t) \rangle = d \cdot \langle i_L(t) \rangle + d' \cdot 0$$

$$= d \cdot \langle i_L(t) \rangle$$

$$\langle v_2(t) \rangle = d \cdot \langle v_g(t) \rangle = d \cdot \langle v_1(t) \rangle$$

$$\langle v_2(t) \rangle = d \cdot \langle v_g(t) \rangle + d' \cdot 0$$

$$= d \cdot \langle v_g(t) \rangle$$

$$\langle i_2(t) \rangle = d \cdot \langle i_L(t) \rangle + d' \cdot \langle i_L(t) \rangle$$

$$= \langle i_L(t) \rangle$$



Buck Converter Model: Eliminate Non-Switch Variables

$$\langle v_1(t) \rangle = d \cdot \langle v_g(t) \rangle + d' \cdot \langle v_g(t) \rangle \\ = \langle v_g(t) \rangle$$

$$\langle i_1(t) \rangle = d \cdot \langle i_L(t) \rangle + d' \cdot 0 \\ = d \cdot \langle i_L(t) \rangle$$

$$\langle v_2(t) \rangle = d \cdot \langle v_g(t) \rangle + d' \cdot 0 \\ = d \cdot \langle v_g(t) \rangle$$

$$\langle i_2(t) \rangle = d \cdot \langle i_L(t) \rangle + d' \cdot \langle i_L(t) \rangle \\ = \langle i_L(t) \rangle$$

$$\langle v_2(t) \rangle = d \cdot \langle v_g(t) \rangle = d \cdot \langle v_1(t) \rangle$$


$$\langle i_1(t) \rangle = d \cdot \langle i_L(t) \rangle = d \cdot \langle i_2(t) \rangle$$

Buck Converter Model: Create Switch Network Model

!


$$\langle i_1(t) \rangle = d(t) \cdot \langle i_2(t) \rangle$$
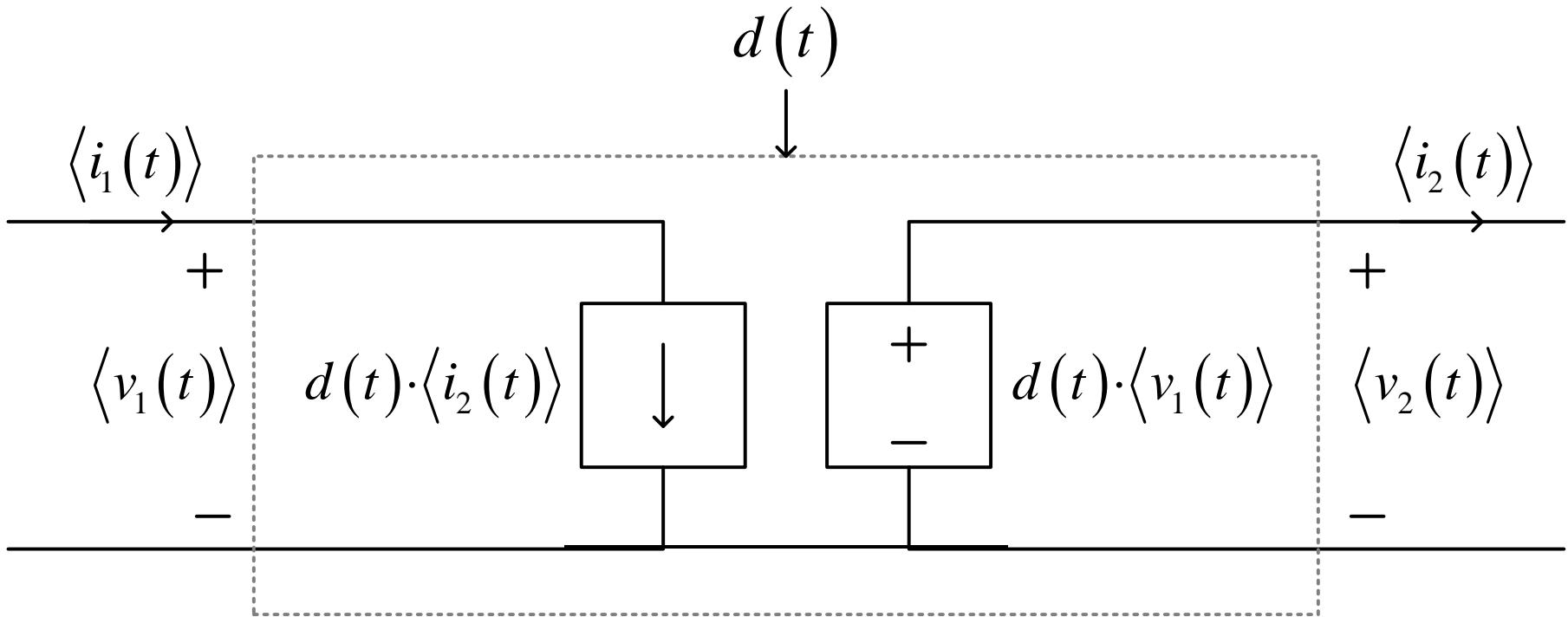
$$\langle v_2(t) \rangle = d(t) \cdot \langle v_1(t) \rangle$$




Buck Converter Model: Complete The Converter Model

!

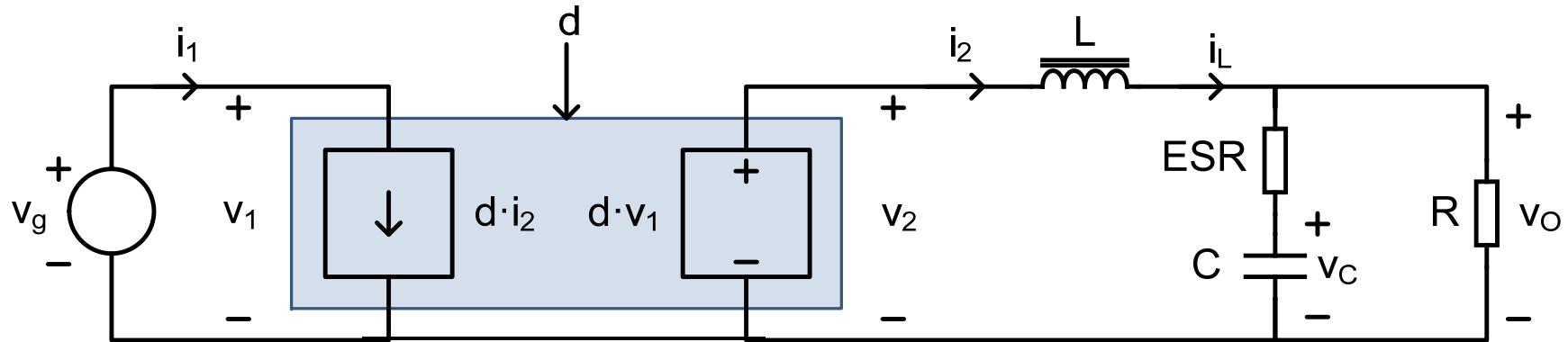



Buck Converter Model: Complete The Converter Model

!

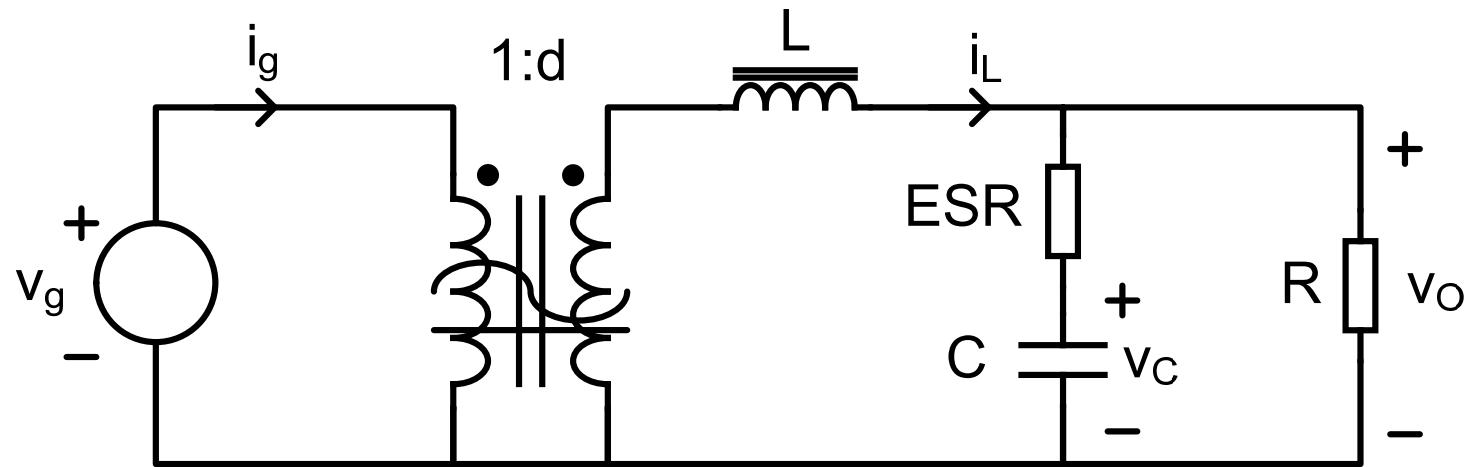




Another View Of The Average Switch Model

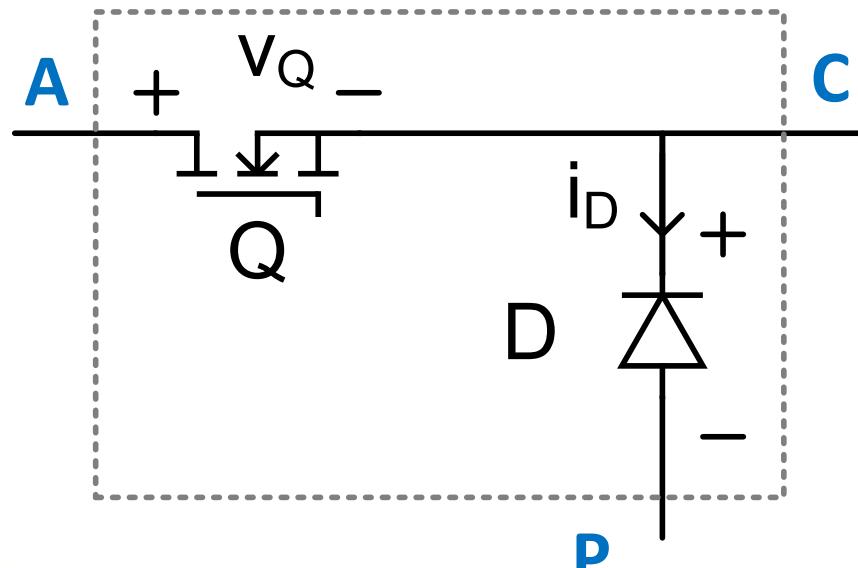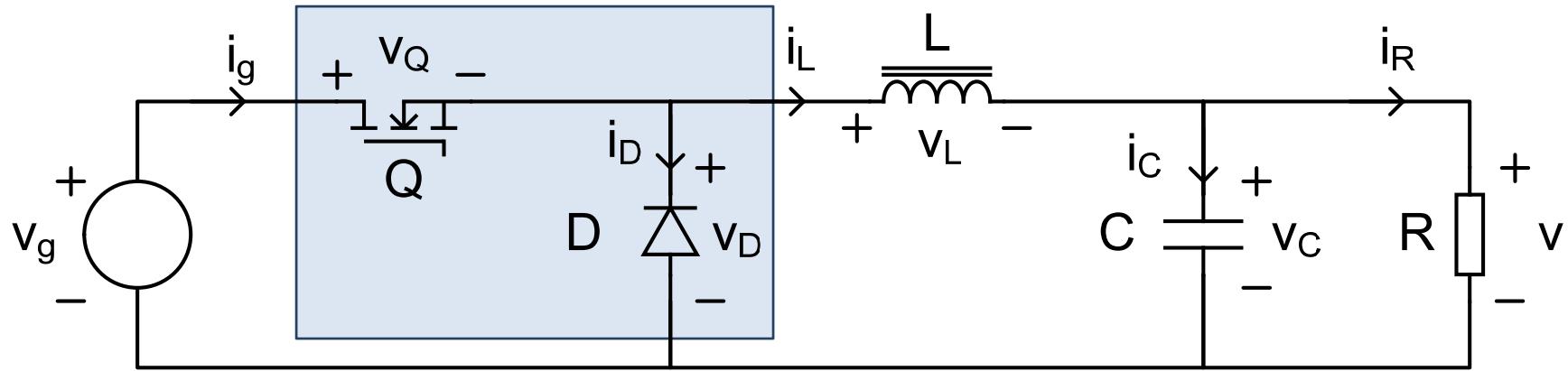


Another View Of The Average Switch Model


+

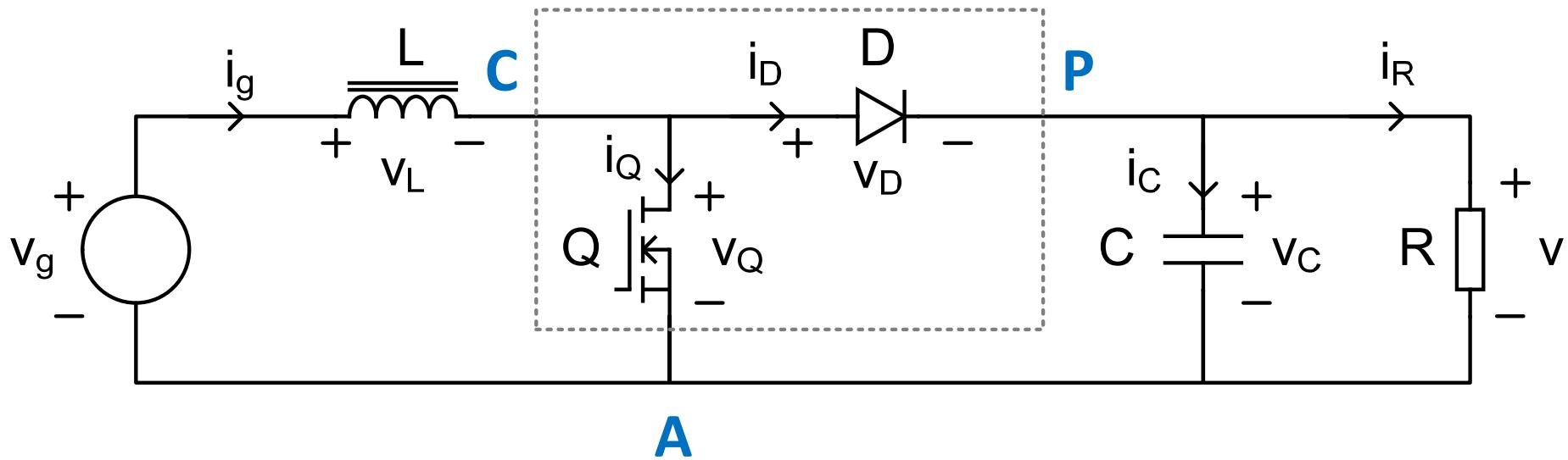

Another View Of The Average Switch Model

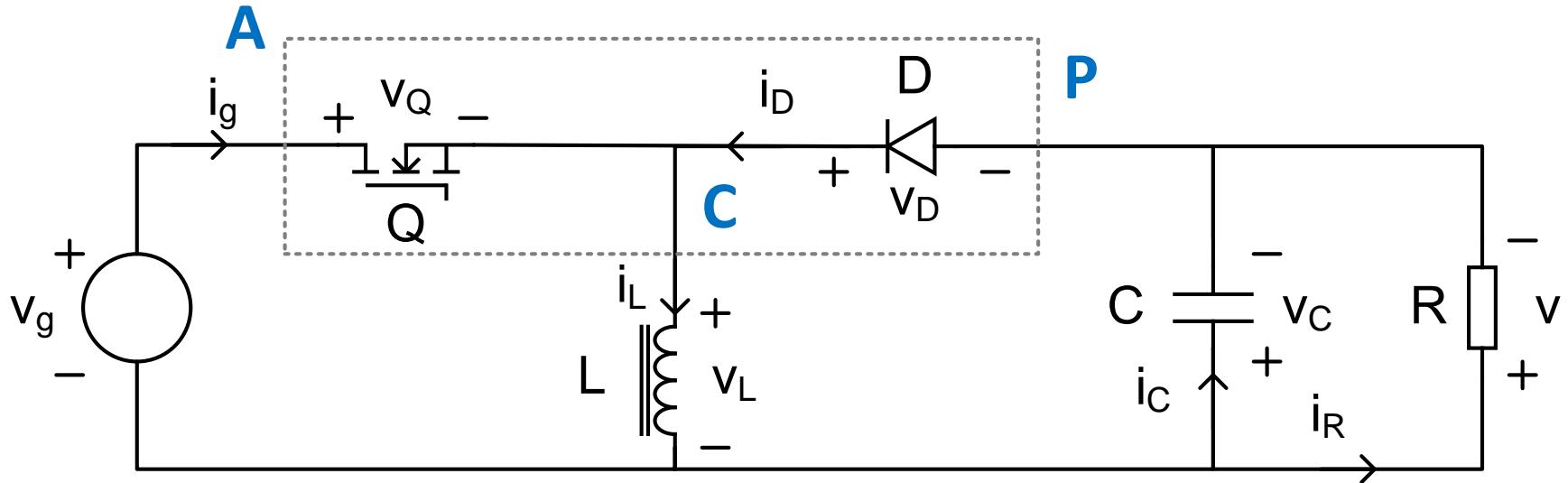


Another View Of The Average Switch Model

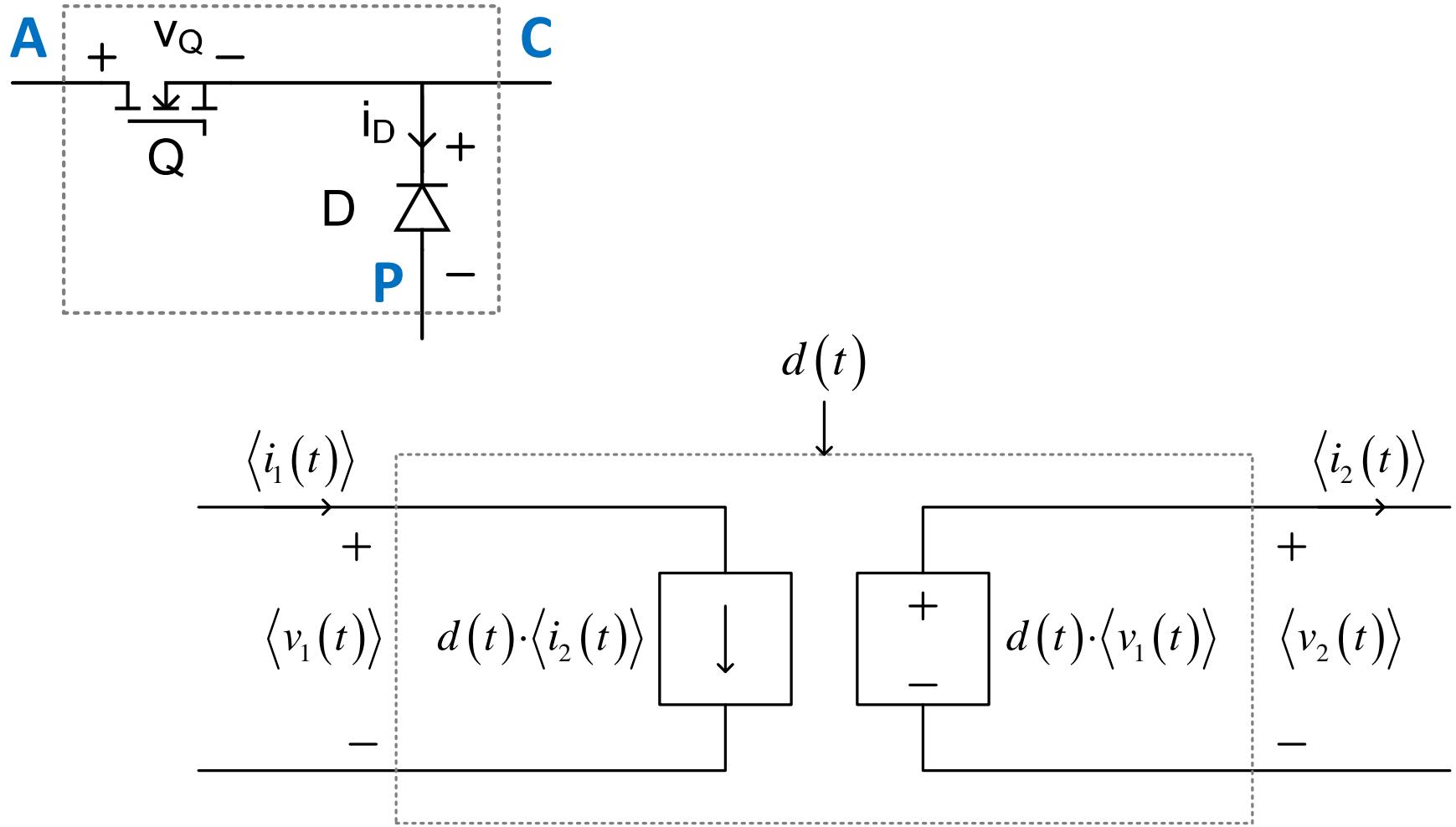


Another View Of The Average Switch Model

+

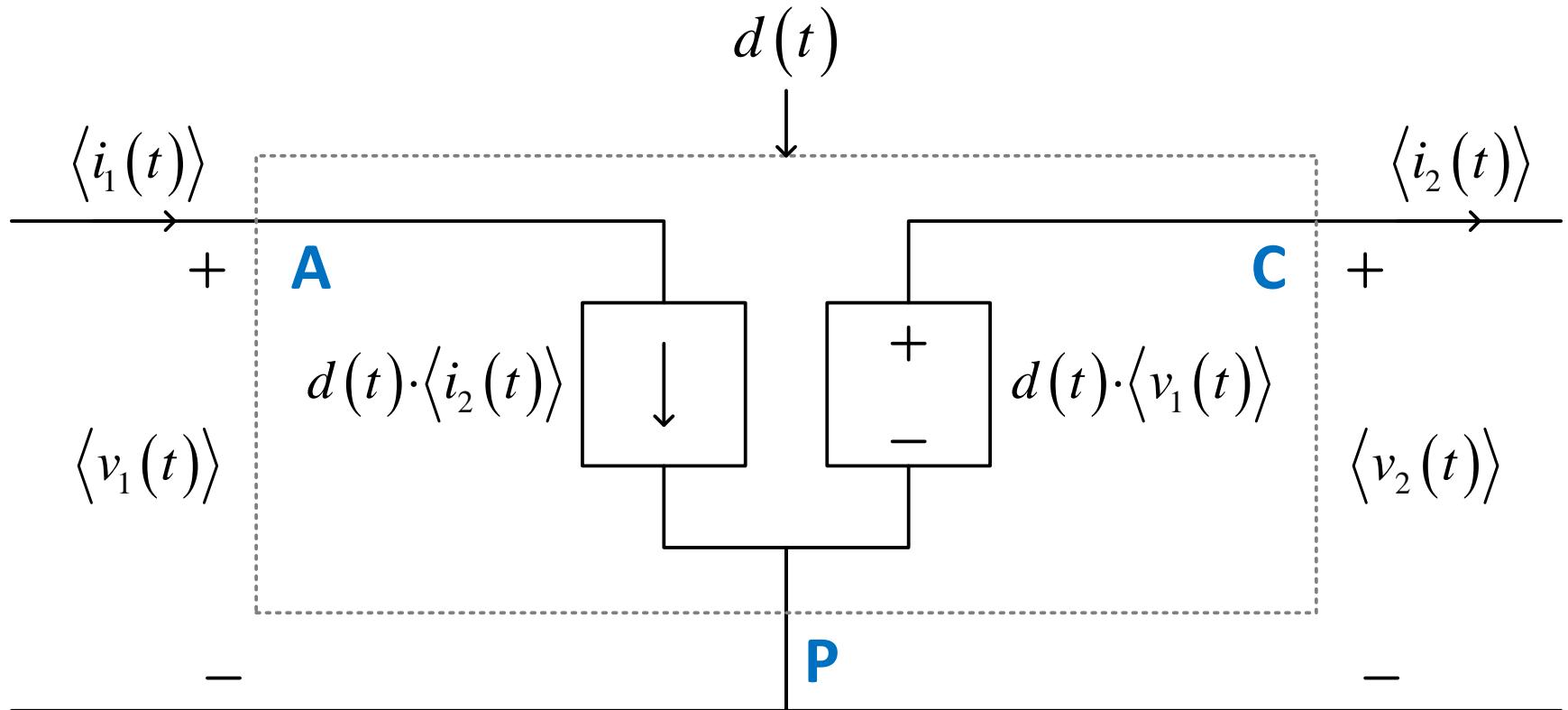

Another View Of The Average Switch Model

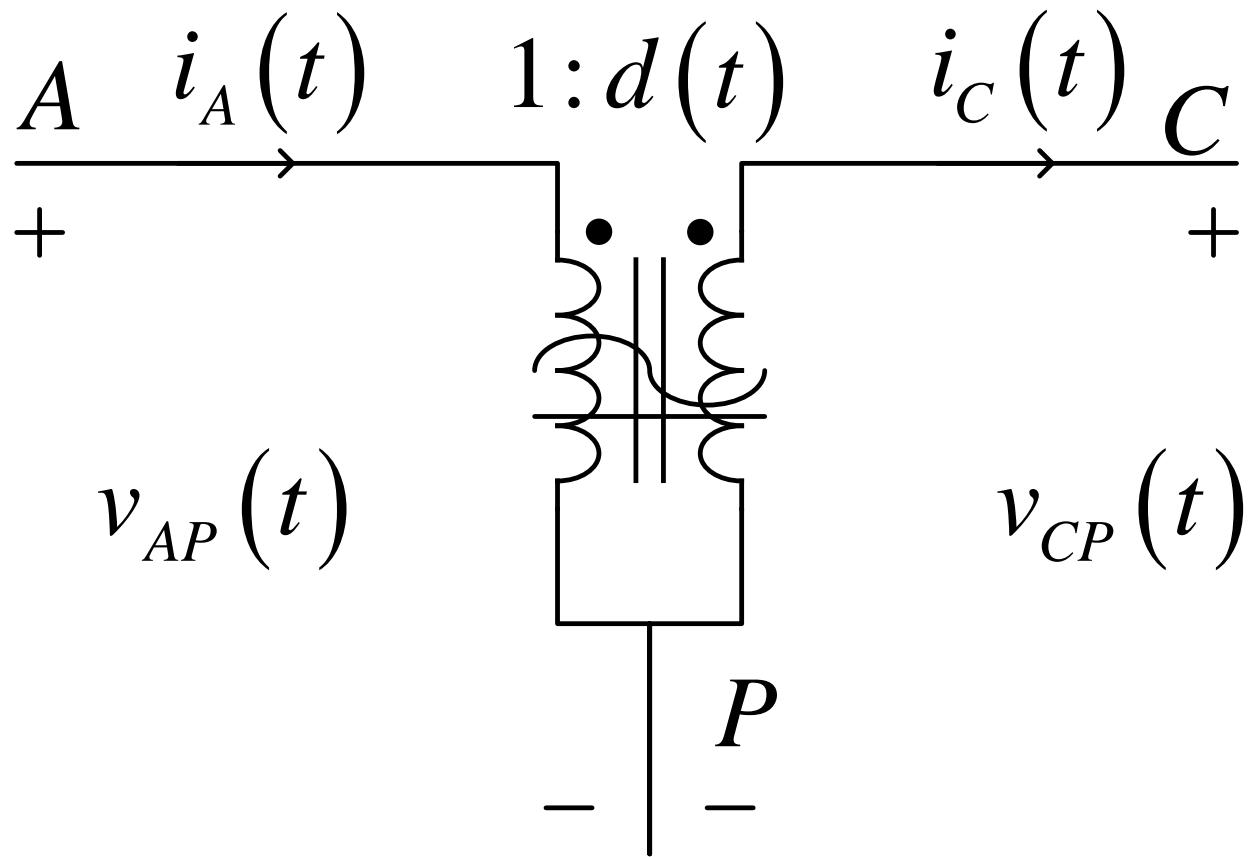

Simulating Buck Converter With Averaged Switch Model

- $F_{SWITCH} = 500 \text{ kHz}$
- $V_g = 12 \text{ Vdc}$
- $V_o = 3 \text{ Vdc}$
- $D = 0.25$
- $I_o = 3 \text{ A}$
- $R_o = 1 \Omega$
- $\Delta I_L = 20\% I_o = 0.6 \text{ A} \Rightarrow L = 7.5 \mu\text{H}$
- $C = 33 \mu\text{F}$
 - ESR = 50 mΩ
 - $F_{ZERO} = 96.5 \text{ kHz}$
 - $\Delta V_C = 9.1 \text{ mV}$
(capacitor only)
- $F_0 = 10.1 \text{ kHz}$
- $Q = 2.1 = 6.4 \text{ dB}$





LTspice Model: DC Sweep

Input Parameters (V_g , V_o_{nom} , R_o) Calculated Parameters (I_o_{nom} , D_{nom})

```
.param Vg = 12  
.param Vo_nom = 3  
.param Ro = 1
```

```
.param Dnom = (Vo_nom/Vg)  
.param Io_nom = Vo_nom/Ro
```


```
.dc VD_nom 0 0.95 0.01
```

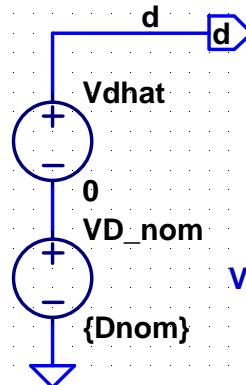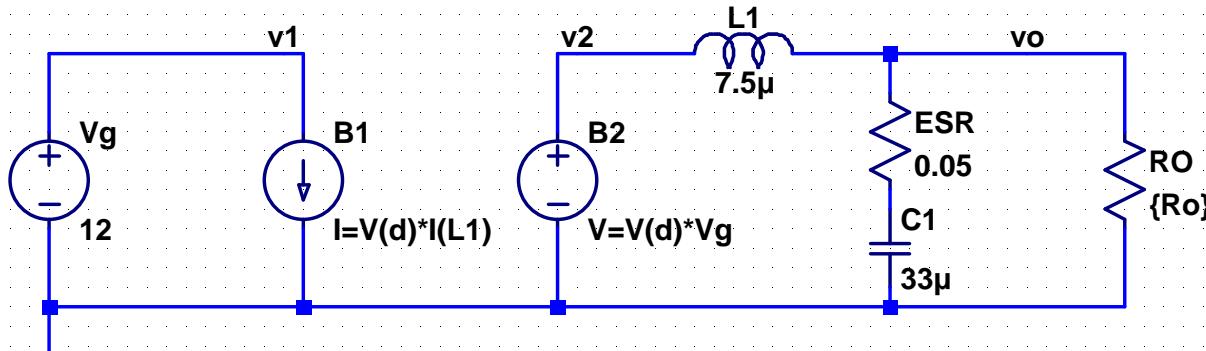

**$Vdhat$ sets the variation around the dc operating point
Set to zero for dc sweep analysis**

VD_{nom} sets the dc duty cycle operating point

LTspice Model: DC Sweep

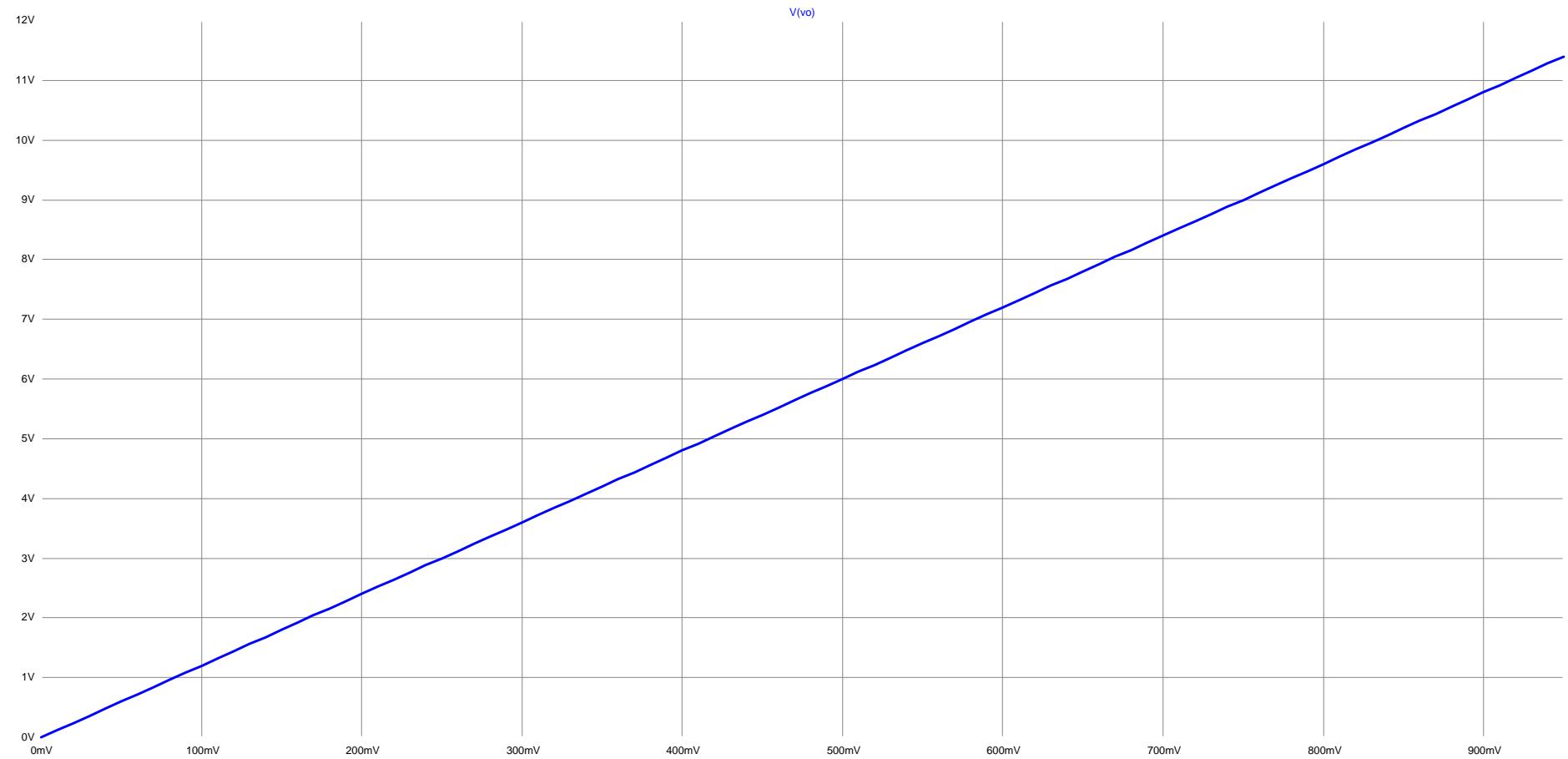



LTspice Model: Transient Response

Input Parameters (V_g , V_o_{nom} , R_o) Calculated Parameters (I_o_{nom} , D_{nom})

```
.param Vg = 12  
.param Vo_nom = 3  
.param Ro = 1
```

```
.param Dnom = (Vo_nom/Vg)  
.param Io_nom = Vo_nom/Ro
```


```
.tran 5m
```

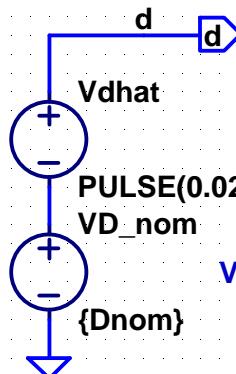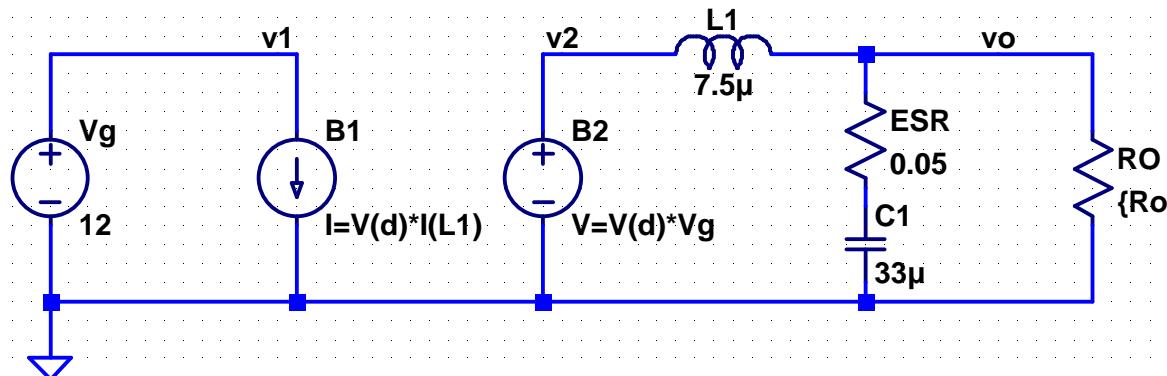

V_dhat sets the variation around the dc operating point

VD_{nom} sets the dc duty cycle operating point

LTspice Transient Simulation

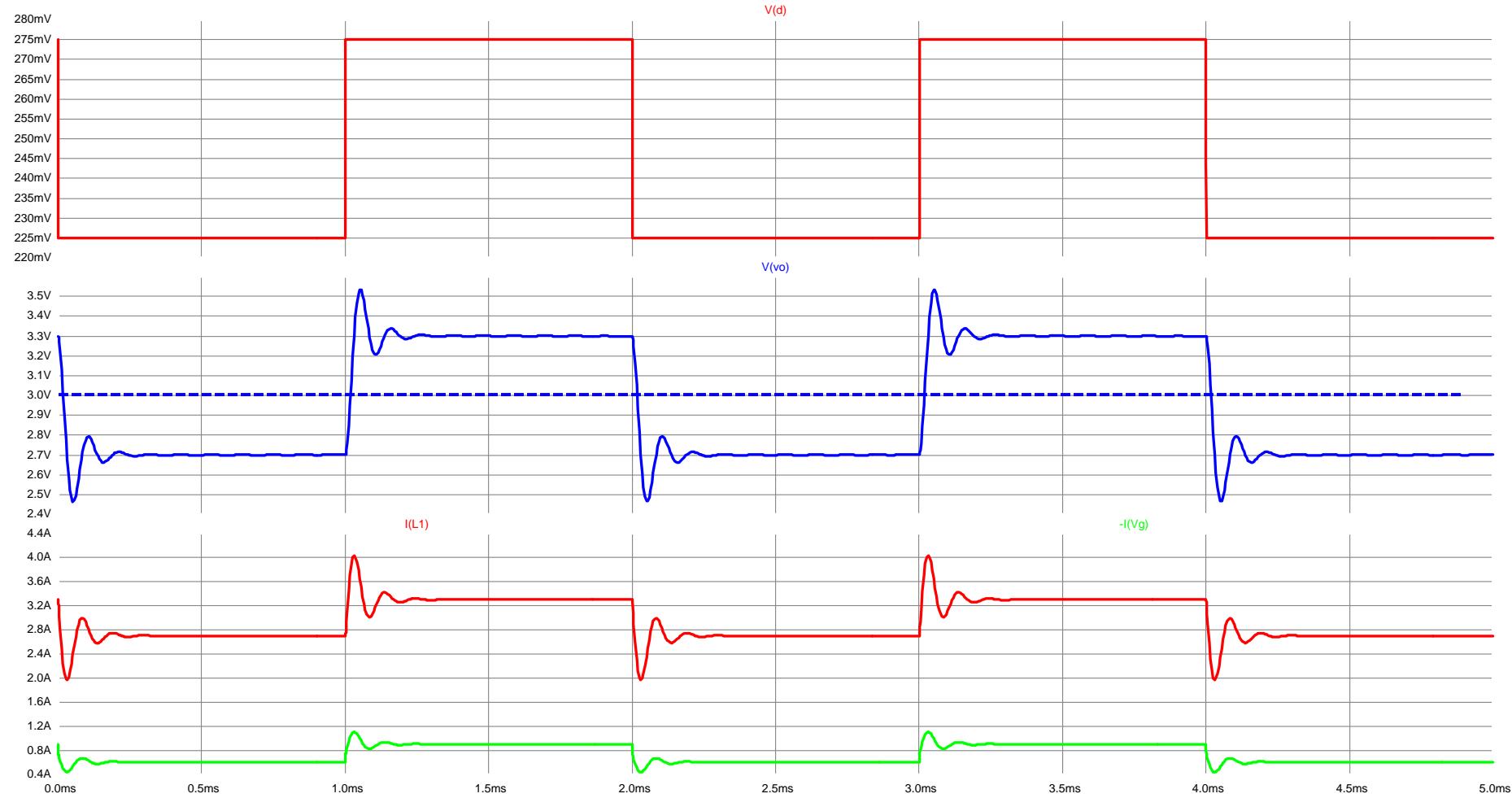


LTspice Model: Plotting G_{vd}

Input Parameters (Vg , Vo_nom , Ro) Calculated Parameters (Io_nom , $Dnom$)


```
param Vg = 12  
param Vo_nom = 3  
param Ro = 1
```

```
.param Dnom = (Vo_nom/Vg)  
.param Io_nom = Vo_nom/Ro
```

```
.ac dec 50 25 250k
```

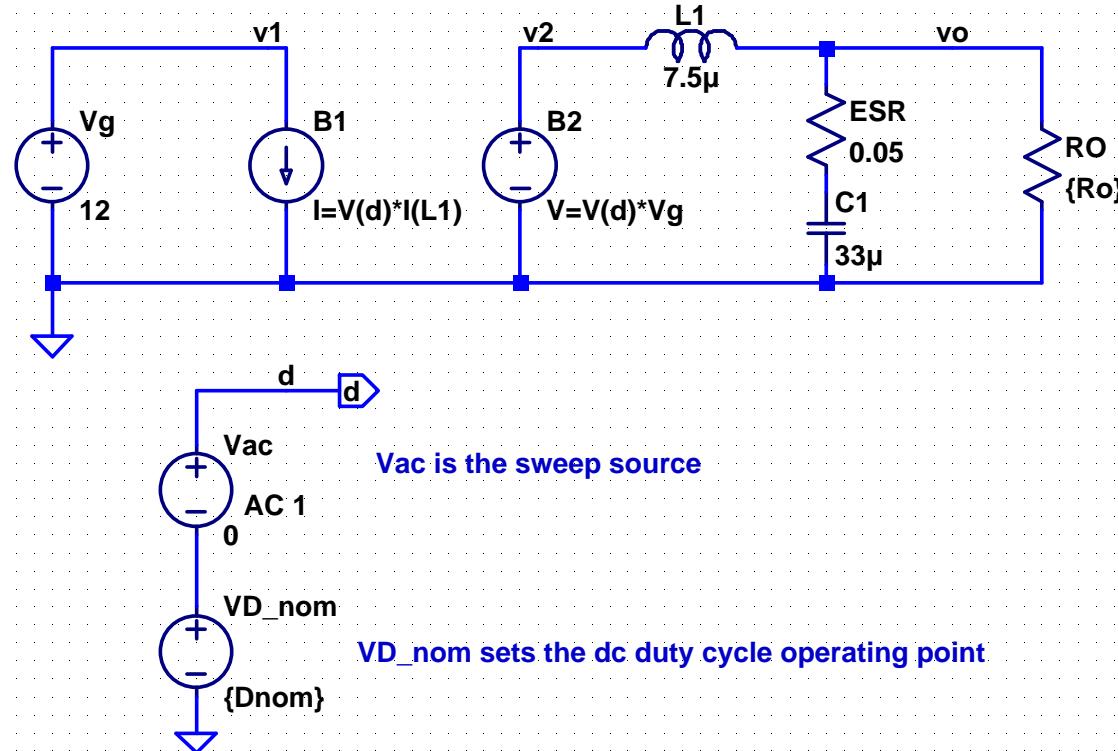


LTspice Model

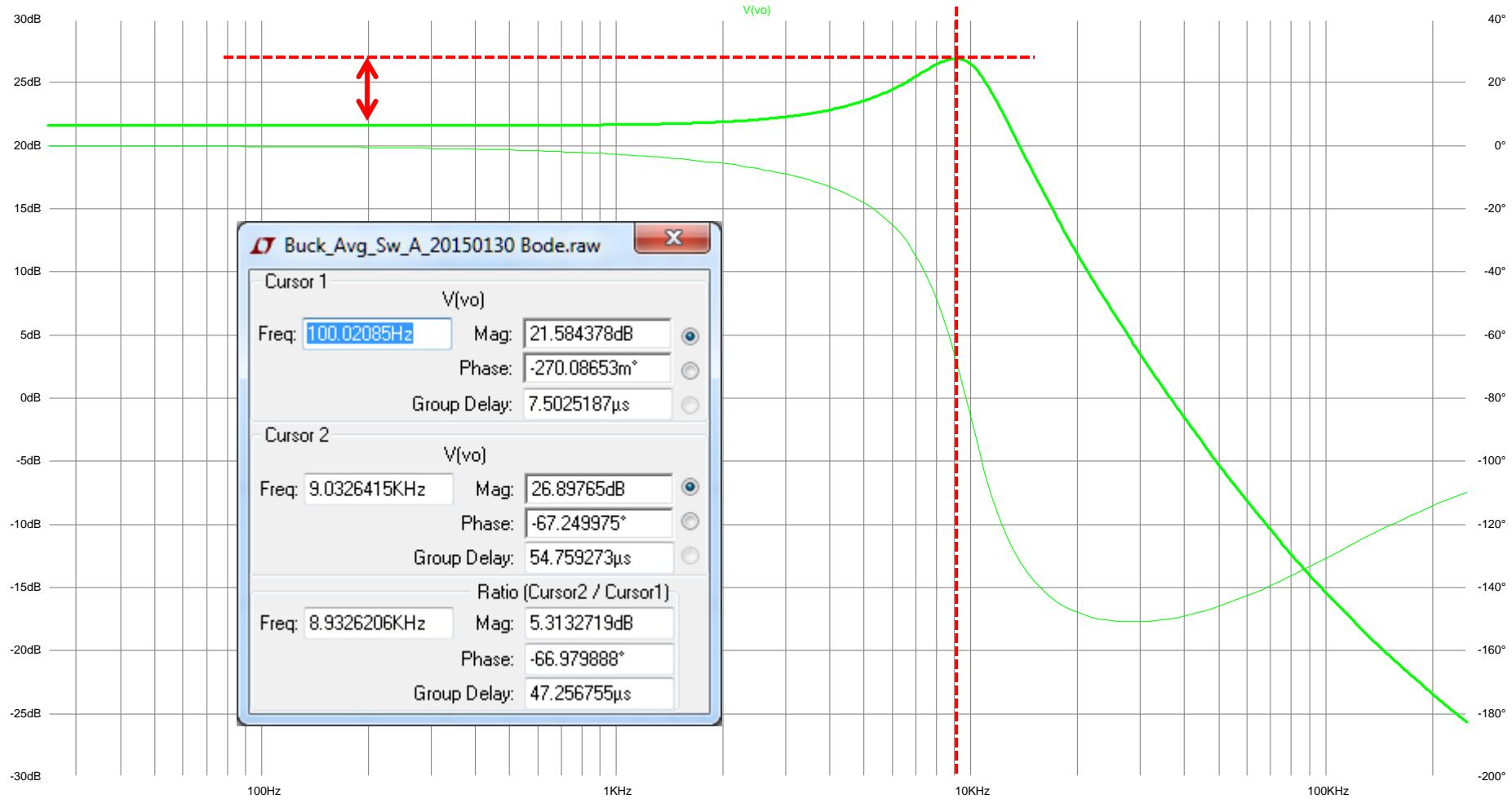


Flyback Simulation With Average Switch Model


+

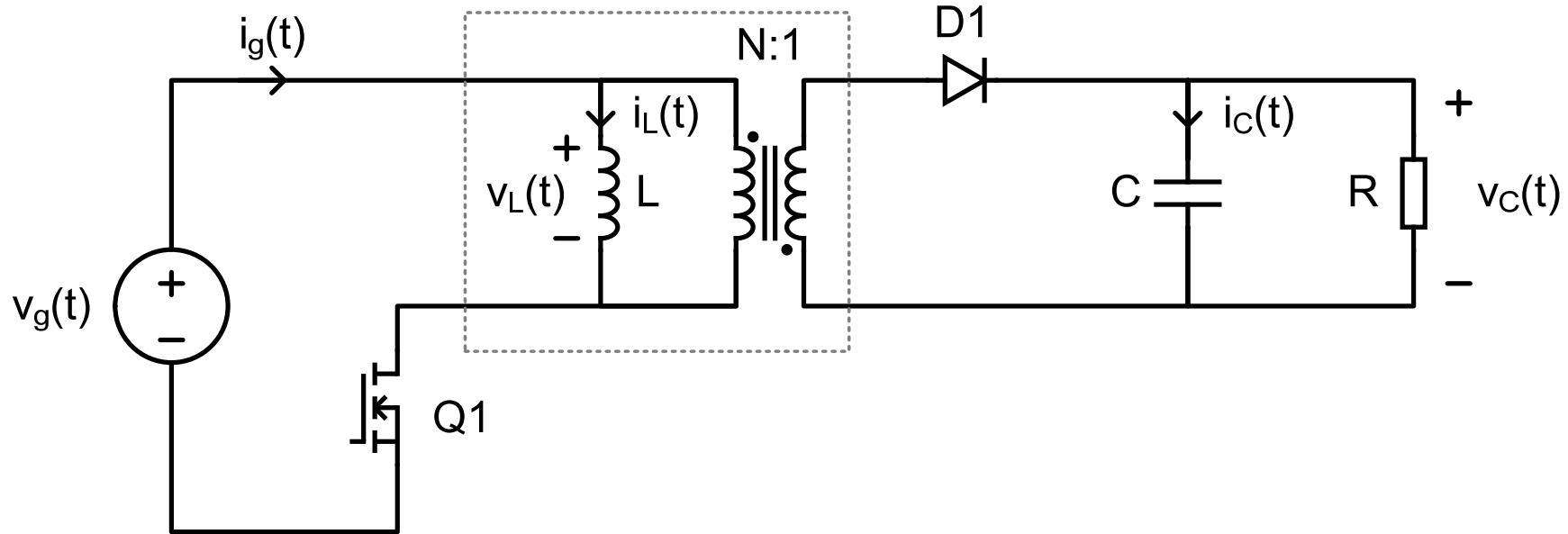

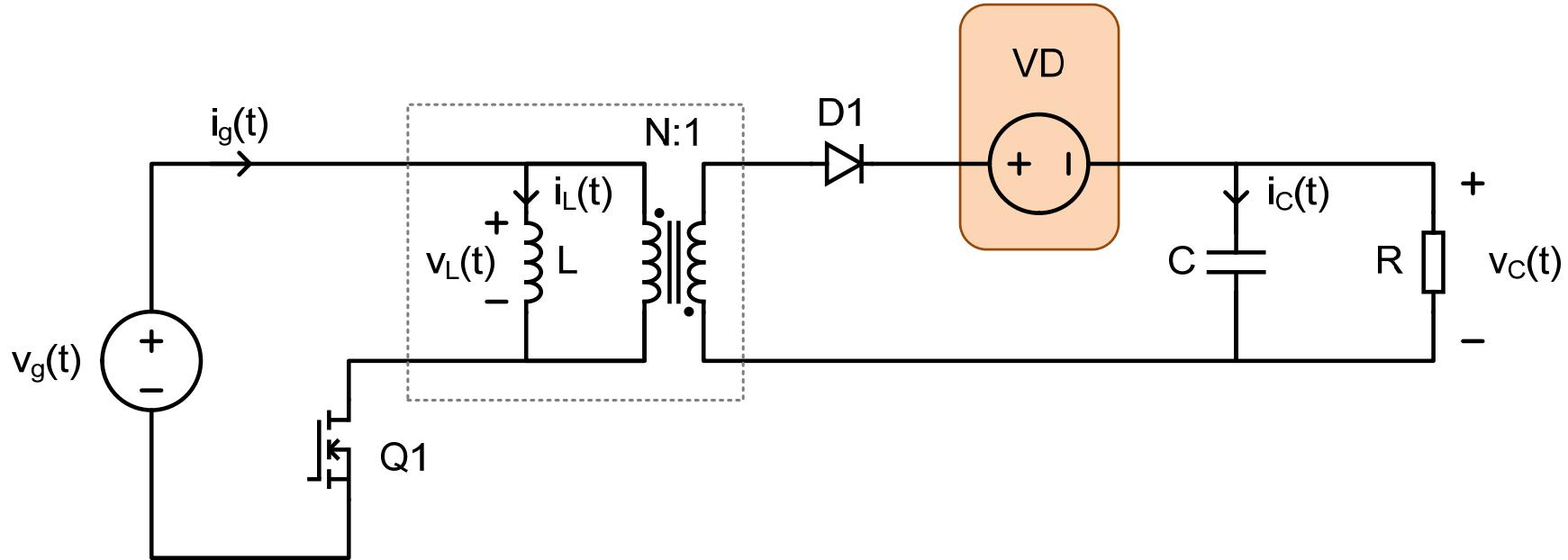
Flyback Simulation With Average Switch Model



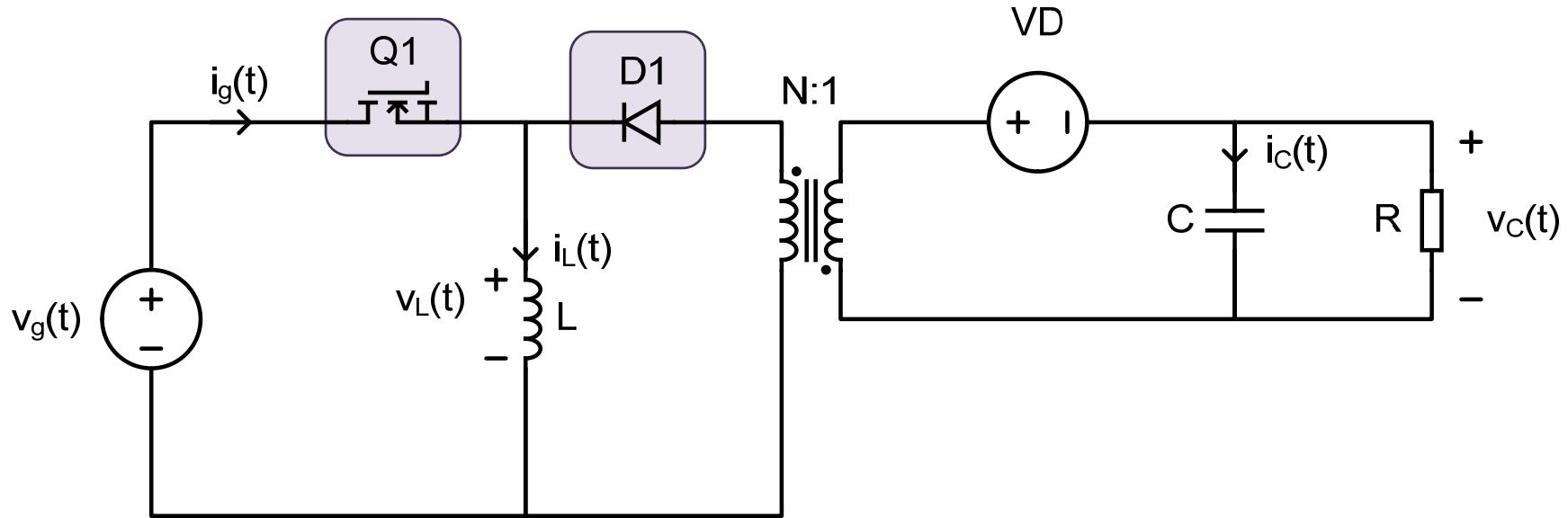
Flyback Simulation With Average Switch Model



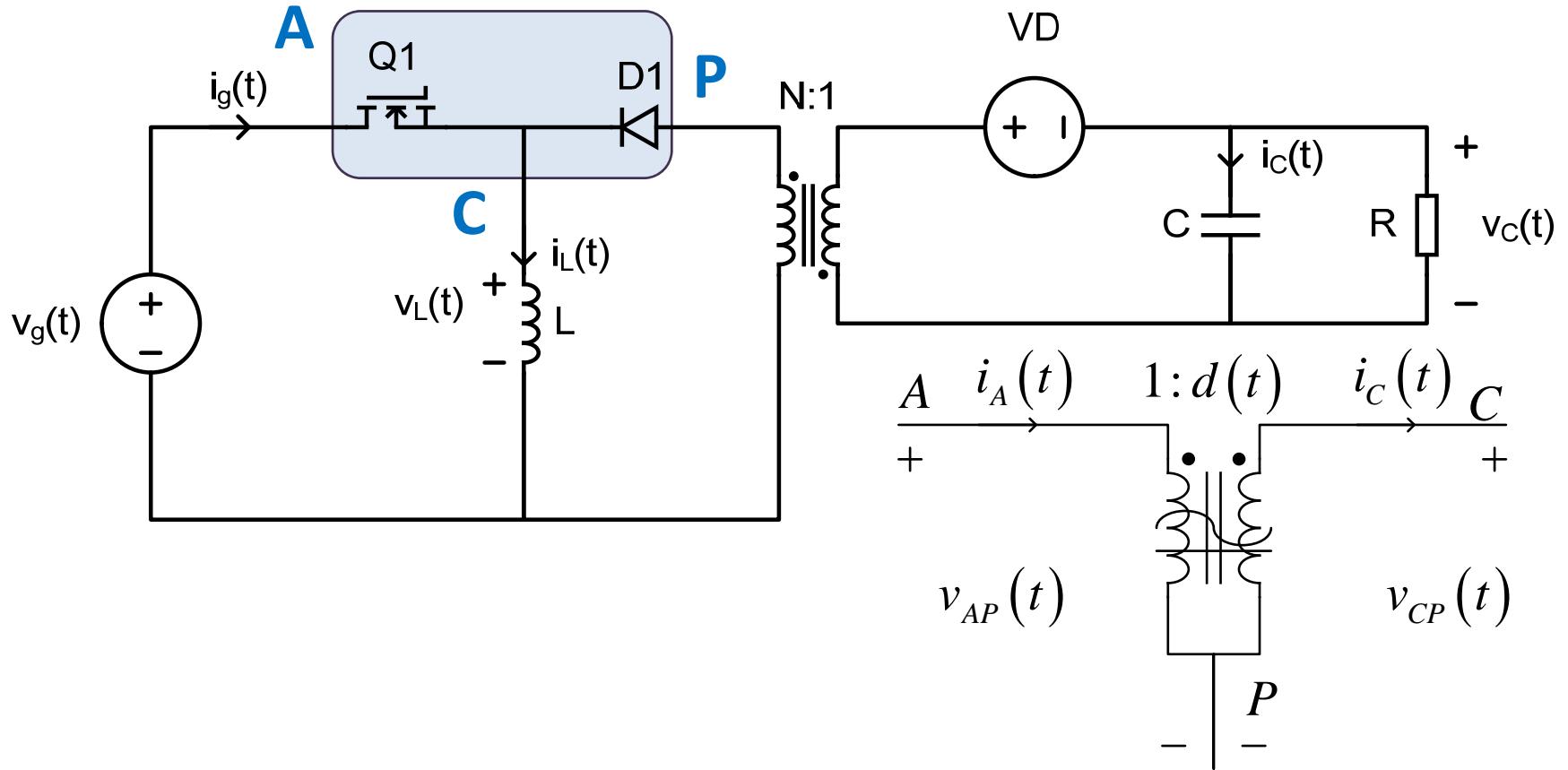
Flyback Simulation With Average Switch Model



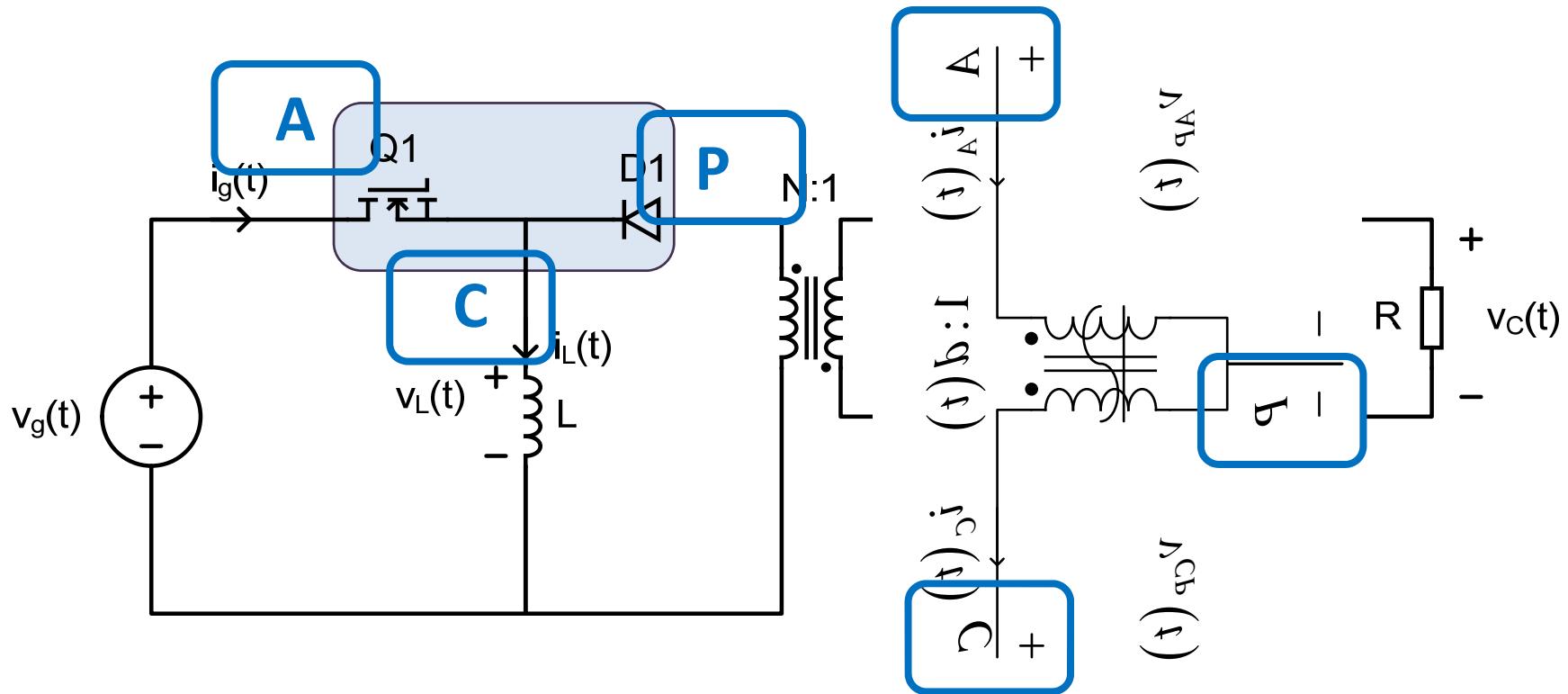Flyback Simulation With Average Switch Model



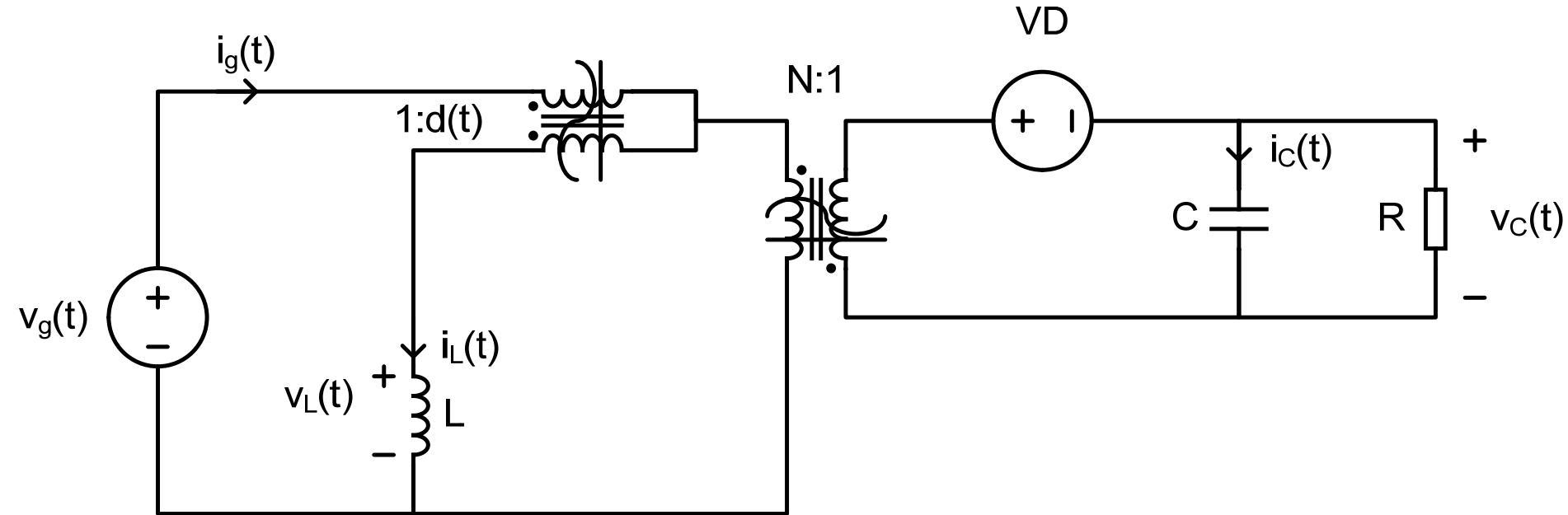
Flyback Simulation With Average Switch Model



Flyback Simulation With Average Switch Model





.IC V(Vo) = 12
.IC I(Lpri) = 0.494

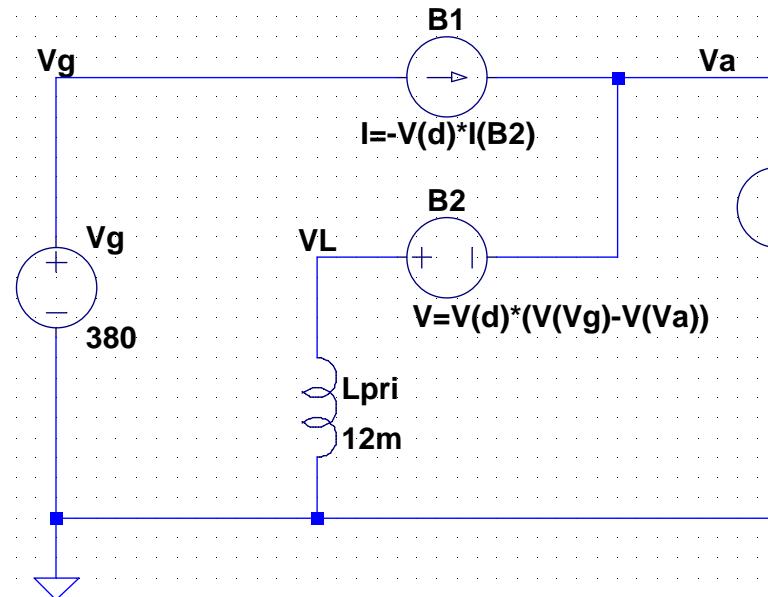

.param D0 0.2646
.param TR 11

.op

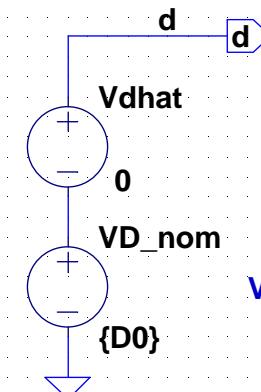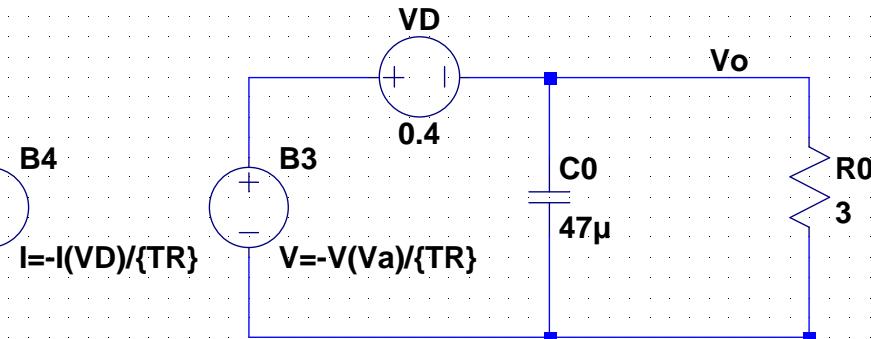

V_dhat sets the variation around the dc operating


V_D_nom sets the dc duty cycle operating point





Flyback Simulation With Average Switch Model

.IC V(Vo) = 12
.IC I(Lpri) = 0.494

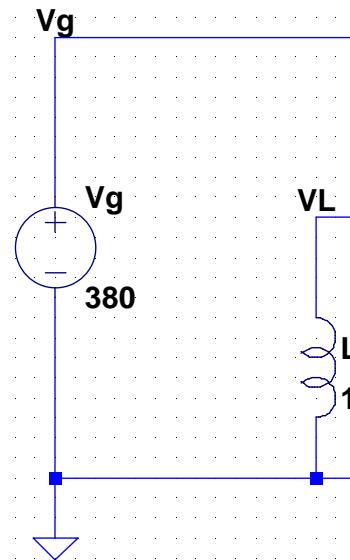

```
.param D0 0.2646  
.op  
.param TR 11
```

D * D:\Clients\APEC 2015\Seminar - Averaging\SPICE Flyback Average Model\Flyback Average Model 2015...

--- Operating Point ---		
V(vg):	380	voltage
V(va):	-136.4	voltage
V(vl):	0.239502	voltage
V(n001):	12.4	voltage
V(vo):	12	voltage
V(d):	0.2646	voltage
V(n002):	0.2646	voltage
I(B4):	-0.363288	device_current
I(B3):	-3.99616	device_current
I(B2):	-0.494	device_current
I(B1):	0.130712	device_current
I(C0):	5.64e-016	device_current
I(Lpri):	0.494	device_current
I(R0):	4	device_current
I(Vd):	3.99616	device_current
I(Vd_nom):	0	device_current
I(Vdhat):	0	device_current
I(Vg):	-0.130712	device_current

{D0}




Flyback Simulation With Average Switch Model




*.IC V(Vo) = 12
 *.IC I(Lpri) = 0.494

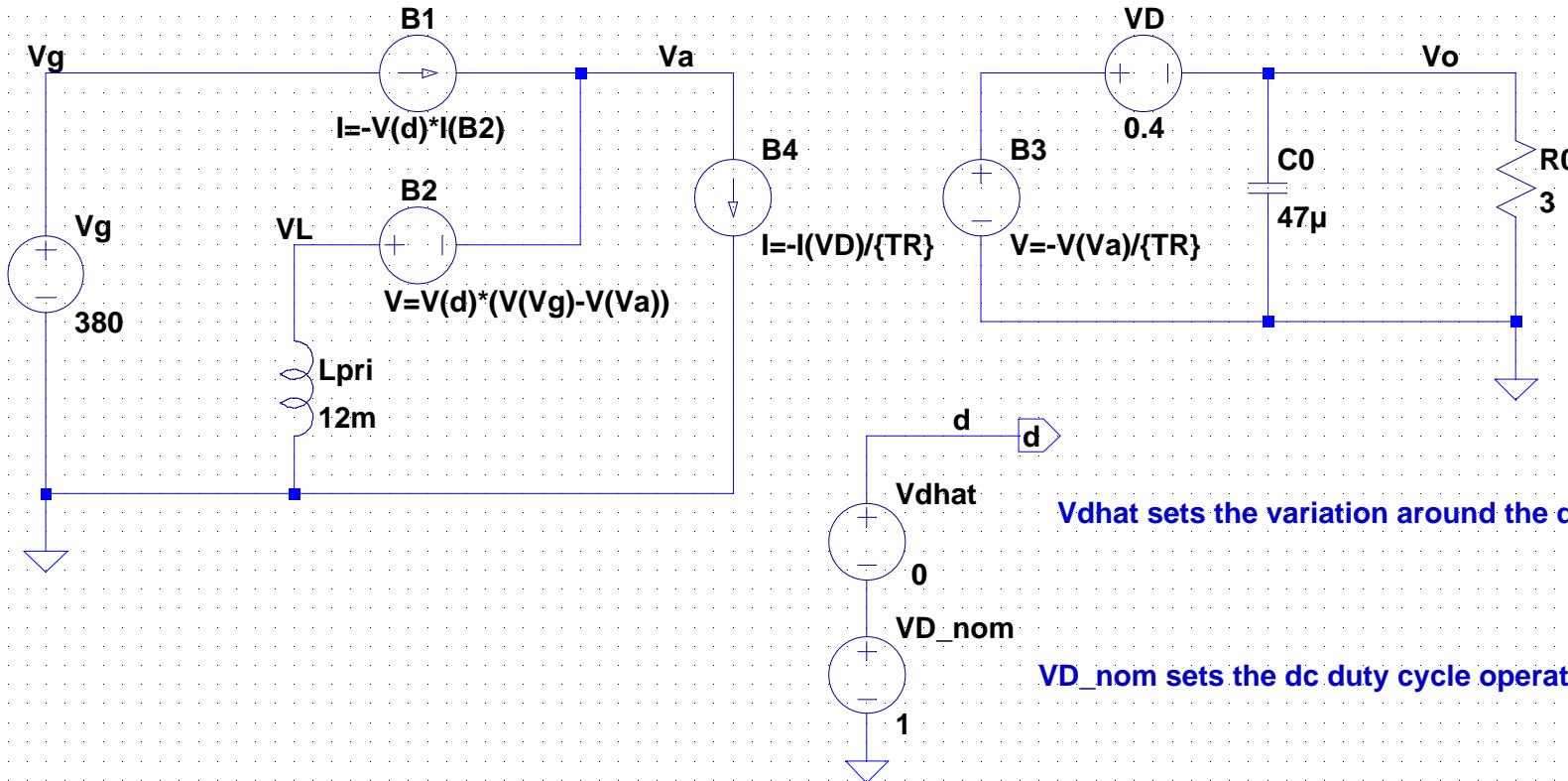*.param D0 0
 .param TR 11
 .dc VD_nom 0.0 0.95 0.025





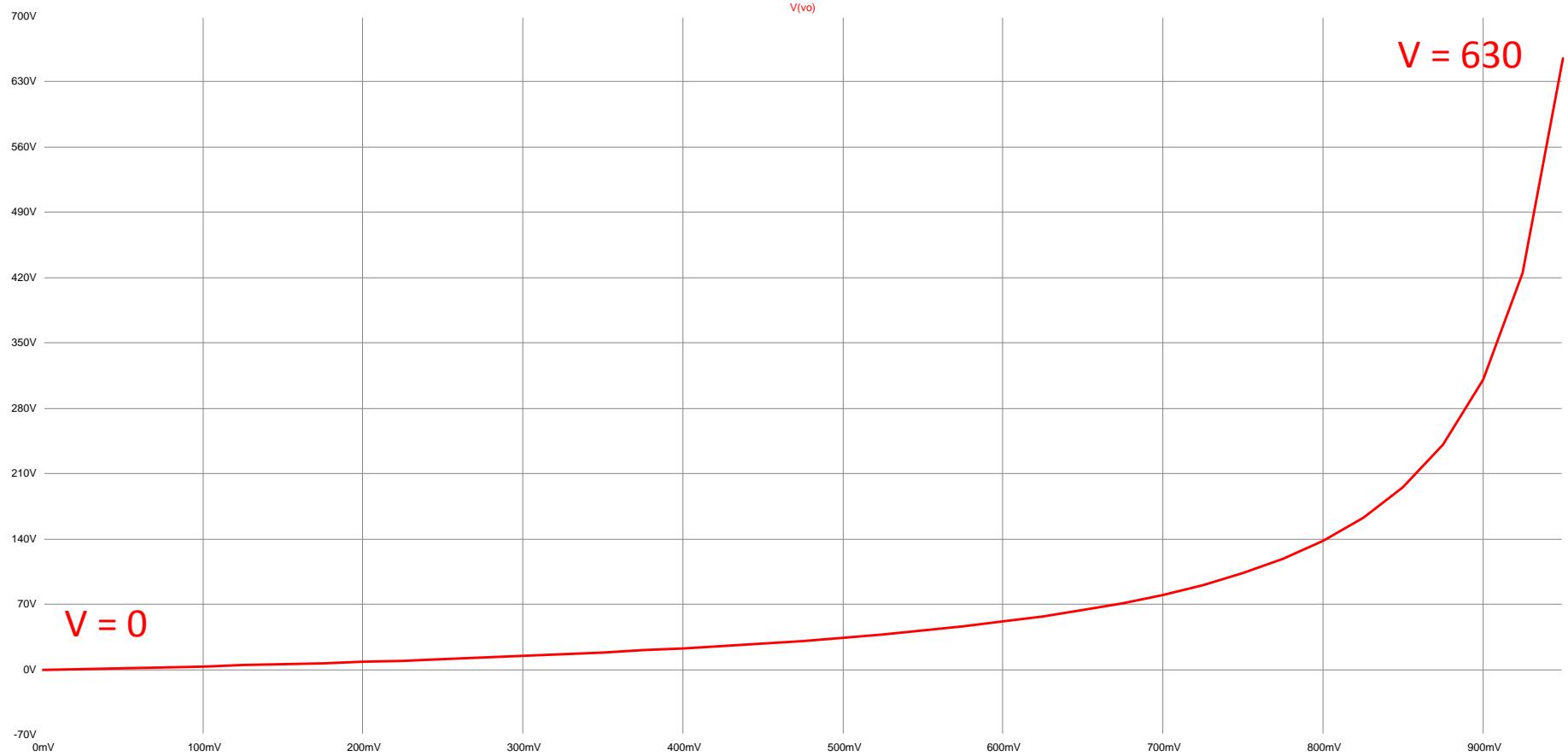Flyback Simulation With Average Switch Model



D = 0

D = 0.95



Flyback Simulation With Average Switch Model



.IC V(Vo) = 12
.IC I(Lpri) = 0.494

.param D0 0.2646
.param TR 11


.tran 20m

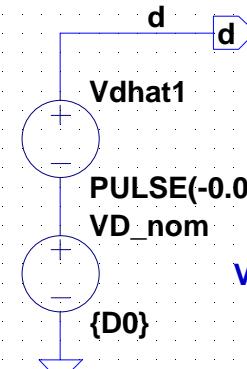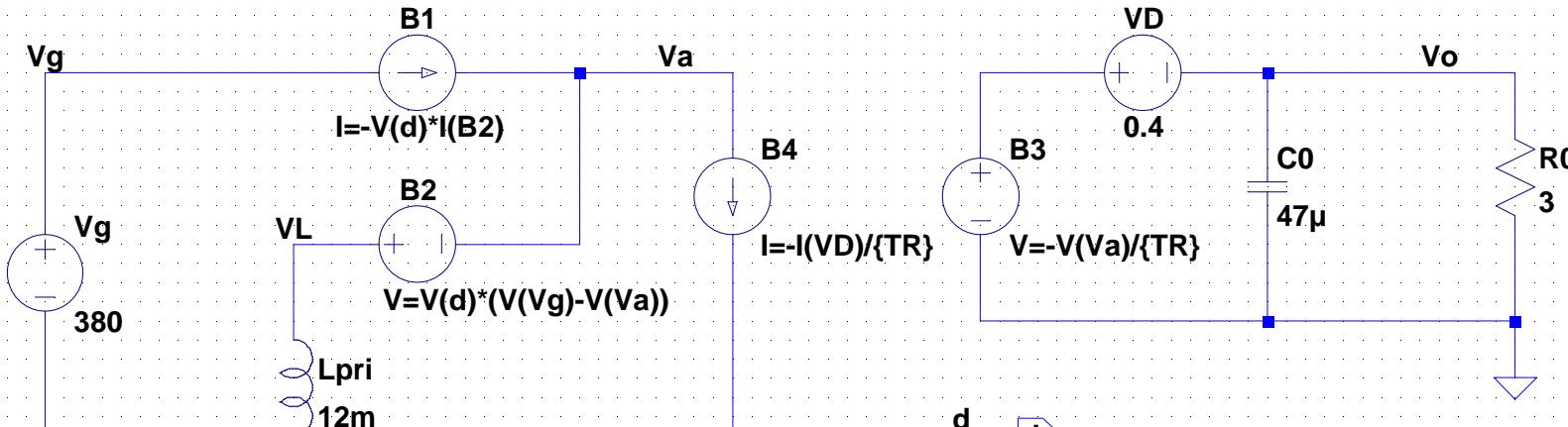

Vdhat sets the variation around the dc operating point

VD_nom sets the dc duty cycle operating point

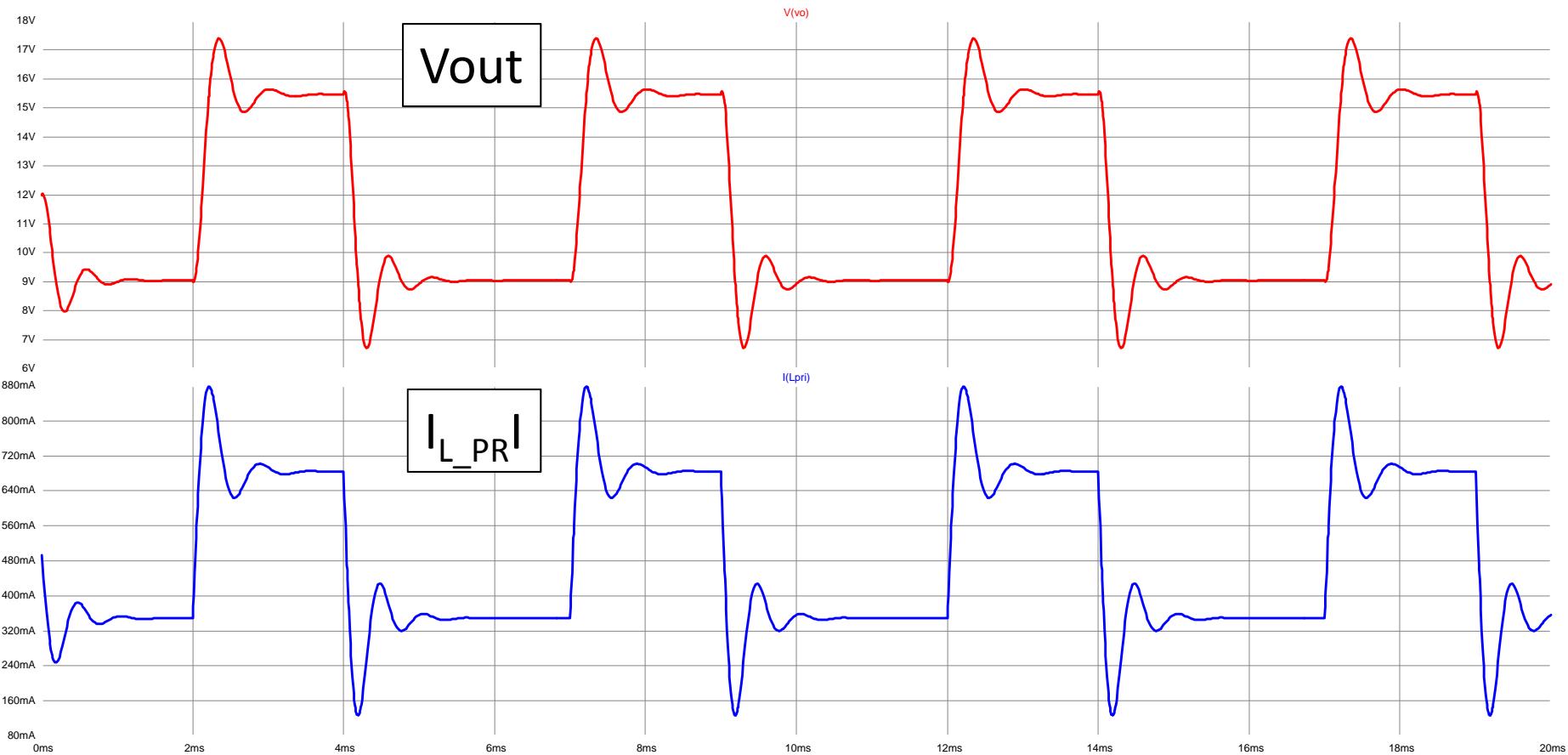
Flyback Simulation With Average Switch Model







Flyback Simulation With Average Switch Model

.IC V(Vo) = 12
.IC I(Lpri) = 0.494

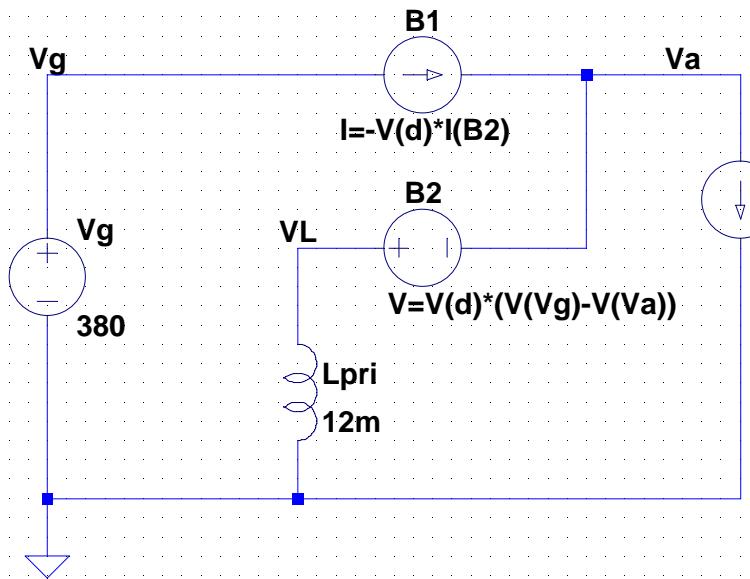

.param D0 0.2646
.param TR 11

.ac dec 100 10 100k

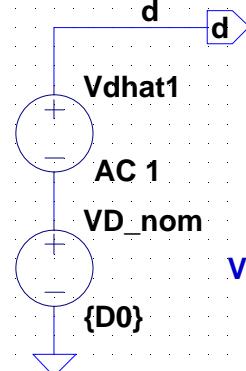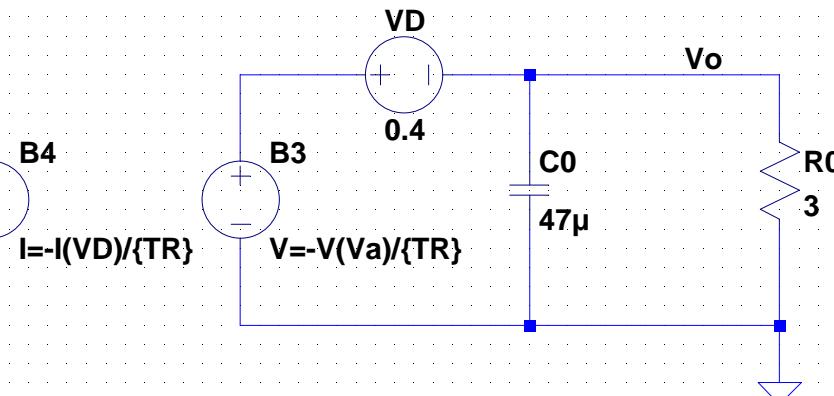


$Vdhat$ sets the variation around the dc operating point

VD_nom sets the dc duty cycle operating point





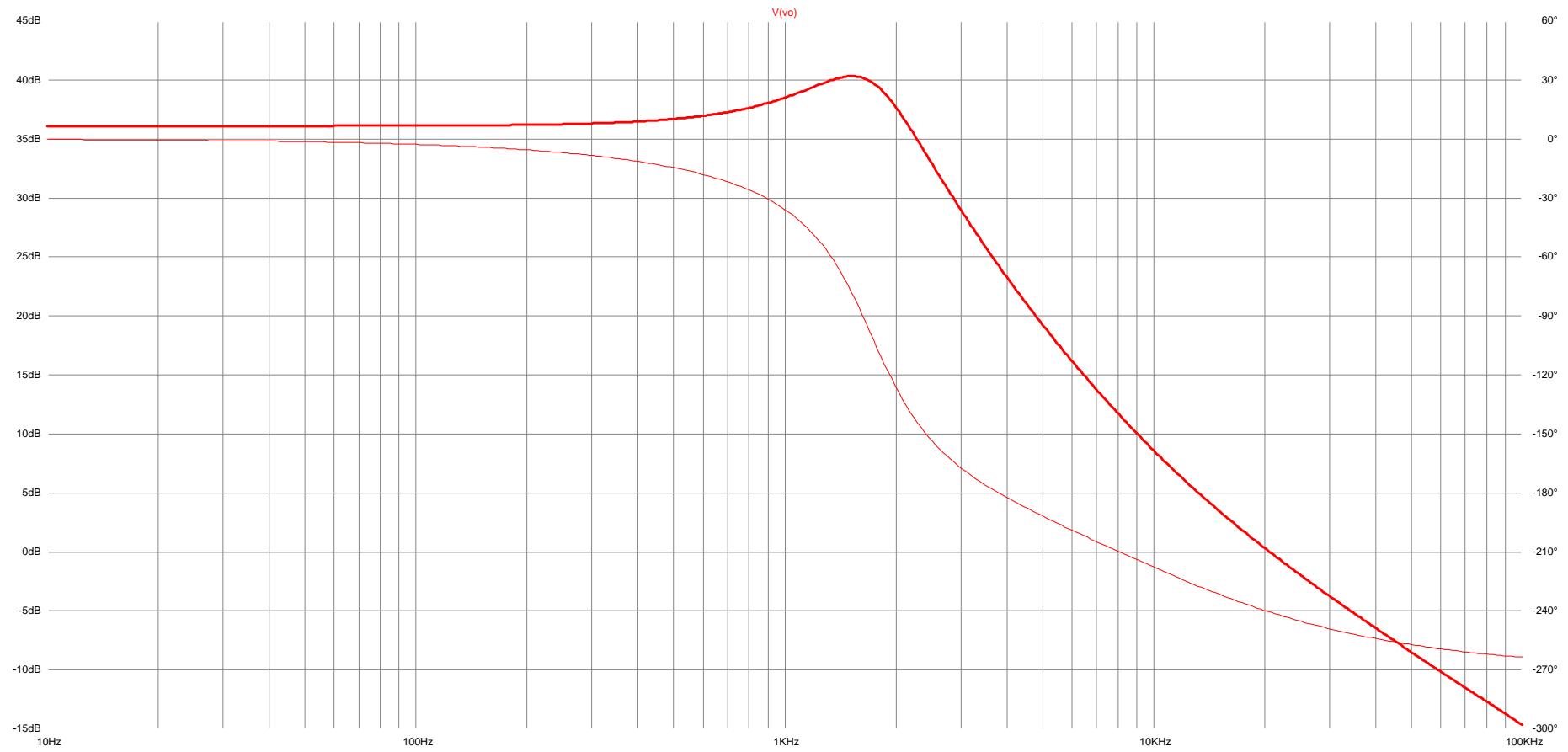Flyback Simulation With Average Switch Model





Flyback Simulation With Average Switch Model



*.IC V(Vo) = 12
 *.IC I(Lpri) = 0.494

*.param D0 0
 .param TR 11


.dc VD_nom 0.0 0.99 0.005

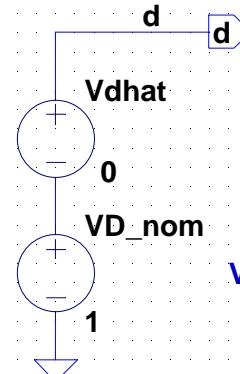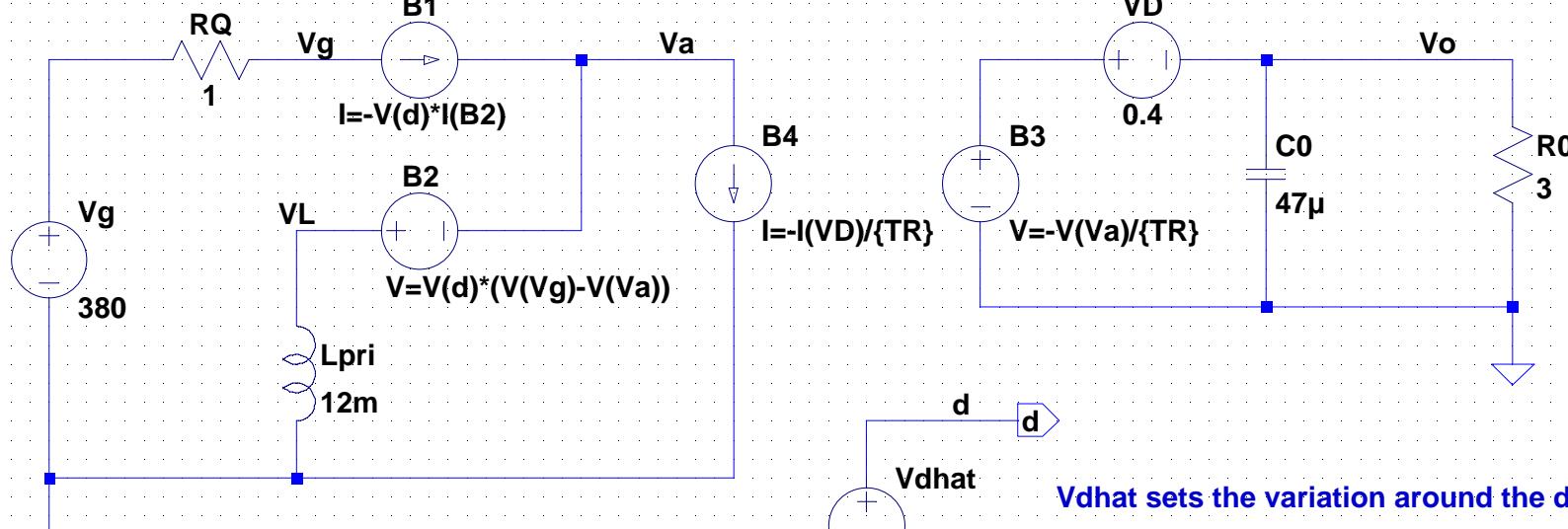

$V_{d\hat{}}$ sets the variation around the dc operating point

VD_{nom} sets the dc duty cycle operating point

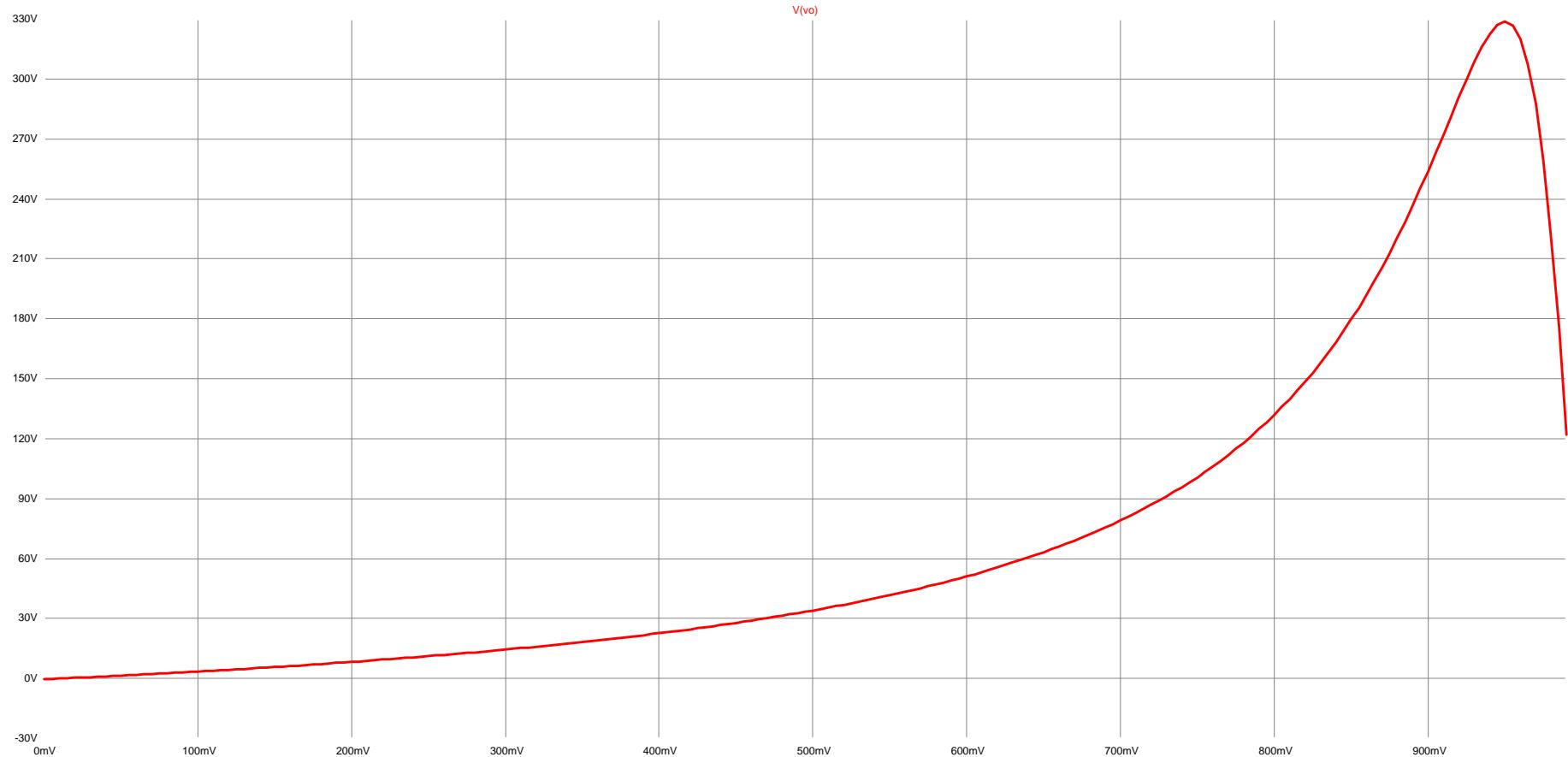
Flyback Simulation With Average Switch Model



D = 0

D = 0.99

Averaged Switch Small Signal Model

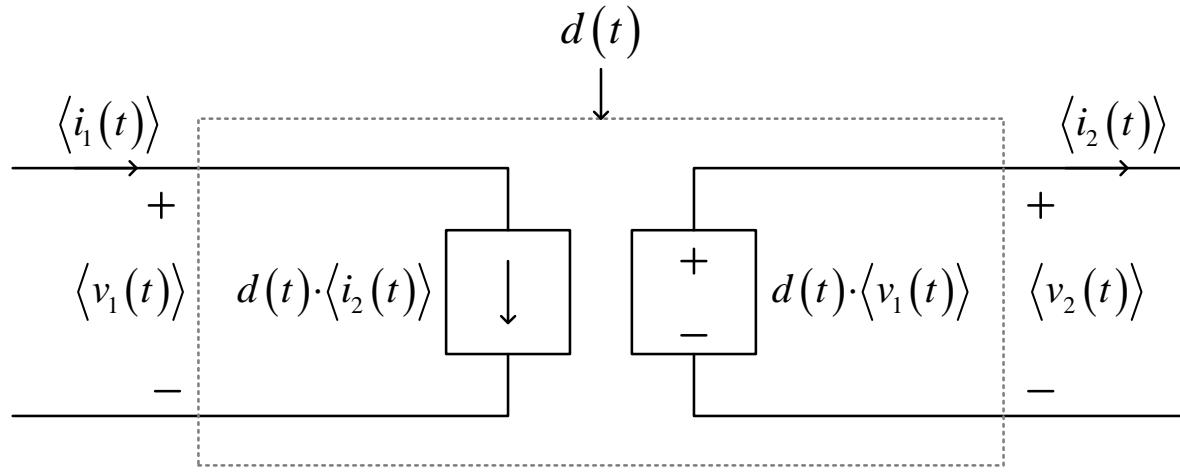

$$\langle v_2(t) \rangle = d(t) \cdot \langle v_1(t) \rangle$$

$$\langle i_1(t) \rangle = d(t) \cdot \langle i_2(t) \rangle$$

$$\langle v_1(t) \rangle = V_1 + \hat{v}_1(t)$$

$$\langle v_2(t) \rangle = V_2 + \hat{v}_2(t)$$

$$\langle i_1(t) \rangle = I_1 + \hat{i}_1(t)$$

$$\langle i_2(t) \rangle = I_2 + \hat{i}_2(t)$$

$$d(t) = D + \hat{d}(t)$$

Averaged Switch Small Signal Model

$$\langle v_2(t) \rangle = d(t) \cdot \langle v_1(t) \rangle$$

$$\begin{aligned} V_2 + \hat{v}_2(t) &= (D + \hat{d}(t)) \cdot (V_1 + \hat{v}_1(t)) \\ &= D \cdot V_1 + D \cdot \hat{v}_1(t) + V_1 \cdot \hat{d}(t) + \hat{d}(t) \cdot \hat{v}_1(t) \end{aligned}$$

$$\hat{d}(t) \cdot \hat{v}_1(t) \approx 0$$

$$\begin{aligned} V_2 + \hat{v}_2(t) &= D \cdot V_1 + D \cdot \hat{v}_1(t) + V_1 \cdot \hat{d}(t) \\ &= D \cdot (V_1 + \hat{v}_1(t)) + V_1 \cdot \hat{d}(t) \end{aligned}$$

Discard Higher
Order Nonlinear
Terms

DC And Small Signal Terms!

Averaged Switch Small Signal Model

$$\langle i_1(t) \rangle = d(t) \cdot \langle i_2(t) \rangle$$

$$\begin{aligned} I_1 + \hat{i}_1(t) &= (D + \hat{d}(t)) \cdot (I_2 + \hat{i}_2(t)) \\ &= D \cdot I_2 + D \cdot \hat{i}_2(t) + I_2 \cdot \hat{d}(t) + \hat{d}(t) \cdot \hat{i}_2(t) \end{aligned}$$


$$\hat{d}(t) \cdot \hat{i}_2(t) \approx 0$$

$$I_1 + \hat{i}_1(t) = D \cdot I_2 + D \cdot \hat{i}_2(t) + I_2 \cdot \hat{d}(t)$$

$$= D \cdot (I_2 + \hat{i}_2(t)) + I_2 \cdot \hat{d}(t)$$


Construct The Switch Model
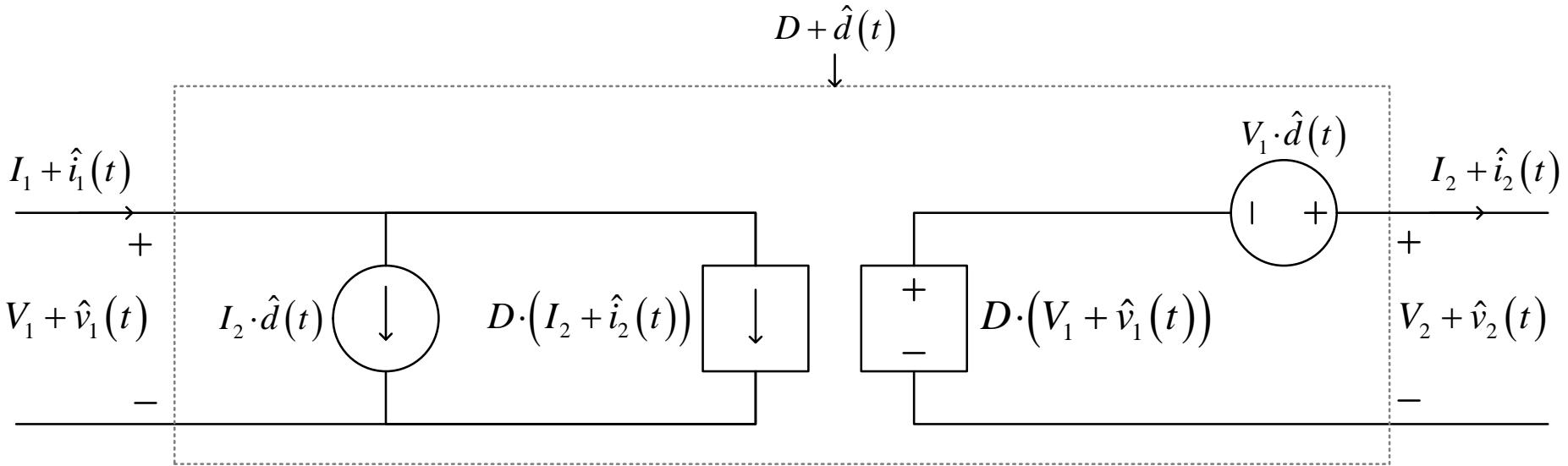
$$I_1 + \hat{i}_1(t) = D \cdot (I_2 + \hat{i}_2(t)) + I_2 \cdot \hat{d}(t) \quad V_2 + \hat{v}_2(t) = D \cdot (V_1 + \hat{v}_1(t)) + V_1 \cdot \hat{d}(t)$$




Construct The Switch Model

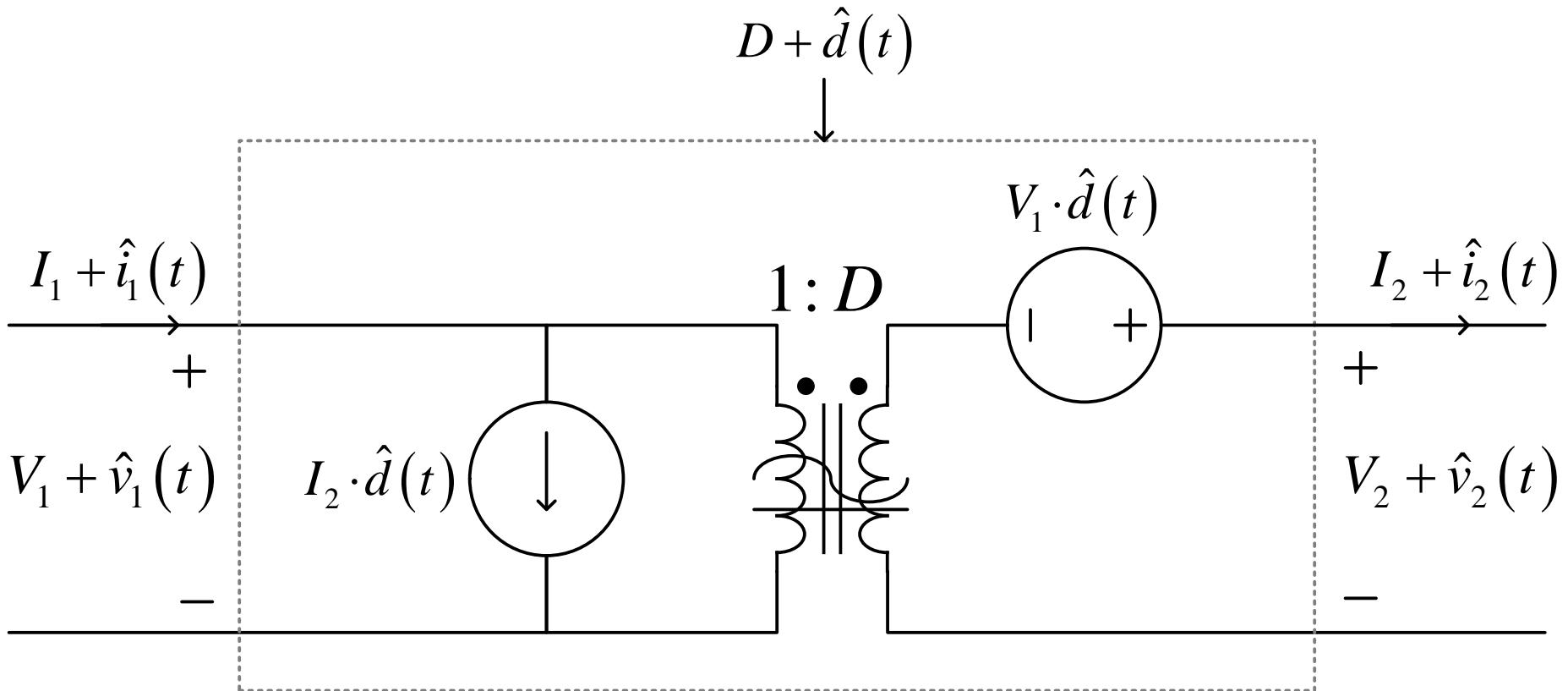
$$I_1 + \hat{i}_1(t) = D \cdot (I_2 + \hat{i}_2(t)) + I_2 \cdot \hat{d}(t) \quad V_2 + \hat{v}_2(t) = D \cdot (V_1 + \hat{v}_1(t)) + V_1 \cdot \hat{d}(t)$$



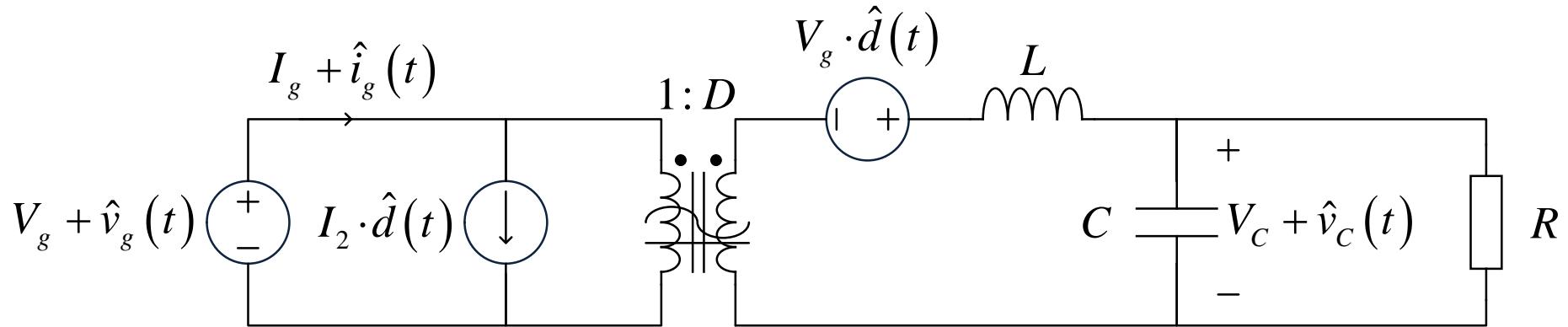Averaged Switch Small Signal Buck Converter Model




Boost Switch Model

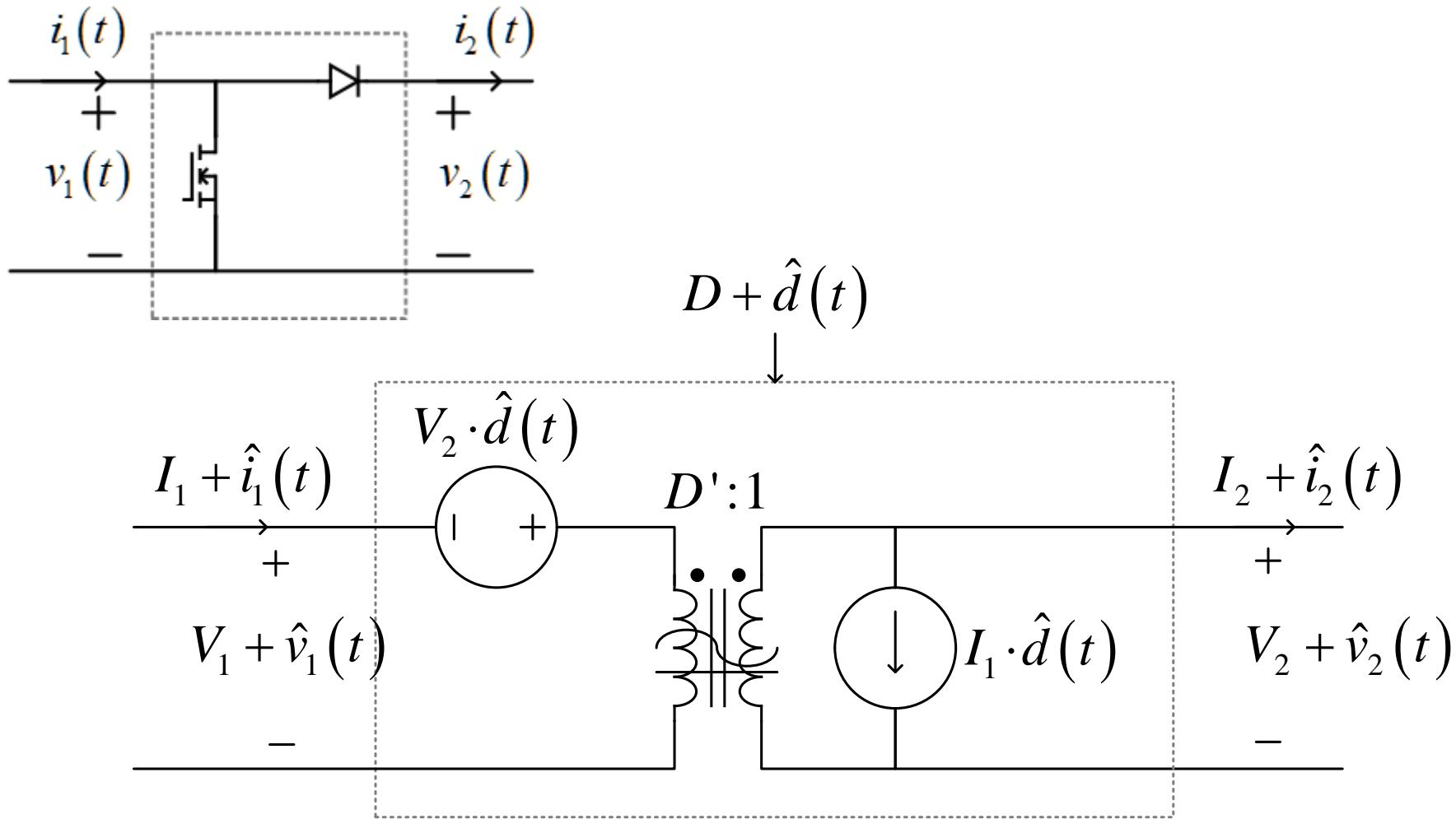


Re-drawn from "Fundamentals of Power Electronics", 2nd ed., Erickson and Maksimovic, Figure 7.50

General Two-Switch Network

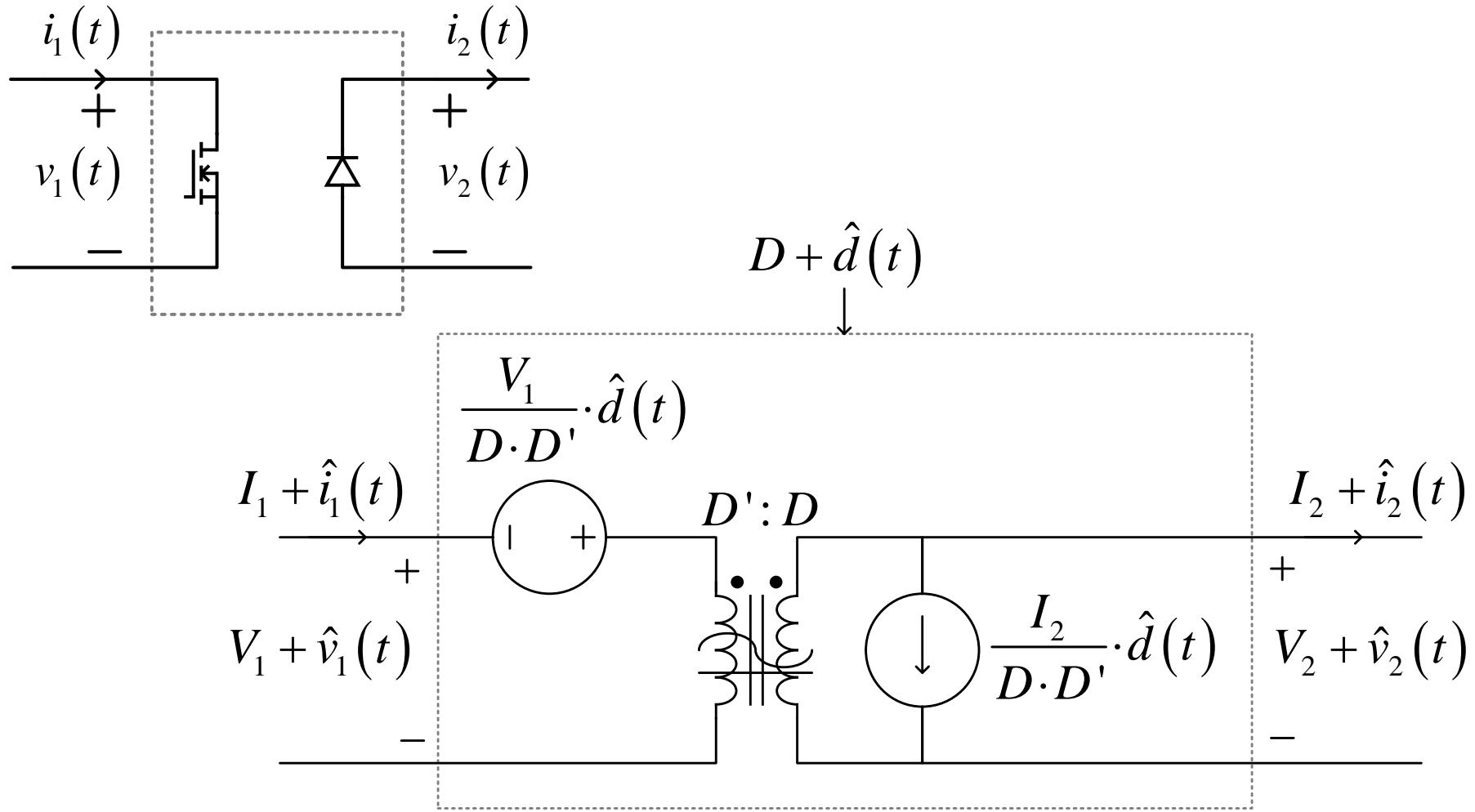


Re-drawn from "Fundamentals of Power Electronics", 2nd ed., Erickson and Maksimovic, Figure 7.50

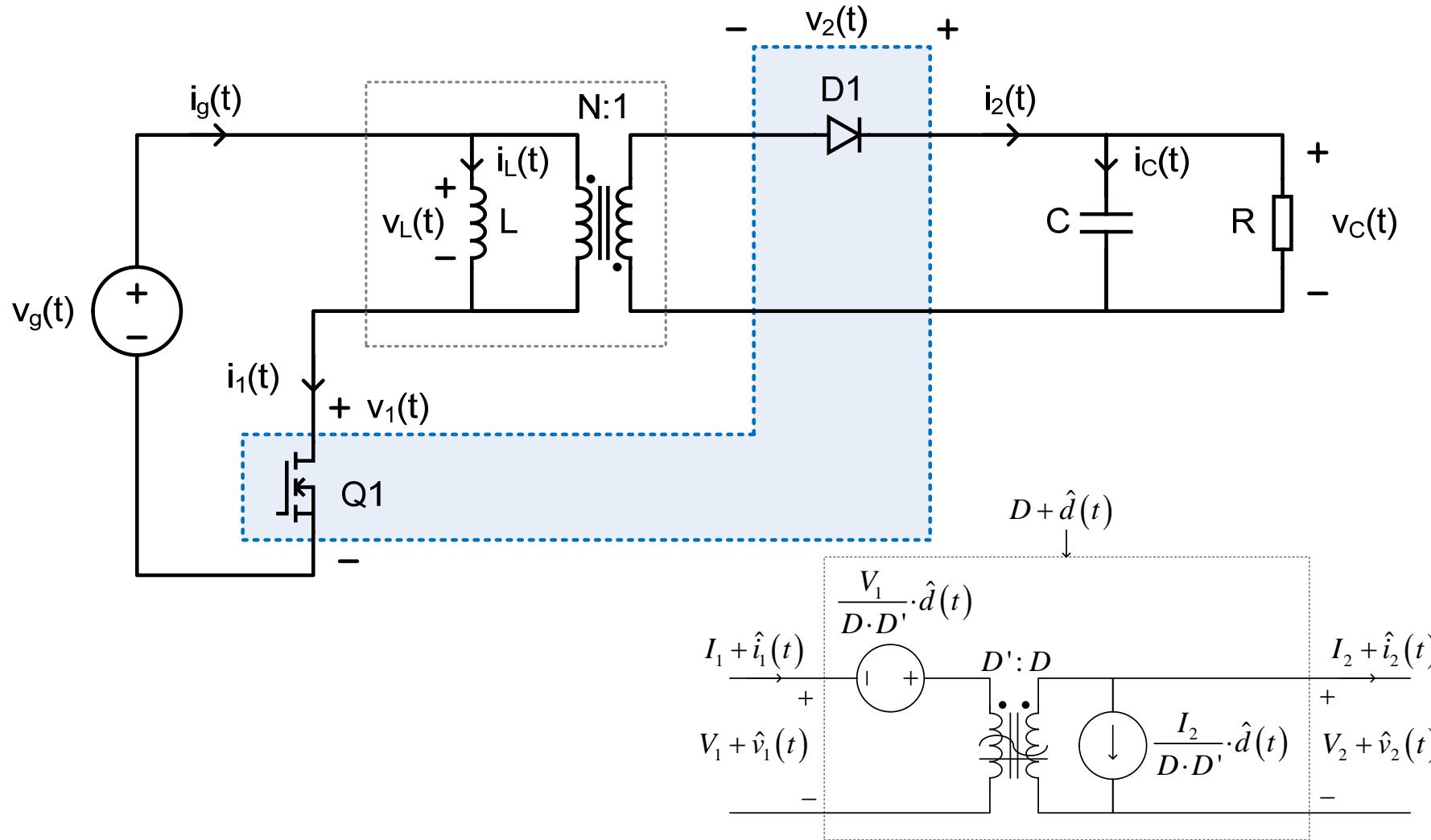
Averaged Switch Small Signal Model: Flyback



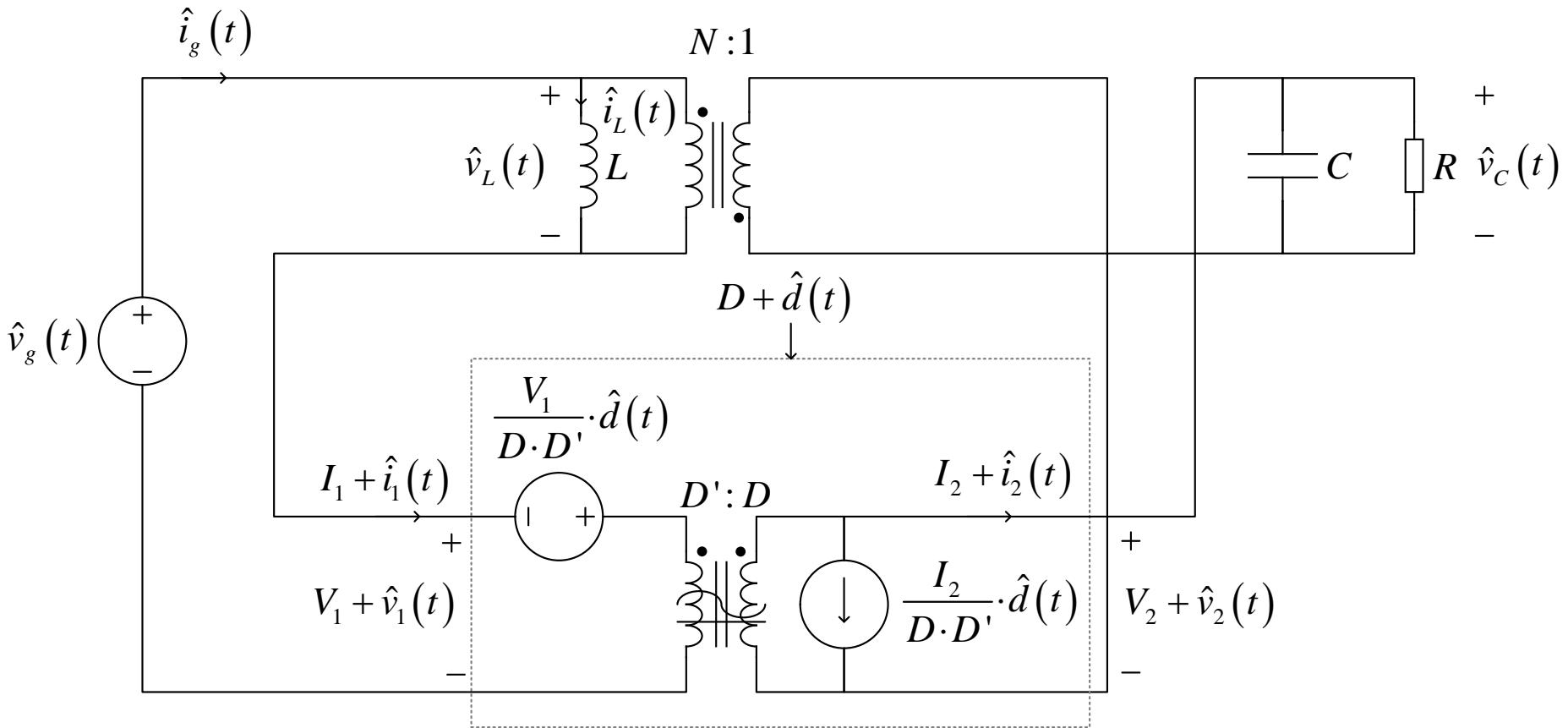Averaged Switch Small Signal Model: Flyback




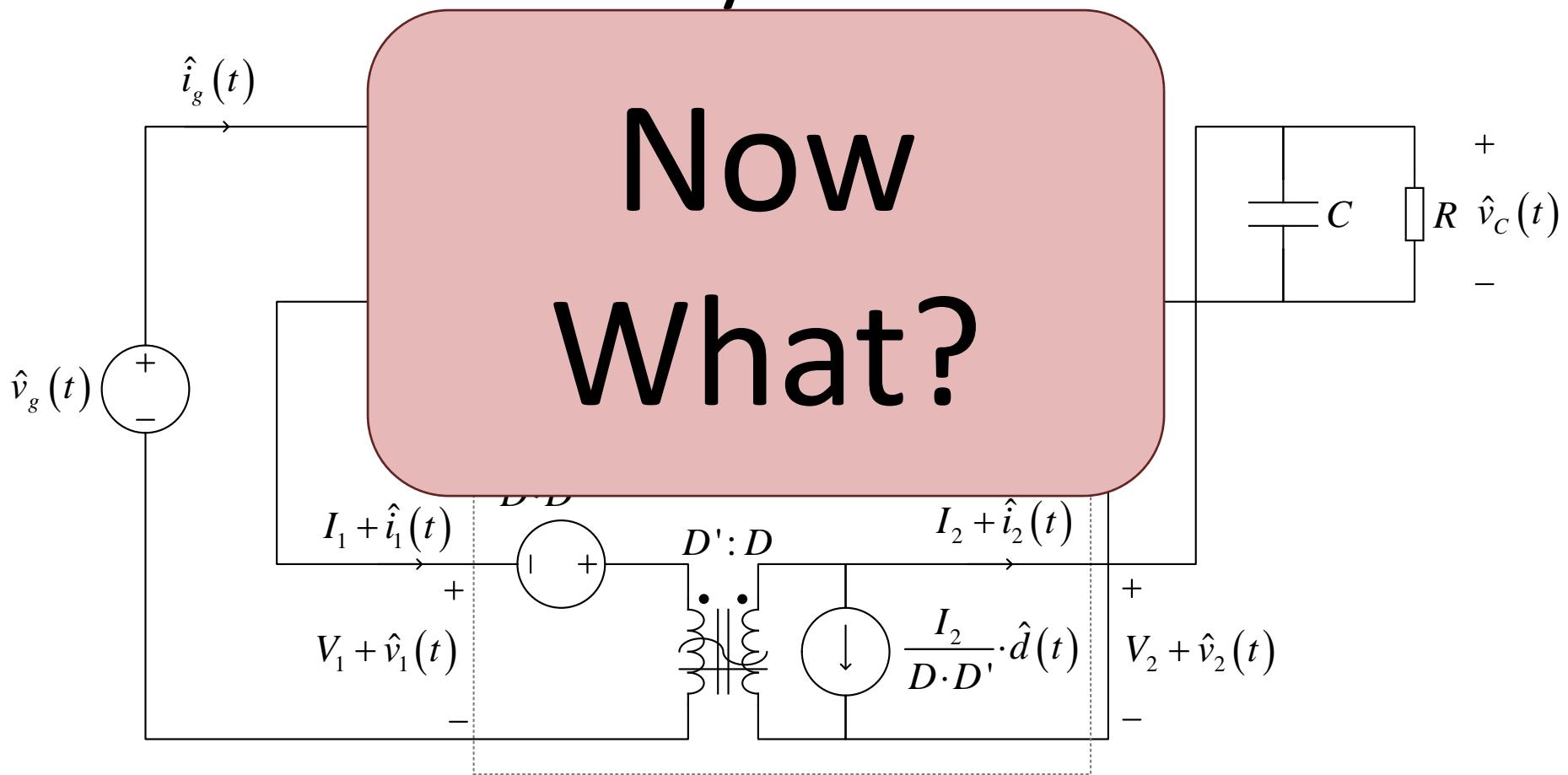Averaged Switch Small Signal Model: Flyback




Averaged Switch Small Signal Model: Flyback

Simulation: Maybe

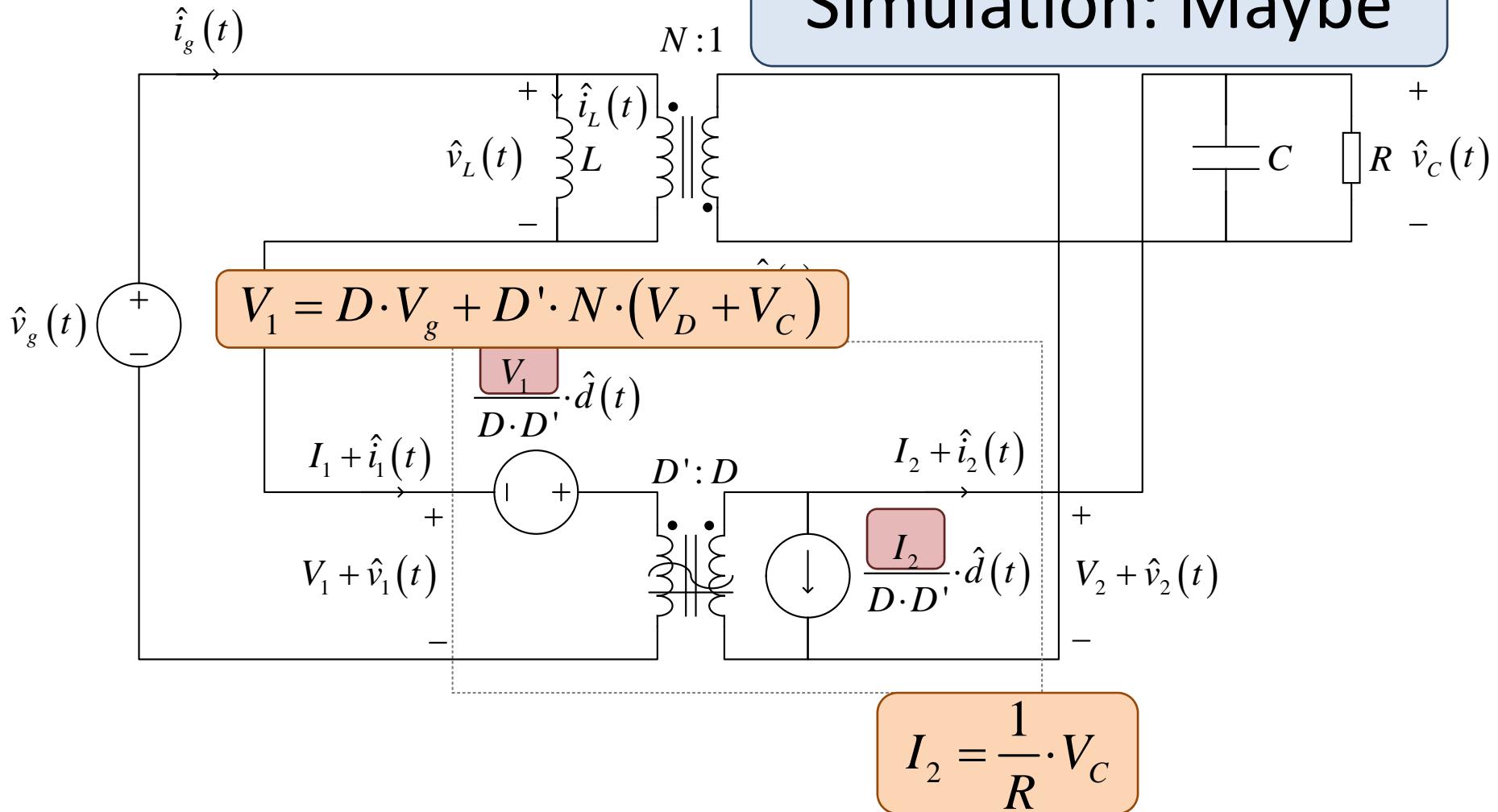


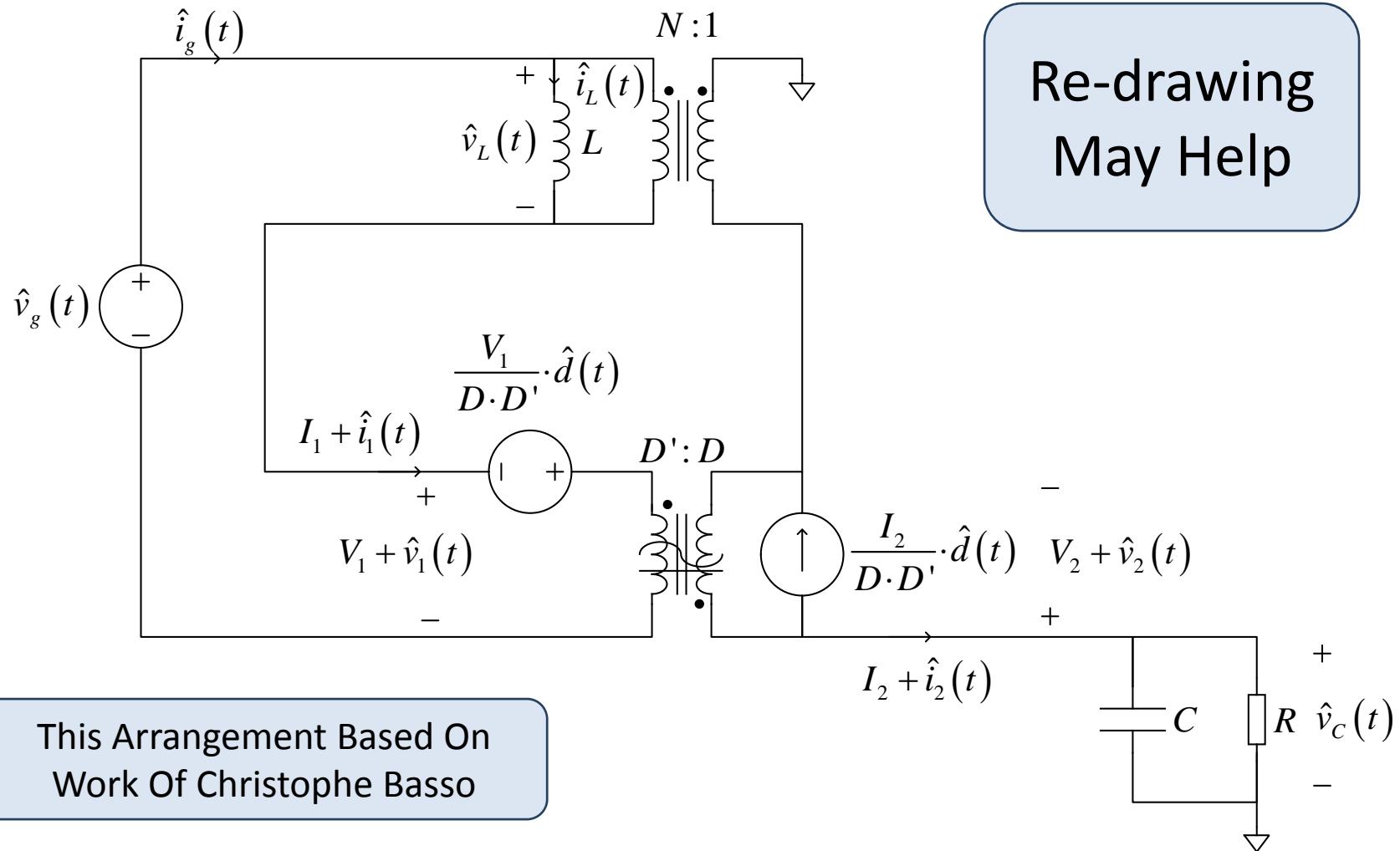Averaged Switch Small Signal Model: Flyback




Averaged Switch Small Signal Model: + Flyback


Re-draw
As For Averaged
Model

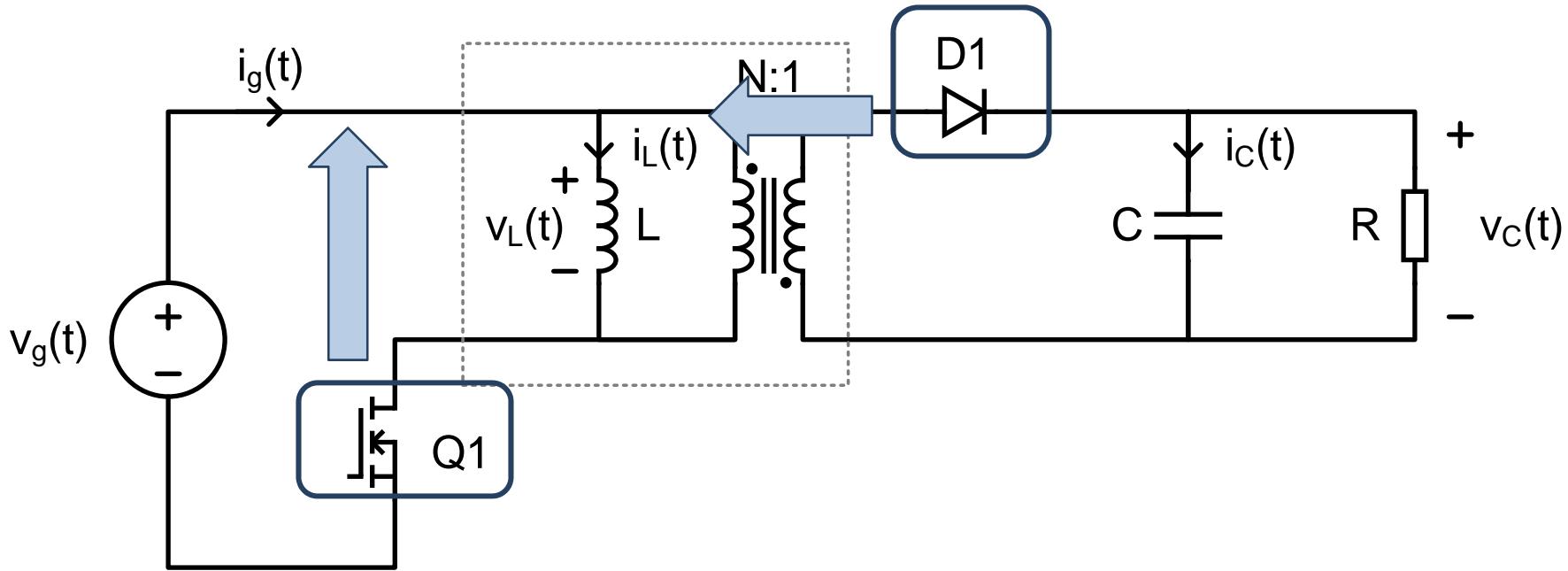

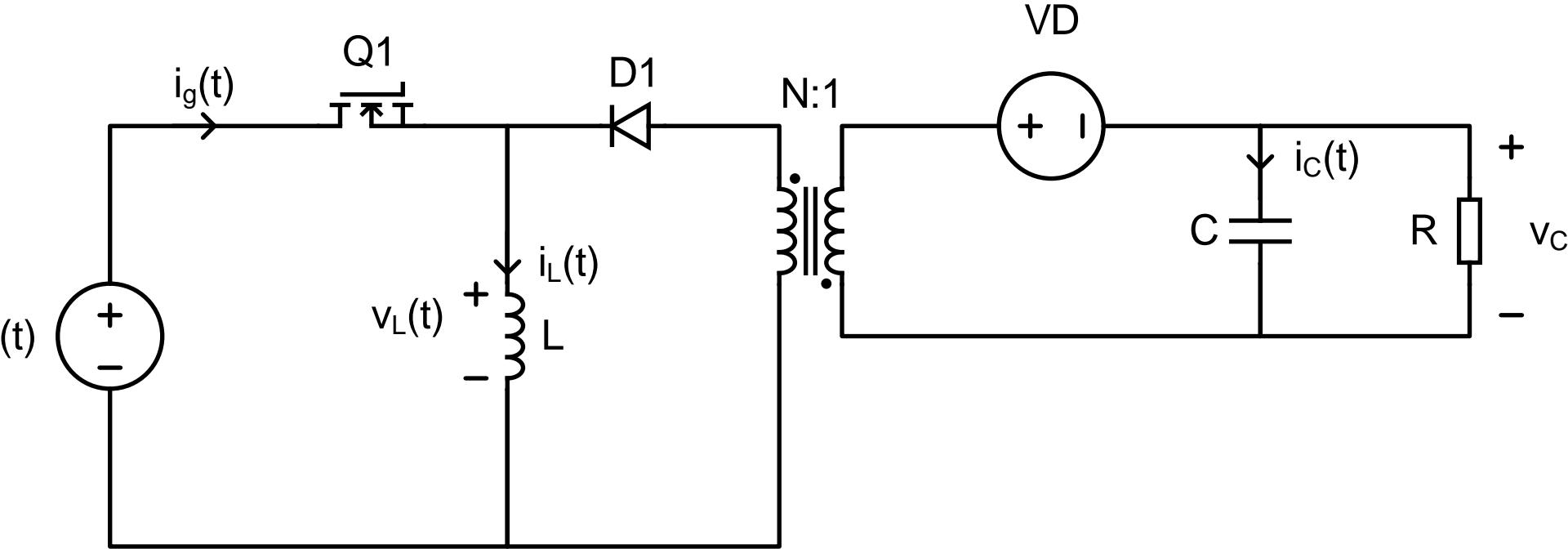
Averaged Switch Small Signal Model: + Flyback



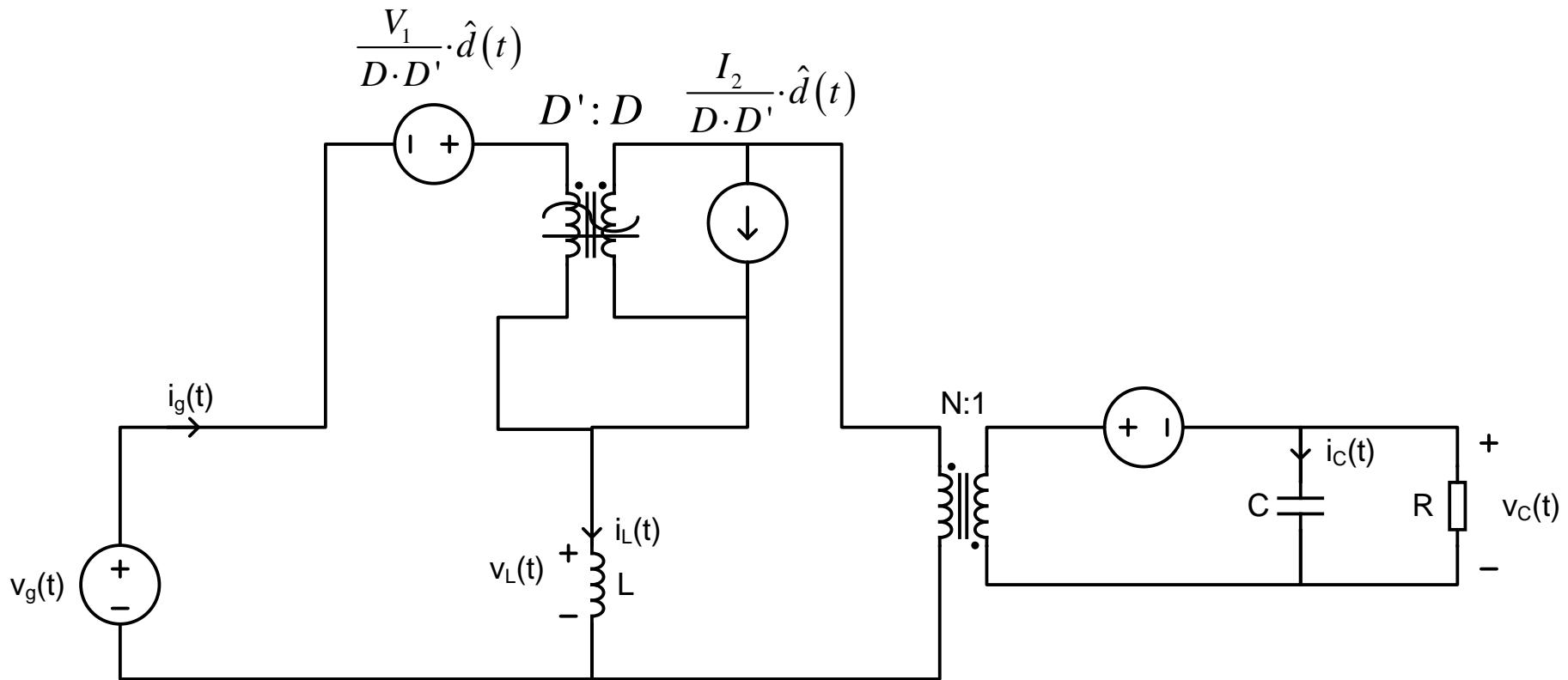Averaged Switch Small Signal Model: + Flyback



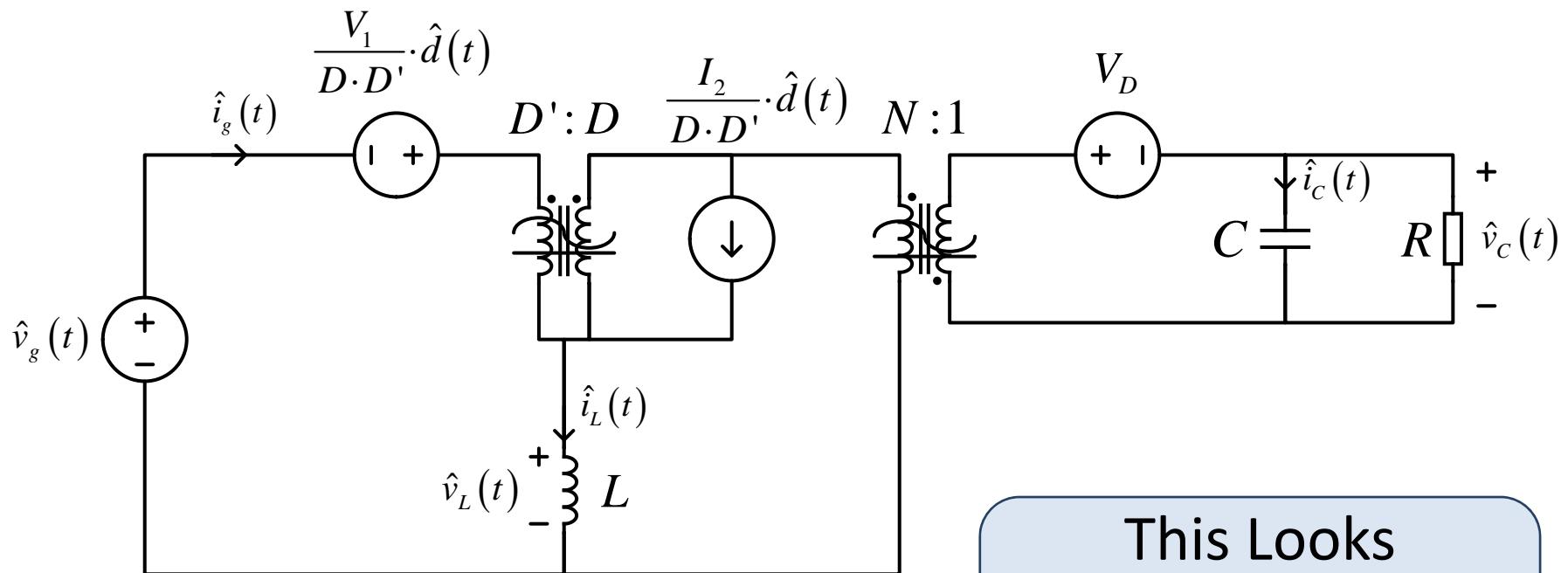
Averaged Switch Small Signal Model: + Flyback



This Looks
More
Promising


Averaged Switch Small Signal Model: Flyback

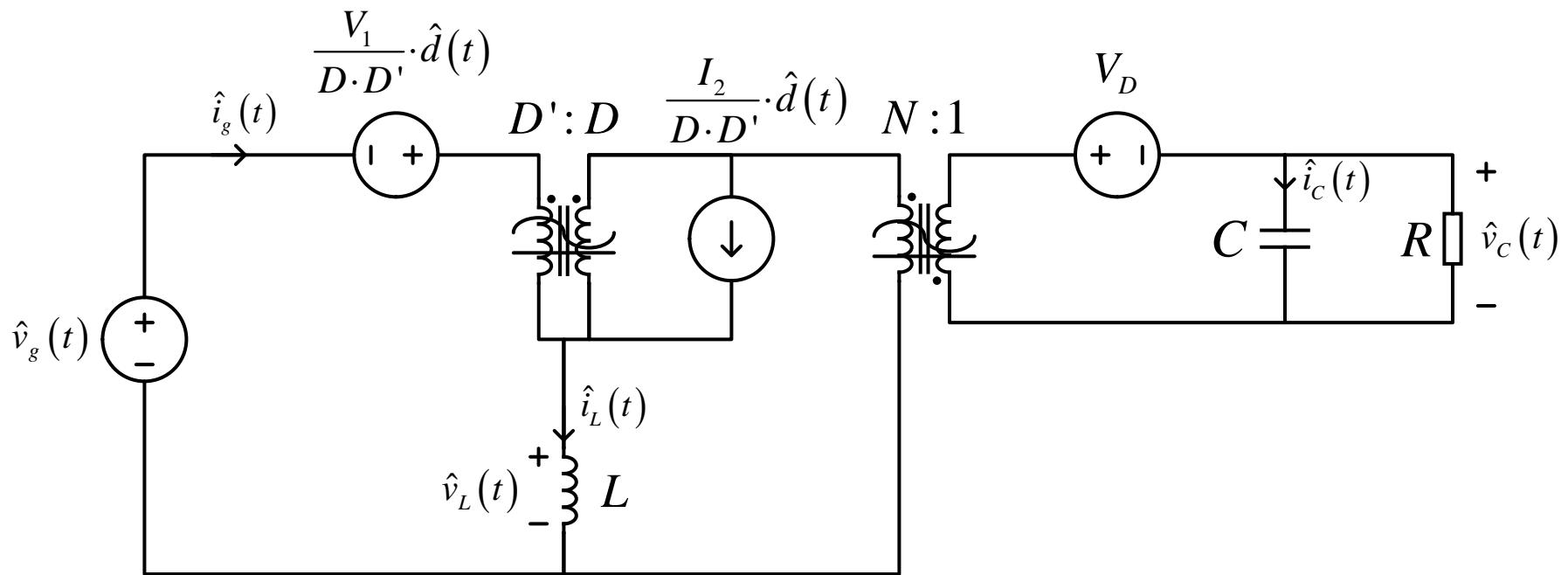Derive Transfer Functions?
Still Very Tedious




Averaged Switch Small Signal Model: Flyback

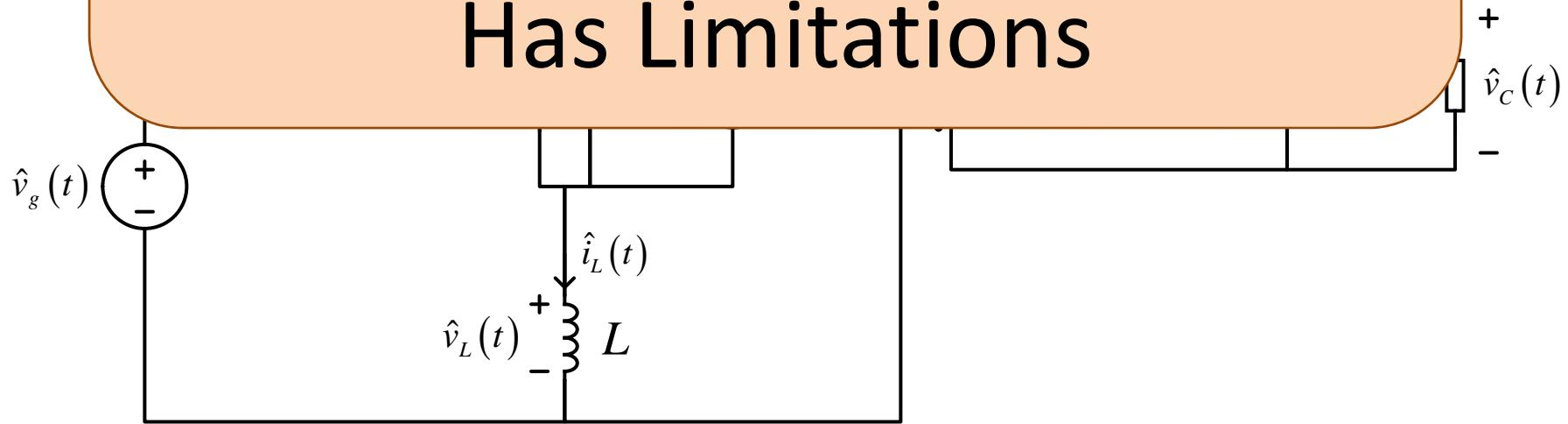The Point Of This Example?
Averaged Switch
Small Signal Modeling
Has Limitations




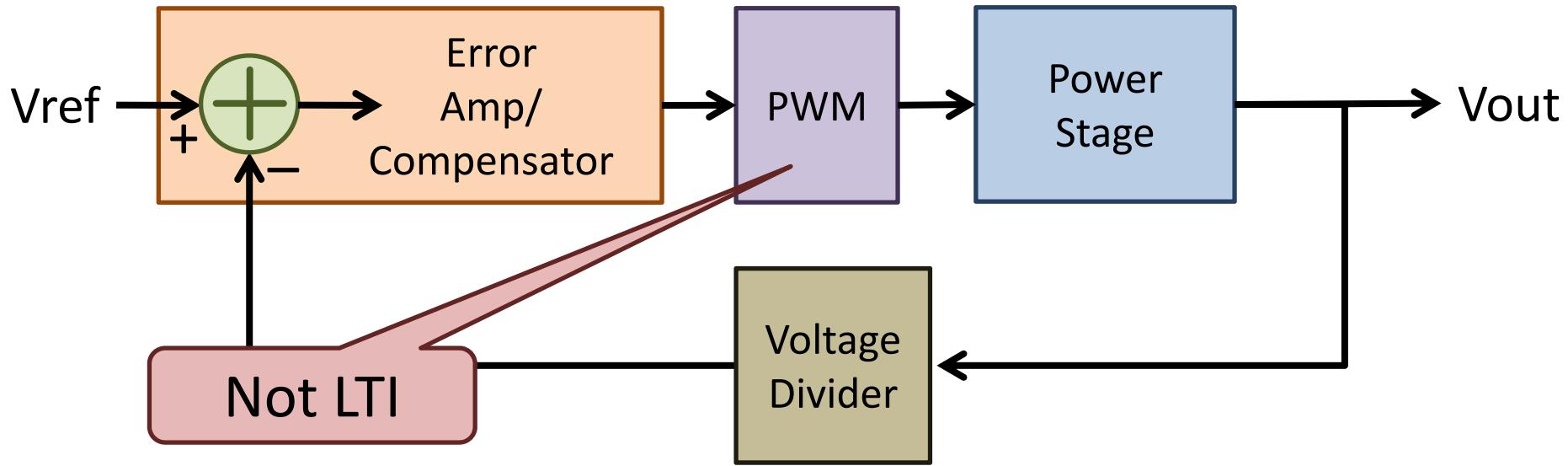Small Signal Model Of Pulse-Width Modulator




We Also Need A Small Signal Model
For The Pulse Width Modulator

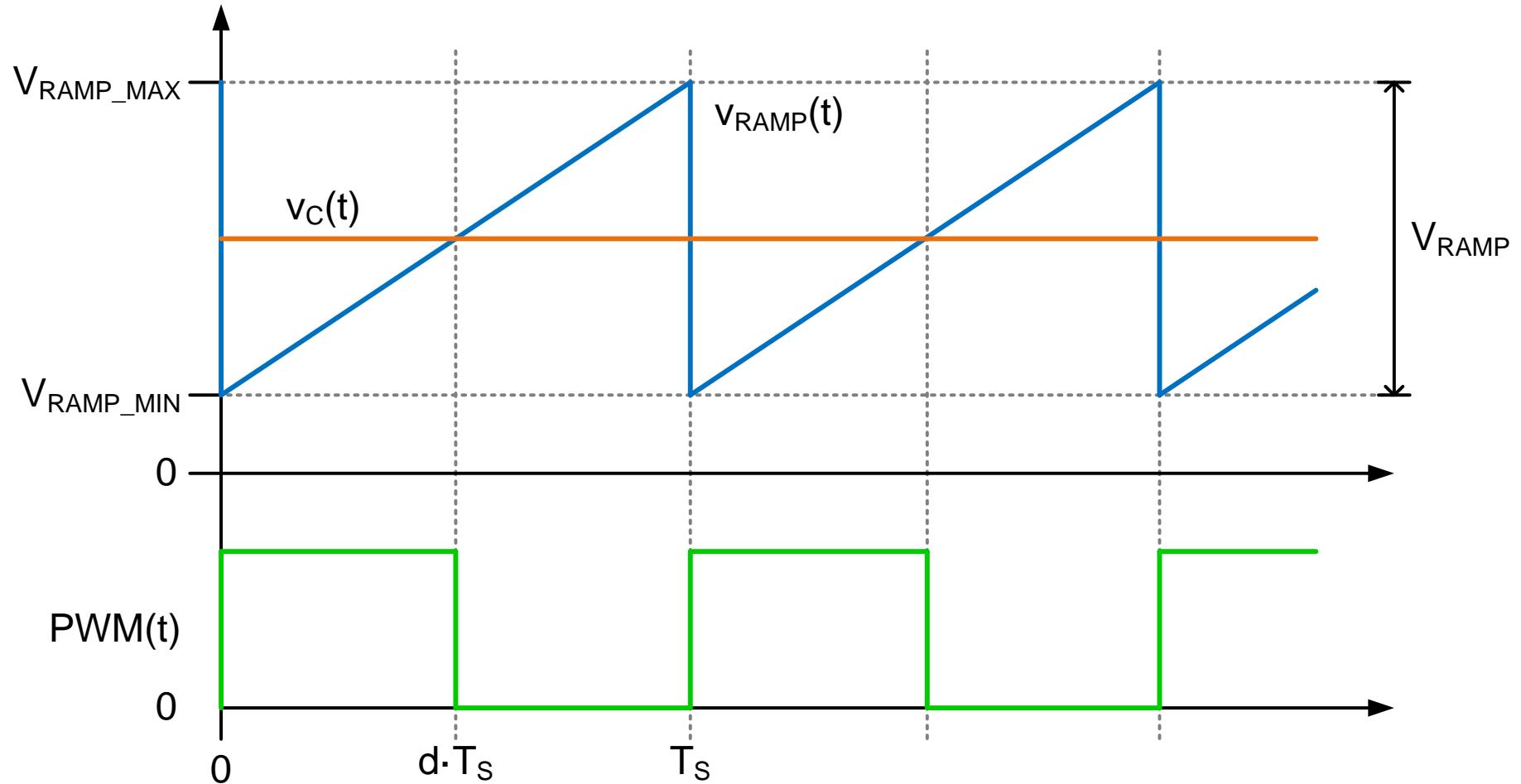Small Signal Model Of Pulse-Width Modulator



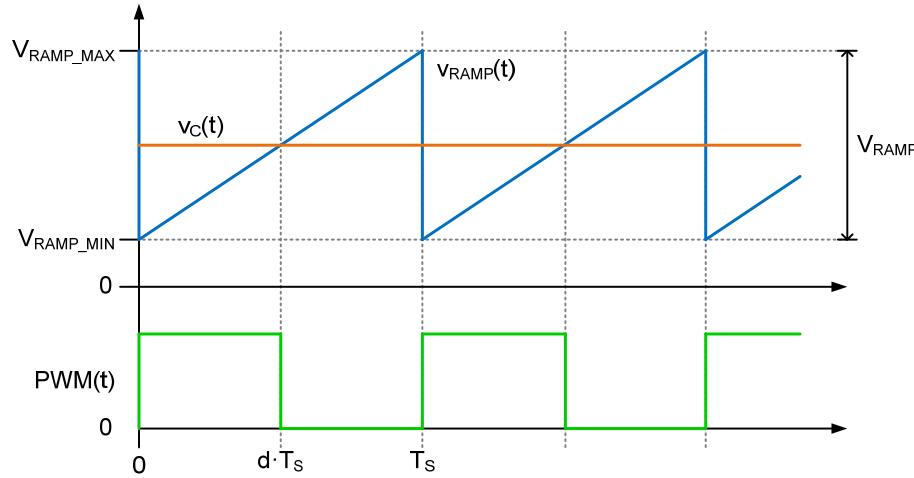Small Signal Model Of Pulse-Width Modulator



$$d(t) = \frac{v_c(t) - V_{RAMP_MIN}}{V_{RAMP}}$$

$$= \frac{v_c(t)}{V_{RAMP}} - \frac{V_{RAMP_MIN}}{V_{RAMP}}$$

$$d(t) = D + \hat{d}(t)$$

$$v_c(t) = V_c + \hat{v}_c(t)$$

$$D + \hat{d}(t) = \frac{V_c + \hat{v}_c(t)}{V_{RAMP}} - \frac{V_{RAMP_MIN}}{V_{RAMP}}$$

$$= \frac{\hat{v}_c(t)}{V_{RAMP}} + \frac{V_c - V_{RAMP_MIN}}{V_{RAMP}}$$


$$D = \frac{V_c - V_{RAMP_MIN}}{V_{RAMP}}$$

$$\hat{d}(t) = \frac{\hat{v}_c(t)}{V_{RAMP}}$$



Small Signal Model Of Pulse-Width Modulator

!

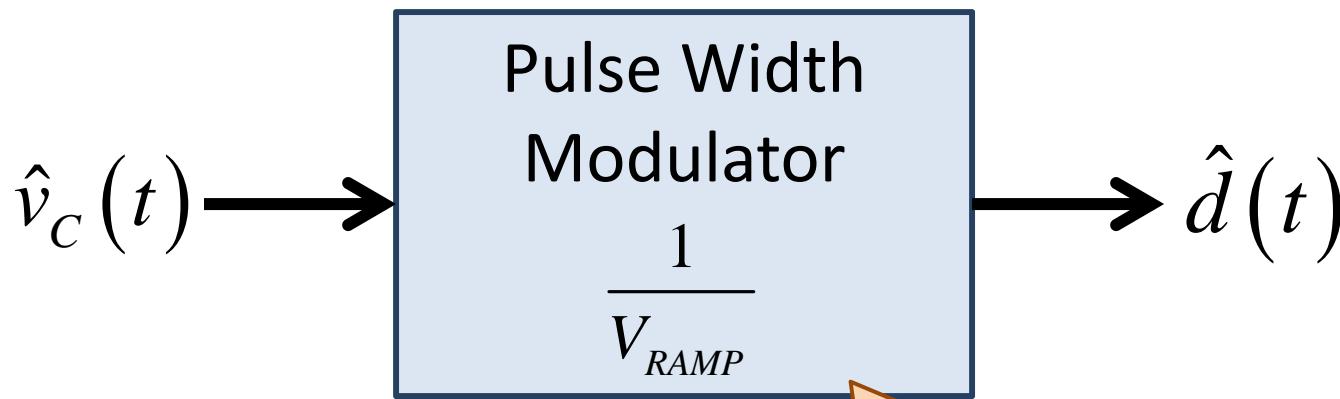

PWM Has A Fixed Small Signal Gain

More On Small Signal Modeling

- “Fundamentals of Power Electronics”, 2nd ed., Erickson and Maksimovic, Chapter 7
- V. Vorperian, "Simplified analysis of PWM converters using model of PWM switch. Continuous conduction mode," *Aerospace and Electronic Systems, IEEE Transactions on*, vol. 26, pp. 490-496, 1990.
- V. Vorperian, "Simplified analysis of PWM converters using model of PWM switch. II. Discontinuous conduction mode," *Aerospace and Electronic Systems, IEEE Transactions on*, vol. 26, pp. 497-505, 1990.
- Papers, seminars, books by Ray Ridley and Christophe Basso



Summary

- We Need Small Signal Models To Use Standard Control Tools To Design The Loop
- Two Averaging Methods Shown To Derive A Small Signal Model Of A Switching Converter:
 - Average Inductor Voltages And Capacitor Currents
 - Average Switch Network Port Voltages And Currents
- Transfer Functions Of Interest Can Be Found From The Small Signal Models



You Can Download The Latest Version Of The Seminar
In Adobe Acrobat (.pdf)
And Microsoft PowerPoint Show Format (.ppsx)
From The Embedded Power Labs website:
<http://www.embeddedpowerlabs.com/publications.html>

About The Presenter

Bob White has over 30 years experience in power electronics. He has held managerial and individual contributor positions in product development, technology development, applications and systems engineering, and technical marketing. His areas of expertise include power systems for computing and telecommunications systems, digital power, and applications of wide bandgap power semiconductor devices. Bob is currently the president and chief engineer of Embedded Power Labs, a power electronics consulting company.



Bob has been very active in the IEEE Power Electronics Society and the APEC committees, including twice serving as the APEC General Chair.

He is a Fellow of the IEEE, has a BSEE from MIT, a MSEE from Worcester Polytechnic Institute and is currently pursuing a Ph.D. in power electronics at the University of Colorado-Boulder. He is also an Honorable Discharged veteran of service in the United States Air Force.

